

Problem Solution #2

Calculation:

a. RG 58A/U: $\epsilon_r = 2.3$, $a \approx 0.4\text{mm}$, $b \approx 1.4\text{mm}$.

$$\mu_0 \approx 4\pi \times 10^{-7} \text{ H/m},$$

$$l = (\mu_0 / 2\pi) \ln(b/a) \approx (4\pi \times 10^{-7} / 2\pi) \ln(1.4/0.4) \approx 2.51 \times 10^{-7} \text{ H/m}$$

$$\epsilon = \epsilon_r \epsilon_0, \quad \epsilon_0 \approx 8.854 \times 10^{-12} \text{ F/m}, \quad \epsilon \approx 2.3 \times 8.854 \times 10^{-12} \approx 2.04 \times 10^{-11} \text{ F/m}$$

$$c = 2\pi\epsilon / \ln(b/a) = 2\pi \times 2.04 \times 10^{-11} / \ln(1.4/0.4) \approx 1.02 \times 10^{-10} \text{ F/m}$$

They are almost the same as the lumped circuit transmission lines in the lab.

To model a 4 meter section of the cable,

$$L = 4 \times l = 4 \times 2.51 \times 10^{-7} = 1.004 \times 10^{-6} \text{ H}$$

$$C = 4 \times c = 4 \times 1.02 \times 10^{-10} = 4.08 \times 10^{-10} \text{ F}$$

so we should choose $\boxed{L = 1.004 \times 10^{-6} \text{ H}}$ and $\boxed{C = 4.08 \times 10^{-10} \text{ F}}$

20 sections:

$$L_{total} = 20 \times L = 20 \times 1.004 \times 10^{-6} \approx 2 \times 10^{-6} \text{ H}$$

$$C_{total} = 20 \times C = 20 \times 4.08 \times 10^{-10} \approx 8.2 \times 10^{-9} \text{ F}$$

80 meters of RG 58:

$$L_{total} = 80 \times l = 80 \times 2.5 \times 10^{-7} = 2 \times 10^{-6} \text{ H}$$

$$C_{total} = 80 \times c = 80 \times 10^{-10} = 8 \times 10^{-9} \text{ F}$$

It's almost equivalent.

b. $V = V_0 \cos(\omega s)$ where $s = t \pm (z/u)$

$$\frac{\partial s}{\partial z} = \pm \frac{1}{u}, \quad \frac{\partial s}{\partial t} = 1, \quad \frac{dV}{ds} = -V_0 \omega \sin(\omega s)$$

$$\begin{aligned} \frac{\partial^2 V}{\partial z^2} &= \frac{\partial}{\partial z} \left(\frac{dV}{ds} \frac{\partial s}{\partial z} \right) = \frac{\partial}{\partial z} \left[-V_0 \omega \sin(\omega s) \frac{\partial s}{\partial z} \right] = -V_0 \omega^2 \cos(\omega s) \left(\pm \frac{1}{u} \right) \frac{\partial s}{\partial z} = -V_0 \omega^2 \cos(\omega s) \left(\pm \frac{1}{u} \right)^2 \\ &= -V_0 \omega^2 \cos(\omega s) \frac{1}{u^2} \end{aligned}$$

$$\frac{\partial^2 V}{\partial t^2} = \frac{\partial}{\partial t} \left(\frac{dV}{ds} \frac{\partial s}{\partial t} \right) = \frac{\partial}{\partial t} \left[-V_0 \omega \sin(\omega s) \frac{\partial s}{\partial t} \right] = -V_0 \omega^2 \cos(\omega s) \frac{\partial s}{\partial t} = -V_0 \omega^2 \cos(\omega s)$$

Since
$$\frac{\partial^2 V(z,t)}{\partial z^2} - lc \frac{\partial^2 V(z,t)}{\partial t^2} = 0,$$

$$-V_0 \omega^2 \cos(\omega s) \frac{1}{u^2} - lc [-V_0 \omega^2 \cos(\omega s)] = 0, \quad \text{This gives } \boxed{u = 1/\sqrt{lc}}$$

For the RG 58 A/U cable,

$$u = 1/\sqrt{lc} = 1/\sqrt{2.51 \times 10^{-7} \times 1.02 \times 10^{-10}} \approx \boxed{1.98 \times 10^8 \text{ m/s}}$$

The time delay for the 4 meter section is,

$$t = z/u = 4/1.98 \times 10^8 \approx \boxed{2.02 \times 10^{-8} \text{ s}}$$

Substitute $V = V_0 \cos(\omega s)$ and $I = I_0 \cos(\omega s)$, where $s = t \pm (z/u)$, into transmission line equation $-\frac{\partial I(z,t)}{\partial z} = GV(z,t) + c \frac{\partial V(z,t)}{\partial z}$, $G=0$.

$$I_0 \omega \sin(\omega s) \left(\pm \frac{1}{u} \right) = -c V_0 \omega \sin(\omega s)$$

$$Z_0 = \left| \frac{V_0}{I_0} \right| = \frac{1}{cu} = \frac{1}{c(1/\sqrt{lc})} = \sqrt{l/c}$$

The characteristic impedance of the cable is,

$$Z_0 = \sqrt{2.51 \times 10^{-7} / 1.02 \times 10^{-10}} \approx \boxed{49.6 \Omega}$$