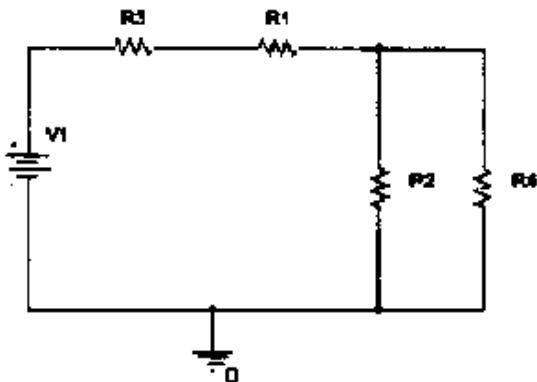


ENGR4300 Test 1B
Spring 2002

Name Answer Key
 Section _____

I. Resistive circuits (20 points)



In the circuit above, $V_1 = 5$ volts. $R_1 = 1000\Omega$, $R_2 = 1000\Omega$, $R_3 = 100\Omega$, $R_4 = 3000\Omega$

a) (10 points) Find the amplitude of the voltage across R_1 .

$$R_{24} = \frac{1K \cdot 3K}{1K+3K} = .75K\Omega \quad R_{eq} = R_3 + R_1 + R_{24}$$

$$= 100 + 1000 + 750$$

$$= 1850\Omega$$

$$I_T = \frac{V_T}{R_{eq}} = \frac{5}{1850} = 2.7mA \quad V_i = I_T R_1$$

b) (10 points) Find the current through R_4 .

$$V_i = (2.7m)(1K) =$$

$$\boxed{V_i = 2.7V}$$

$$V_{24} = I \cdot R_{24} = (2.7m)(.75K)$$

$$= 2.025V$$

$$V_4 = I_4 R_4$$


$$2.025 = I_4 (3000)$$

$$\boxed{I_4 = .675mA}$$

ENGR4300 Test 1B
Spring 2002

Name _____
 Section _____

2. Thevenin circuits (20 points)

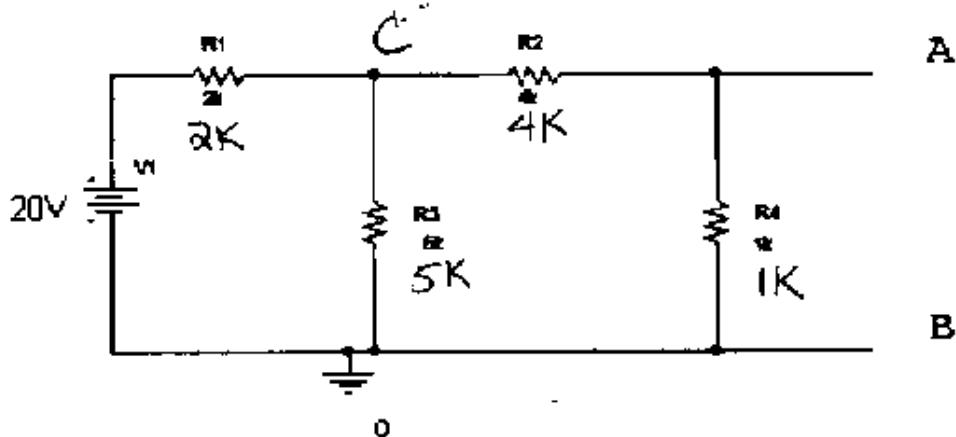


a) Find the Thevenin Voltage (V_{oc}) of the Circuit (8 points)

$$R_{24} = 4K + 1K = 5K \quad R_{324} = \frac{5K \cdot 5K}{5K + 5K} = 2.5K$$

$$V_C = 20 \left(\frac{2.5K}{2K + 2.5K} \right) = 11.11V$$

$$V_A = 11.11 \left(\frac{1K}{1K + 4K} \right) = 2.22V \quad V_B = 0 \quad | \quad V_{AB} = 2.22V$$

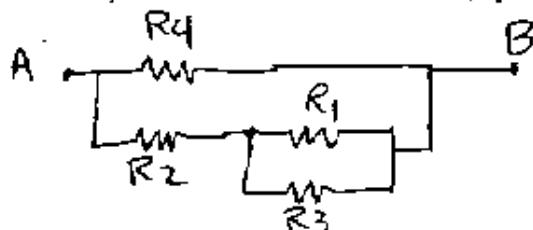b) Find the Thevenin Resistance (8 points)




$$R_{13} = \frac{2K \cdot 5K}{2K + 5K} = 1.43K\Omega$$

$$R_{213} = 4K + 1.43K = 5.43K\Omega$$

$$R_{4213} = \frac{5.43K + 1K}{5.43K + 1K} = .844K\Omega = 844\Omega$$

c) Draw the Standard Thevenin Circuit, including a load Resistor (4 points)

$$R_{Th} = 844\Omega$$

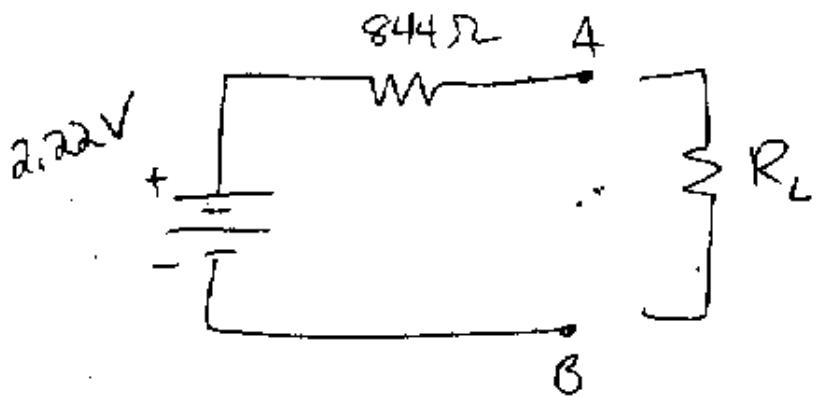


ENGR4300 Test 1B
Spring 2002

Name _____

Section _____

3. Sine Waves (20 points)

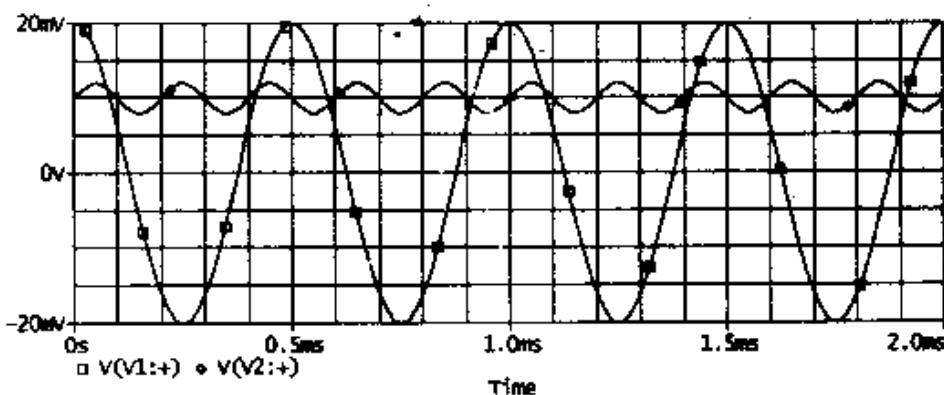

- a) Consider trace A in the plot above and give the following values (6 points):

(Do not forget the units.)

$$\text{frequency: } 2K \text{ Hz}$$

$$\text{amplitude: } 20 \text{ mV}$$

$$\text{rms value: } \frac{20}{\sqrt{2}} = 14.1 \text{ mV}$$

$$\text{peak-to-peak voltage: } 40 \text{ mV}$$

$$\text{phase shift: } +\frac{\pi}{2} \text{ rad}$$

$$\text{offset voltage: } 10 \text{ mV}$$

$$f = \frac{1}{T} \quad T = 1.5 \text{ ms} \quad f = 2K \text{ Hz}$$

$$\phi = -\omega t_0 = -2\pi \left(\frac{-12.5 \text{ ms}}{1.5 \text{ ms}} \right)$$

$$\phi = +0.5\pi = \frac{\pi}{2}$$

- b) Write down the mathematical expression for A in the form $v(t) = V_{dc} + A \sin(\omega t + \phi)$.

(4 points)

$$v(t) = 10 + 20 \sin(4000\pi t + \frac{\pi}{2}) \quad \omega = 2\pi f = 2\pi(2K) \\ = 4K\pi \\ = 12566.37 \text{ rad/sec}$$

- c) Consider trace B in the plot above and give the following values (6 points):

(Do not forget the units.)

$$\text{frequency: } 5K \text{ Hz}$$

$$\text{amplitude: } 2 \text{ mV}$$

$$\text{rms value: } (\text{see next page})$$

$$\text{peak-to-peak voltage: } 4 \text{ mV}$$

$$\text{phase shift: } \phi \text{ rad}$$

$$\text{offset voltage: } 10 \text{ mV}$$

$$f = \frac{1}{T} = \frac{1}{0.2 \text{ ms}} = 5K \text{ Hz}$$

$$2\pi f = (2\pi)(5K) = 10K\pi$$

$$= 314,159.26 \text{ rad/sec}$$

- d) Write down the mathematical expression for B in the form $v(t) = V_{dc} + A \sin(\omega t + \phi)$.

(4 points)

$$v(t) = 10 + 0.02 \sin(314,159.26 t)$$

V_{rms}

[1] No DC offset

$$V_{\text{rms}} = \frac{V_{\text{Amp}}}{\sqrt{2}}$$

[2] With DC offset

$$V_{\text{rms}} = \sqrt{(V_{\text{DC}})^2 + \frac{(V_{\text{Amp}})^2}{2}}$$

Test B

$$V_{\text{rms}} = \sqrt{(10m)^2 + \frac{(2m)^2}{2}}$$

$$V_{\text{rms}} = 10.1 \text{ mV}$$

Test A

$$V_{\text{rms}} = \sqrt{(5m)^2 + \frac{(2m)^2}{2}}$$


$$V_{\text{rms}} = 5.2 \text{ mV}$$

Since we did not cover this equation, you were all given the point. (Thank you, AC for clarification)

ENGR4300 Test 1B
Spring 2002


Name Answer Key
 Section _____

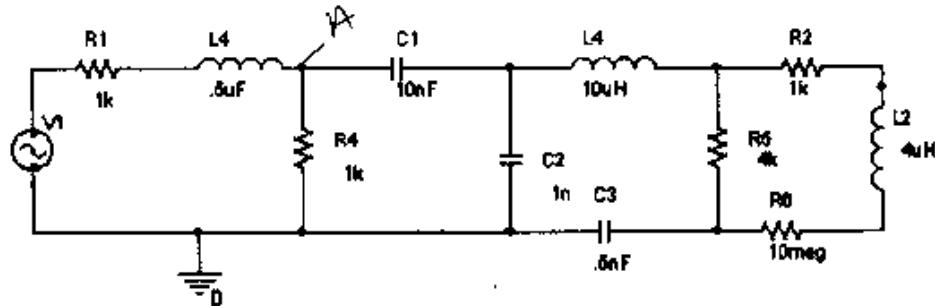4. Inductance and Capacitance at very high and very low frequencies (20 points).



Given that you know that inductors and capacitors can behave like short and open circuits at very high and low frequencies, we want to redraw the above circuit by replacing components that look like open circuits by open circuits and components that look like short circuits by short circuits.

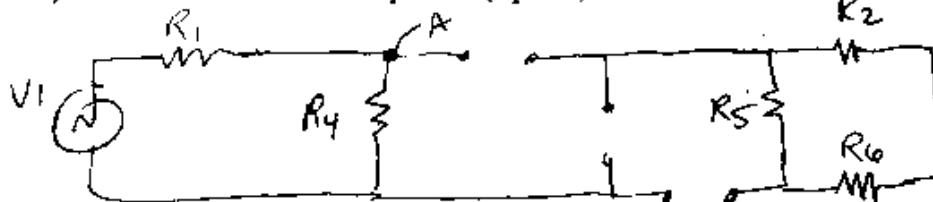a) Redraw this circuit at low frequencies (8 points).



b) At low frequencies, this circuit behaves most like (circle one) (2 points)


a voltage divider

an open circuit

a short

an op amp

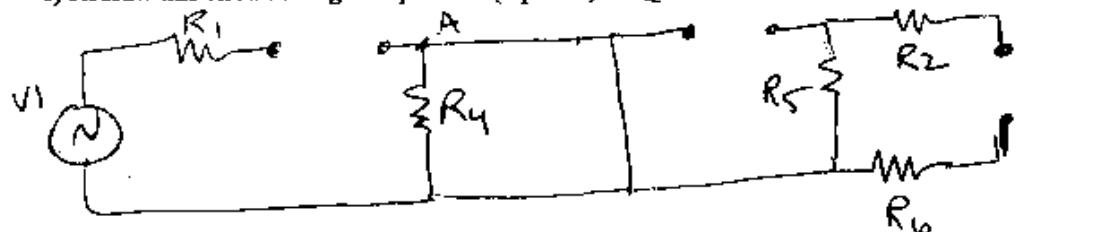c) Redraw this circuit at high frequencies (8 points).



d) At high frequencies, this circuit behaves most like (circle one) (2 points).

a voltage divider

an open circuit


a short

an op amp

ENGR4300 Test 1A
Spring 2002

Name _____
 Section _____

5. Instrumentation (20 points)

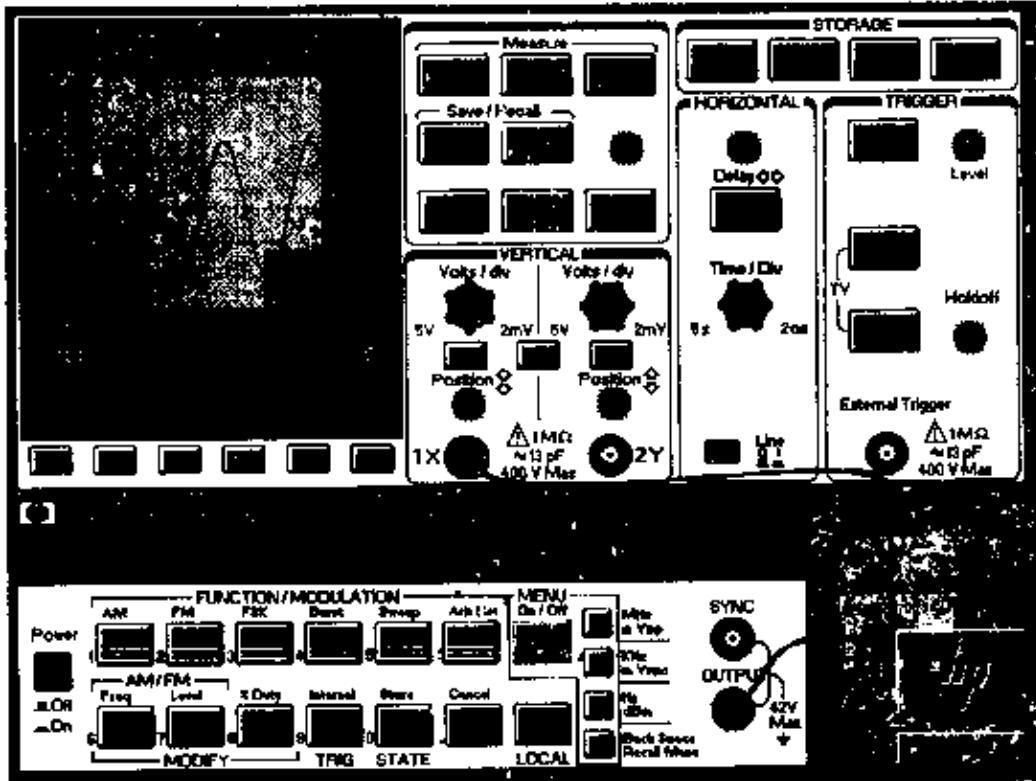

a) List two ways to obtain the frequency of the signal using the oscilloscope (4 points)

- 1) Use TIME button to display frequency of signal.
- 2) Use scale (20μs per division) to find the period (50μs)
and take inverse (20 KHz)

b) When the function generator is connected to the scope you should notice a discrepancy between the reading on the display panel of the function generator, and the signal displayed on the scope. What discrepancy do you see and which device is correct?

(2 points) Why? (6 points)

The scope shows the peak-to-peak voltage as 800mV and the function generator shows 400mV. The scope is right. The function generator expects a 50Ω load, but the load of the scope is 1MΩ.

This very large load is so far from the expected load, that the scope ends up showing

c) Explain as simply as possible how to set up the function generator and scope to display the signal shown. (Use of Autoscale is NOT allowed). Give specific values.

(8 points)

- 1) Set FG to 20KHz
 - 2) set FG Amp to 400mVp-p
 - 3) turn off FG offset
 - 4) set Volts/div on scope channel 1 to 200mV
 - 5) set time/div on scope to 20μs.
 - (e) move position of trace to 0.5 on channel 1
- to 200mV
trace the amount on the generator.