


# ENGR4300 Test 1A

## Spring 2005

Name \_\_\_\_\_  
Section \_\_\_\_\_

### 1) Resistive Circuits (25 points)

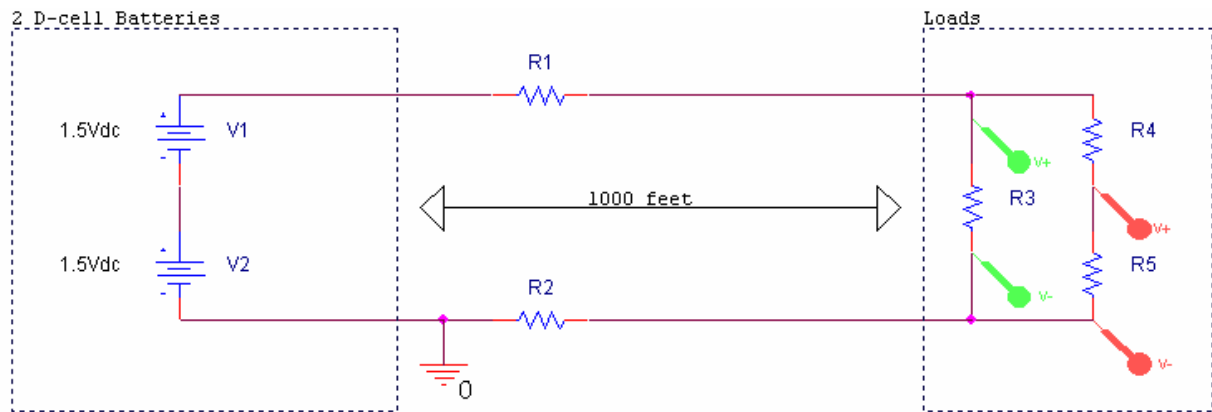**Part A** Two series connected D-cell batteries power three loads over an extension cable 1000' long. The cable is made using 24AWG (American Wire Gauge) wire that has a resistance of  $27.3\Omega/1000'$ . The figure below shows this resistance as  $R1=27.3\Omega$  &  $R2=27.3\Omega$ . Loads  $R3=1k\Omega$ ,  $R4=800\Omega$ ,  $R5=400\Omega$  and are configured as shown in the circuit below. All calculations should be carried to three decimal places.



$R1=27.3\Omega$   $R2=27.3\Omega$   $R3=1K\Omega$   $R4=800\Omega$   $R5=400\Omega$

a) What is the total resistance seen by the batteries? (6 points):

$$R_{45} = 800 + 400 = 1200 \quad R_{345} = (1000 \times 1200) / (1000 + 1200) = 545.454$$

$$R_T = 27.3 + 545.454 + 27.3 = \mathbf{600.054\Omega}$$

b) Find the current that will be drawn from the batteries (2 points):

$$V_T = 1.5 + 1.5 = 3 \quad I = V_T / R_T = 3 / 600.054 = \mathbf{5.000 \text{ mA}}$$

c) Assuming all resistors are exactly their stated value, find the voltage drop across R3 and R5. (6 points):

$$R3: V3 = V_{345} = V_T \times (R_{345} / R_T) = 3(545.454) / 600.054 = \mathbf{2.727 \text{ V}}$$

$$R5: V5 = V_{345} \times R5 / (R_{45}) = 2.727(400) / (1200) = \mathbf{0.909 \text{ V}}$$

# ENGR4300 Test 1A

## Spring 2005

Name \_\_\_\_\_  
Section \_\_\_\_\_

d) If the last color band on all resistors is red (+/- 2%), what are the minimum and maximum *currents* R3, R4 and R5 together should draw from the batteries? (3 points):

$$\text{Maximum} = R_{345} + R_{345} \times 0.02 = 545.454 + 10.909 = 556.363 \Omega$$

$$\text{Minimum} = R_{345} - R_{345} \times 0.02 = 545.454 - 10.909 = 534.545 \Omega$$

Recalculate voltage

$$V_{R234} = 3(R_{234}/RT) \quad I_{R234} = V_{R3}/R_{345}$$

$$\text{Maximum: } RT = 534.545 + 2(27.3) = 589.145 \quad VR_{234} = (534.545/589.145)(3) = 2.722V$$

$$I_{R234} = 2.722/534.634 = \mathbf{5.092mA}$$


$$\text{Minimum: } RT = 556.363 + 2(27.3) = 610.963 \quad VR_{234} = (556.363/610.963)(3) = 2.732$$

$$I_{R234} = 2.732/556.363 = \mathbf{4.910mA}$$

Part B Now suppose our D-cell batteries are replaced by an ideal function generator (no 50 ohm internal impedance to worry about):

Ideal Function

Generator (having no internal impedance)

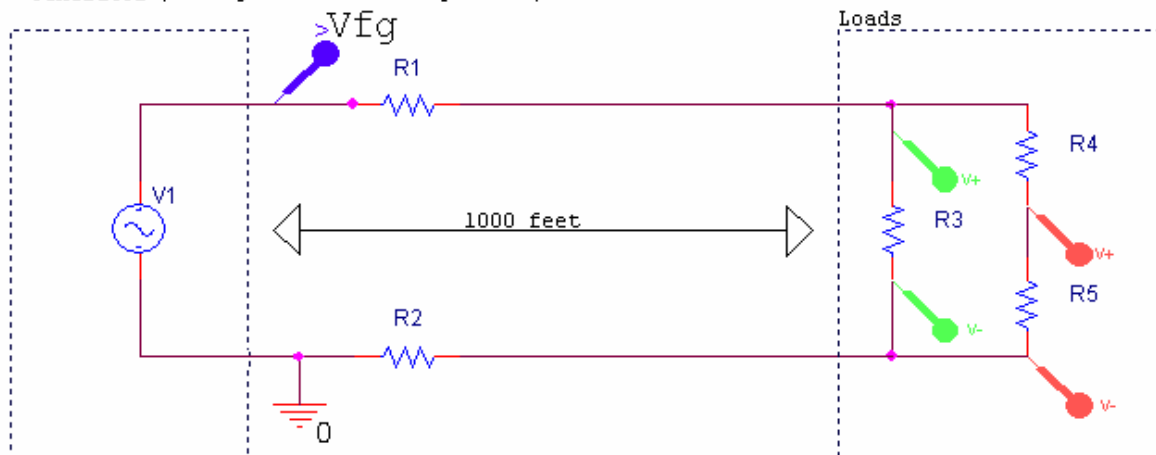

V1: VOFF=3V VAMPL = 5V FREQ = 1KHz

R1=27.3Ω R2=27.3Ω R3=1KΩ R4=800Ω R5=400Ω

# ENGR4300 Test 1A

## Spring 2005

Name \_\_\_\_\_  
Section \_\_\_\_\_

a) What is the maximum voltage at Vfg referenced to ground (1 point)?

$$\text{Maximum } V_{fg} = V_{OFF} + V_{AMPL} = 3 + 5 = 8V$$


b) What is the minimum voltage at Vfg referenced to ground (1 point)?

$$\text{Minimum } V_{fg} = V_{OFF} - V_{AMPL} = 3 - 5 = -2V$$

c) What is the average voltage at Vfg referenced to ground (1 point)?

$$\text{Average } V_{fg} = V_{OFF} = 3V$$

 d) On the graph below, using pencil if you have one, sketch and label the voltage at Vfg. Start the drawing with  $V_{fg} = V_{avg}$  at time zero (5 points). (blue trace)



*Extra Credit:* On the same graph, sketch and label the voltage drop across R5 assuming the waveform drawn in (d) as the input signal. Show all calculations required below (1 extra point). (red trace)

*Since DC offset is 3V. It can be handled in the same manner as the 3 volts from the 2 1.5 volt batteries. This means the DC offset of the voltage across R5 is 0.909V (from part c). We can also apply the procedure we used to the amplitude (5V) to find the new amplitude*

$$R3: V3 = V345 = V_{AMPL} \times (R345) / RT = 5(545.454) / 600.054 = 4.545 V$$

$$R5: V5 = V345 \times R5 / (R45) = 4.545(400) / (1200) = 1.515 \text{ volts}$$

*The red trace has a DC offset of about 1V and an amplitude of about 1.5 V*


# ENGR4300 Test 1A

## Spring 2005


Name \_\_\_\_\_  
Section \_\_\_\_\_

### 2) Filters (25 points)

 
Part A: You want to determine what type of filter the following circuit is.



 a) Redraw the circuit at very low frequencies. (2 points)



 b) Redraw the circuit at very high frequencies. (2 points)



**ENGR4300 Test 1A**  
**Spring 2005**

Name \_\_\_\_\_  
Section \_\_\_\_\_

c) What is the value of  $V_{out}$  at very low frequencies? (1 point)

$$V_{out} = 0V$$

d) What is the value of  $V_{out}$  at very high frequencies? (1 point)

$$V_{out} = 0V$$

e) What type of filter is this? (1 point)

***Band Pass Filter***

*Part B:* You wire the circuit in Part A of this question on your protoboard with real components.

a) Your capacitor,  $C$ , has “683” written on it. What is its rated value in microfarads? (2 points)

$$C = 68 \times 10^3 \times 10^{-6} = 0.068 \mu F$$

b) Your resistor,  $R$ , has an orange band, a black band, a red band, and a gold band (5% tolerance) in that order. What is the rated value of the resistor? (2 points)

$$R = 30 \times 10^2 = 3K\Omega \pm 5\%$$

c) Your inductor,  $L$ , is long and thin. It has 300 turns, a core diameter of 0.5 cm, a coil length of 5 cm, a wire gauge of 26 (diameter=0.4 mm). It is wound around an air core ( $\mu = 4\pi \times 10^{-7}$  H/m). Calculate an estimate for the inductance. (4 points)

$$L = \mu N^2 \pi r^2 / d = 4\pi (10^{-7}) (300^2) \pi (.0025^2) / .05 = 44.4 \mu H$$

**ENGR4300 Test 1A**  
**Spring 2005**

Name \_\_\_\_\_  
Section \_\_\_\_\_

d) Based on the values of the components, give an estimate for the resonant frequency of the circuit in Hertz. (3 points)

$$f = 1/(2\pi\sqrt{LC}) = 1/(2\pi\sqrt{44.4\mu\times 0.068\mu}) = \mathbf{91.6\text{ K Hertz}}$$

e) If input a signal,  $v(t)=2V \sin(2\pi Kt)$ , is applied at the input to your circuit, will your output amplitude be less than, greater than, or about equal to the input amplitude? Explain why. (3 points)

$$\omega=2\pi K \quad 2\pi f=2K\pi \quad f=1000\text{ Hertz}$$

*The resonance is at around 92000 Hertz. The band will pass only frequencies around the resonance. The input frequency of about 1000 Hertz is not near the resonance, it will not be passed, and **the output will be less than the input.***


f) You connect your circuit to a source and find that the actual resonance occurs at  $f_0$  hertz. Assuming you now have measured values for C, R, and the resistance of the inductor, describe how you could use PSpice to get a closer estimate (than that found in part c) for the inductance of your inductor. Be specific. (4 points)

- 1) Wire the circuit in PSpice. Model the inductor as an inductance and a resistance.*
- 2) Set the values of the components -- R, C, and the resistance of the inductor -- to their measured values. Set the initial value of the inductor to the value calculated in part c.*
- 3) Place a voltage marker at the output, Vout.*
- 4) Set up an AC sweep from 1000 to 1Meg Hertz. (The exact minimum and maximum are not critical, but they must include the decade between 10,000 and 100,000.)*
- 5) Run the AC sweep. The resonant frequency is the location where the output peaks. (We know it will be the highest point because it is a band pass filter.)*
- 6) If the resonance in the plot is above  $f_0$ , then increase the value of L. If the resonance in the plot is below  $f_0$ , then decrease the value of L. Rerun the simulation and repeat the process until the resonance is exactly at the experimental resonant frequency,  $f_0$ .*
- 7) The value of L obtained in this manner will be a better estimate than the calculated value in part c.*

**ENGR4300 Test 1A**  
**Spring 2005**

Name \_\_\_\_\_  
 Section \_\_\_\_\_

 **3) Transfer Functions and Phasors (25 points)**



a) Find the transfer function for the above circuit. (2 points)

$$H(j\omega) = [R + j\omega L] / [(1/j\omega C) + R + j\omega L] = [j\omega RC - \omega^2 LC] / [1 + j\omega RC - \omega^2 LC]$$

b) Find the function to describe the behavior of the circuit at very low frequencies. Also determine the magnitude and phase of this circuit at very low frequencies. (3 points)

$$H_{LO}(j\omega) = [j\omega RC] / [1] = j\omega RC$$

$$|H_{LO}| = 0$$

$$\angle H_{LO} = \pi/2$$

c) Find the function to describe the behavior of the circuit at very high frequencies. Also determine the magnitude and phase of this circuit at very high frequencies. (3 points)

$$H_{HI}(j\omega) = [-\omega^2 LC] / [-\omega^2 LC] = 1$$

$$|H_{HI}| = 1$$

$$\angle H_{HI} = 0$$

**ENGR4300 Test 1A**  
**Spring 2005**

Name \_\_\_\_\_  
 Section \_\_\_\_\_

d) Find the function to describe the behavior of the circuit at the resonant frequency in terms of L, R, and C. Also determine the magnitude and phase of the circuit at the resonant frequency. (6 points)


$$H_0 = \frac{j \frac{1}{\sqrt{LC}} RC - \frac{1}{LC} LC}{1 + j \frac{1}{\sqrt{LC}} RC - \frac{1}{LC} LC} = \left( j \frac{1}{\sqrt{LC}} RC - 1 \right) \times \frac{1}{j} \frac{\sqrt{LC}}{RC}$$

$$H_0 = 1 + j \frac{\sqrt{LC}}{RC}$$

$$|H_0| = \sqrt{1 + \left( \frac{\sqrt{LC}}{RC} \right)^2} = \sqrt{1 + \frac{LC}{(RC)^2}}$$

$$\angle H_0 = \tan^{-1} \left( \frac{\sqrt{LC}}{RC} \right)$$

 e) Given the input signal pictured, find the values listed Include all units. (3 points)



amplitude voltage: **2V**

peak-to-peak voltage: **4V**

frequency (f): **1/5ms = 200 Hertz**

angular frequency ( $\omega$ ): **400 $\pi$  or 1257rad/sec**

RMS voltage: **2/ $\sqrt{2}$  = 1.41V**

phase shift ( $\phi$ ): **-2 $\pi$ (-1/4) =  $\pi/2$  or 1.57 rad**



**ENGR4300 Test 1A**  
**Spring 2005**

Name \_\_\_\_\_  
Section \_\_\_\_\_

f) Assuming the input signal pictured and given values  $C=0.1\mu\text{F}$ ,  $L=10\text{mH}$  and  $R=1\text{K}$ , find a complex expression for the transfer function of the circuit at the input frequency. Also, find the magnitude and phase of the function. (6 points).

$$H = \frac{j\omega RC - \omega^2 LC}{j\omega RC + 1 - \omega^2 LC} = \frac{j0.1257 - 0.001579}{j0.1257 + 1 - 0.001579} = \frac{j0.1257 - 0.001579}{j0.1257 + 0.9984}$$

$$|H| = \frac{\sqrt{0.1257^2 + 0.001579^2}}{\sqrt{0.1257^2 + 0.9984^2}} = 0.125$$

$$\angle H = \tan^{-1}\left(\frac{0.1257}{-0.001579}\right) - \tan^{-1}\left(\frac{0.1257}{0.9984}\right) = (\pi - 1.569) - 0.125 = +1.44 \text{ or } -4.84 \text{ rad}$$

(also acceptable  $\angle H = -1.569 - 0.125 = -1.69 \text{ rad or } +4.56 \text{ rad}$ )

(Technically, the first is correct. The phase shift must be positive and between 0 and  $+\pi/2$ . The best way to get it right is to use reference angles (like in trig) to get the correct magnitudes. Subtract the magnitudes and then, consider the sign based on what you know about the transfer function.)

g) For the input signal given in e), what will be the amplitude and phase of the output? (2 points)

$$A_{out} = A_{in} * |H| = 2 (0.125) = 0.25\text{V}$$

$$\phi_{out} = \phi_{in} + \angle H = 1.57 + 1.44 = +3.01 \text{ rad or } -3.27 \text{ rad}$$

(also acceptable  $\phi_{out} = 1.57 - 1.69 = -0.12 \text{ rad or } 6.16 \text{ rad}$ )

(Technically, the first is correct.)

(Different calculators calculate inverse tangent differently and they don't find tangent effectively in some quadrants. Since we never told them anything except that they needed to take the inverse tangent, we need to be flexible with the phase answers.)

# ENGR4300 Test 1A

## Spring 2005

Name \_\_\_\_\_

Section \_\_\_\_\_


ASIDE -- This is going into the Steady State handout for next semester. Since you did not get this information, we did not deduct for the phase calculation as long as it was substituted correctly into the equation.

### Calculating phases using the inverse tangent function

If the transfer function is given as a ratio of two complex numbers, then the phase is given by the difference between the phases of the numerator and denominator:

$$\text{if } H(j\omega) = \frac{x_1 + j y_1}{x_2 + j y_2} \text{ then } \angle H = \tan^{-1}\left(\frac{y_1}{x_1}\right) - \tan^{-1}\left(\frac{y_2}{x_2}\right)$$

If  $x_1, y_1, x_2$  and  $y_2$  are all positive, then the phase changes are all in the first quadrant, and the equation can be applied directly with a calculator. If one or more of them is negative, then one must worry about which quadrant the phase angle is in. The most reliable way to determine a phase change is to take the absolute value of the  $x$  and  $y$  coordinates of a complex number, calculate  $\tan^{-1}(|y/x|)$  to find the reference angle, use the signs of  $x$  and  $y$  to determine the quadrant, and find the phase based on the reference angle and the quadrant.

 

In the figure above,  $\beta$  is the reference angle for  $\theta$ . We want to find  $\theta$  -- the actual phase.  $\tan^{-1}(|y/x|)$  will always give us the reference angle  $\beta$ . We can find  $\theta$  based on the sign and the quadrant:

$x$	$y$	quadrant	$\theta$ (radians)	$\theta$ (degrees)
$x > 0$	$y > 0$	I	$\beta$	$\beta$
$x < 0$	$y > 0$	II	$\pi - \beta$	$180 - \beta$
$x < 0$	$y < 0$	III	$\beta - \pi$	$\beta - 180$
$x > 0$	$y < 0$	IV	$-\beta$	$-\beta$

Note that all angles in the above chart represent a phase shift between  $-\pi$  and  $+\pi$  radians (between  $-180$  and  $+180$  degrees).

# ENGR4300 Test 1A

## Spring 2005

Name \_\_\_\_\_  
Section \_\_\_\_\_

some examples:  $H(j\omega) = \frac{3 + j4}{4 + j3}$

numerator:  $\beta = \tan^{-1}(|4/3|) = 0.93$  ( $x > 0$ ,  $y > 0$ , Q1)

$\angle_{\text{num}} = 0.93$

denominator:  $\beta = \tan^{-1}(|3/4|) = 0.54$  ( $x > 0$ ,  $y > 0$ , Q1)

$\angle_{\text{den}} = 0.54$

$\angle H = \angle_{\text{num}} - \angle_{\text{den}} = 0.93 - 0.54 = 0.39 \text{ rad}$

$$H(j\omega) = \frac{-3 + j4}{4 - j3}$$

numerator:  $\beta = \tan^{-1}(|4/3|) = 0.93$  ( $x < 0$ ,  $y > 0$ , Q2)

$\angle_{\text{num}} = 3.14 - 0.93 = 2.21$

denominator:  $\beta = \tan^{-1}(|3/4|) = 0.54$  ( $x > 0$ ,  $y < 0$ , Q3)

$\angle_{\text{den}} = 0.54 - 3.14 = -2.60$

$\angle H = \angle_{\text{num}} - \angle_{\text{den}} = 2.21 - (-2.60) = 4.81 \text{ rad} = -1.47 \text{ rad}$

$$H(j\omega) = \frac{-3 - j4}{4 + j3}$$

numerator:  $\beta = \tan^{-1}(|4/3|) = 0.93$  ( $x < 0$ ,  $y < 0$ , Q4)

$\angle_{\text{num}} = -0.93$

denominator:  $\beta = \tan^{-1}(|3/4|) = 0.54$  ( $x > 0$ ,  $y > 0$ , Q1)

$\angle_{\text{den}} = 0.54$

$\angle H = \angle_{\text{num}} - \angle_{\text{den}} = -0.93 - 0.54 = -1.47 \text{ rad}$

And now back to the test.....


# ENGR4300 Test 1A

## Spring 2005

Name \_\_\_\_\_  
Section \_\_\_\_\_

### 4) Transformers (25 points)

 *Part A* In the transformer below, the value of the input inductance (the inductance of the primary winding of the transformer) is 1mH. You can assume that the coupling coefficient is 1 and that the resistance of R1 is negligible. Use the equations for an ideal transformer to determine the following:



$$L1 = 1\text{mH}, k=1, R1 = 5\Omega, R2 = 5\text{K}\Omega, V1 = 200\text{mV}$$

a) You would like the output voltage of the transformer to be 5 times that of the input voltage. What should the value of the constant,  $a$ , be? (1 point)

$$a = 5$$

b) Given the value for  $a$  you found in part a, what should you set the value of the output inductance (the inductance of the secondary winding of the transformer) to in order to obtain the desired voltage ratio? (3 points)

$$a = \sqrt{L2} / \sqrt{L1} \quad L2 = a^2 \times L1 = 25 \times 1\text{m} = 25\text{m}$$

c) For the case in part b, what will be the amplitude of the output *current*? (3 points)


$$a = V2/V1 \quad 5 = V2/200\text{m} \quad V2 = 1000\text{mV} \quad V = IR \quad 1\text{V} = I(5\text{K}) \quad I = 0.2\text{mA}$$

d) What is the input impedance,  $Z_{in}$ , of this transformer under the conditions given? (3 points)

$$Z = R2/a^2 = 5\text{K}/25 = 200\Omega$$

*Part B* Applying an input signal to your transformer.

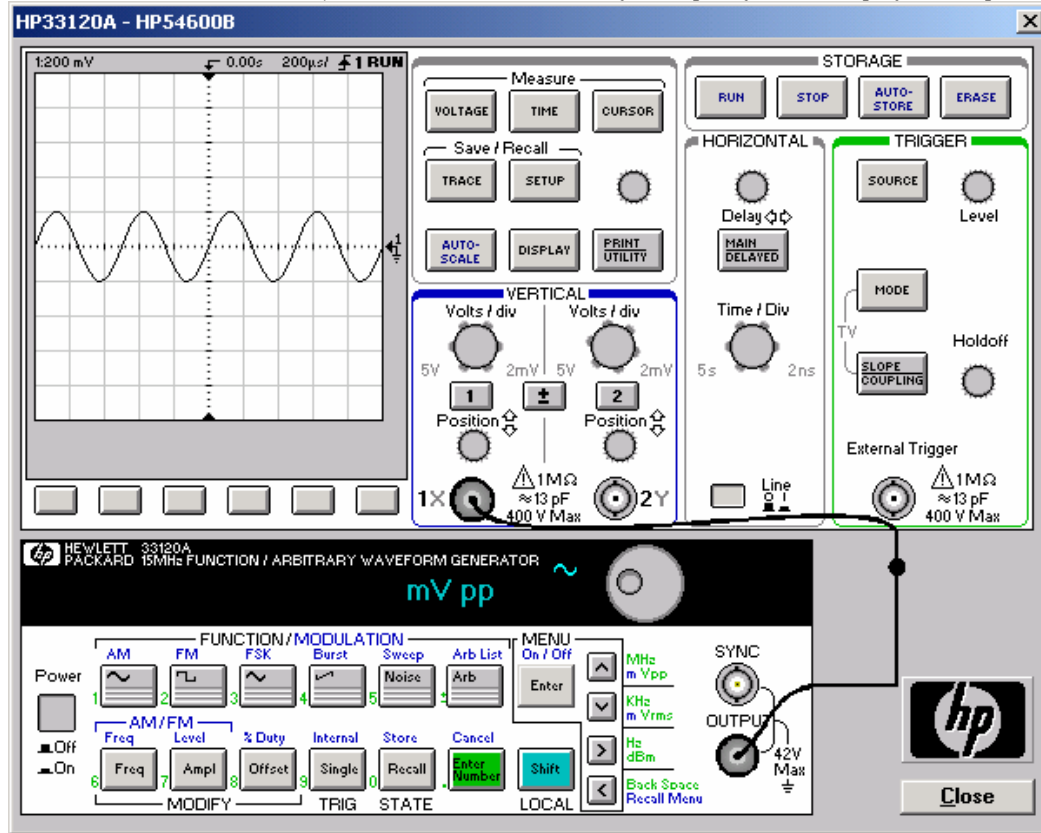1:200mV      0.00s 200μs/ 1 RUN    (The text at left is copied from the top of the scope display)



a) Describe how you would set the function generator and manually adjust the scope to get the signal shown above. Assume that the scope is connected directly to the function generator as shown. Give specific details. (4 points)

- 1) Push the Freq button on the function generator. Set it to  $(1/500\mu)=2\text{K}$  Hertz.
- 2) Push the Ampl button on the function generator. Set it so that the mV pp is equal to 200mV (This is  $1/2$  the desired peak-to-peak voltage.)
- 3) Set the Volts/div knob on the voltage scale is 200 mV.
- 4) Set the Time/Div knob so that the time scale is 200μs/.

b) Describe two ways that you could verify that the output signal has the correct peak-to-peak amplitude voltage using the scope. (2 points)

- 1) You can use the vertical scale on the scope display. The peak-to-peak voltage of the trace goes from -200mV to 200mV. So the peak-to-peak voltage is 400mV.
- 2) You can push the VOLTAGE button and the Vp-p soft key. The peak-to-peak voltage will be displayed underneath the scope display.

# ENGR4300 Test 1A


## Spring 2005

Name \_\_\_\_\_  
Section \_\_\_\_\_

c) As you are setting up the input signal, you notice that the function generator and the scope display a different value for peak-to-peak voltage. Which is correct, the function generator or the scope? Why? (3 points)

*The scope is correct. The function generator assumes that there is a 50 ohm impedance attached to it. Therefore, it displays  $\frac{1}{2}$  of what it is actually putting out. The scope has an impedance much larger than 50 ohms (1Meg). This discrepancy causes the display on the function generator to be incorrect.*

 d) Once you have set up the correct input to the circuit, you attach the transformer circuit and observe the output. Based on the ideal behavior of a transformer, sketch the expected output voltage on the scope screen below. (3 points)



e) When you observe the output on the scope, the amplitude of the output relative to the input is less than expected. How could you change the input signal to force the transformer to act more like an ideal transformer? (3 points)

***Increase the frequency of the input signal.***