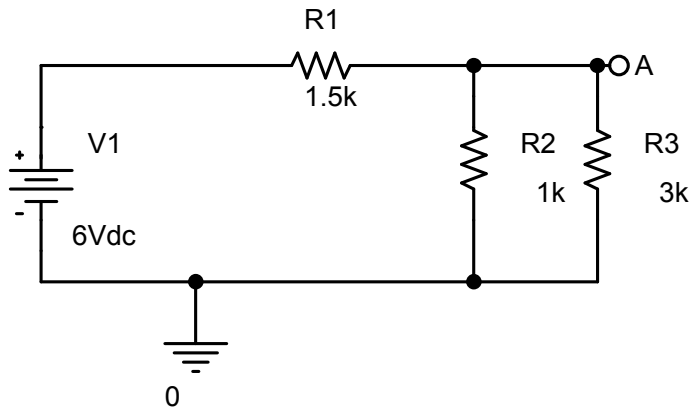


Question 1 – Resistive Circuits (25 points) (Test B)



Part 1: Voltages and currents.

1a) What is the voltage at point A in the figure above. (4 pt)


$$R_{23} = (1k \cdot 3k) / (1k + 3k) = 0.75k\Omega \quad V_A = 6V(0.75k) / (0.75k + 1.5k) = 2V$$

$$V_A = 2V$$

1b) What is the current through R2 ? (3 pt)

$$V_{R2} = V_A = 2V \quad I_{R2} = 2V / 1k = 2mA$$

$$I_{R2} = 2mA$$

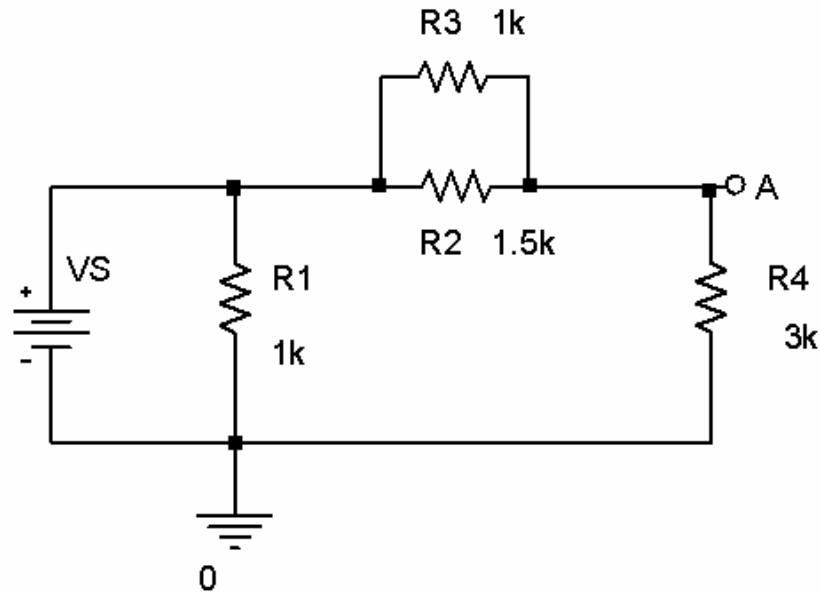

Question 1, Part 2: Equivalent circuits:

2a) What is the total resistance seen by the source V_S in the figure above?(6 pt)

$$R_{23} = 1k * 1.5k / (1k + 1.5k) = 0.6k$$

$$R_{234} = 0.6k + 3k = 3.6k$$

$$R_t = 1k * 3.6k / (1k + 3.6k) = 0.782k$$

$$\mathbf{R_{total} = 782\Omega}$$

2b) If $V_S = 5V$, what is the current out of this source? (2 pt)

$$I = 5V / 782\Omega = 6.4mA \quad \mathbf{I = 6.4mA}$$

2c) If $V_S = 5V$, what is the voltage at point A in this circuit? (3 pt)

$$V_A = 5(3k) / (0.6k + 3k) = 4.17V \quad \mathbf{V_A = 4.167V}$$

2d) If $V_S = 5V$, what is the current through R_2 ? (3 pt)

$$V_{R2} = 5V - 4.167V = 0.833V \quad I_{R2} = 0.833V / 1.5k = 0.56mA \quad \mathbf{I_{R2} = 0.56mA}$$

Question 1, Part 3: color code

3a) Resistors are found to have the color bands listed below. For each state the resistance. (4 pt)


Yellow-Violet-Orange *47k Ω* _____

Brown-Red-Brown *120 Ω* _____

3b) Extra credit: If a resistor has color bands of Yellow-Violet-Yellow-Silver, what is the significance of the Silver band? (1 point)


xtra: +/- 10% tolerance

Question 2 – Filters (15 points) (Test B)

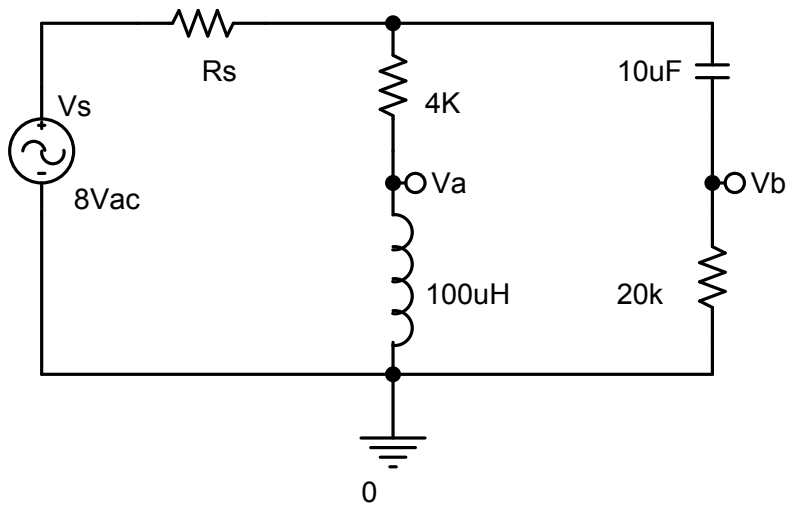

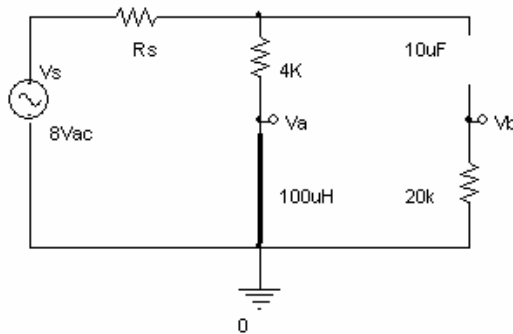Part 1: Filters, Using $R_s=0\Omega$


1a) Let $R_s=0\Omega$ Redraw the circuit above for very low frequencies. Label points Va and Vb on your diagram. (3 pt)



1b) Let $R_s=0\Omega$ What is Va at very low frequencies? (2 pt)

$V_a = 0V$

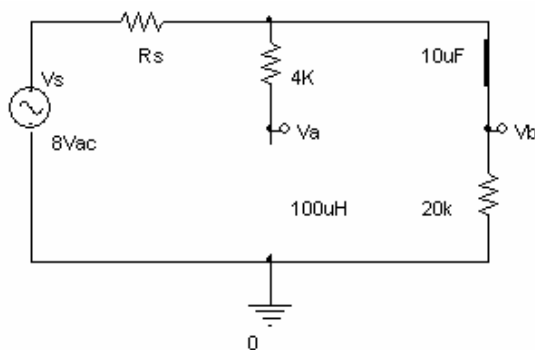1c) Let $R_s=0\Omega$ Redraw the circuit above for very high frequencies. Label points Va and Vb on your diagram. (3 pt)



1d) Let $R_s=0\Omega$ What is V_a at very high frequencies? (2 pt)

$$\text{Since } R_s=0\Omega, V_a=8V$$

1e) Let $R_s=0\Omega$ If V_a is considered the output, what type of filter is this? (1 point)

High Pass Filter

Part 2: Filters using $R_s=10k\Omega$


2a) Let $R_s=10k\Omega$ Referring to your picture in part 1a, what is V_b at very low frequencies? (2 pt)

$$V_b = 0V$$

2b) Let $R_s=10k\Omega$ Referring to your picture in part 1c, what is V_b at very high frequencies? (2 pt)

$$V_b = 8(20k)/(10k+20k) = 5.33V \quad V_b=5.33V$$

Question 3 – Transfer Functions (20 points) (Test B)

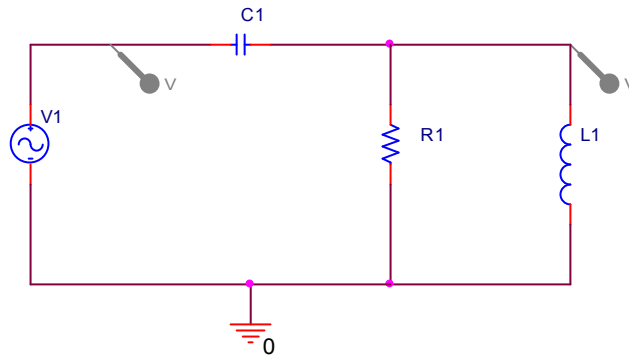

Part 1: Transfer Functions

1a) What is the transfer function for the circuit? You must simplify. (6 pt)

$$Z_{out} = \frac{j\omega L1 \cdot R1}{j\omega L1 + R1} \quad H(j\omega) = \frac{Z_{out}}{Z_{in}} = \frac{\frac{j\omega L1 \cdot R1}{j\omega L1 + R1}}{\frac{1}{j\omega C1} + \frac{j\omega L1 \cdot R1}{j\omega L1 + R1}}$$

$$H(j\omega) = \frac{(j\omega R1L1)(j\omega C1)}{(j\omega L1 + R1) + (j\omega R1L1)(j\omega C1)}$$

$$H(j\omega) = \frac{-\omega^2 R1L1C1}{j\omega L1 + R1 - \omega^2 R1L1C1}$$

1b) What are the simplified transfer function, the magnitude, and the phase of the circuit at low frequencies? (4 pt)

$$H_{LO}(j\omega) = \frac{-\omega^2 R1L1C1}{R1} = -\omega^2 L1C1$$

$$|H_{LO}| = 0 \quad \angle H_{LO} = \pi$$


(We know phase is positive because of the graph.)

1c) What are the simplified transfer function, the magnitude, and the phase of the circuit at high frequencies? (4 pt)

$$H_{HI}(j\omega) = \frac{-\omega^2 R_1 L_1 C_1}{-\omega^2 R_1 L_1 C_1} = 1$$

$$|H_{HI}| = 1 \quad \angle H_{HI} = 0$$

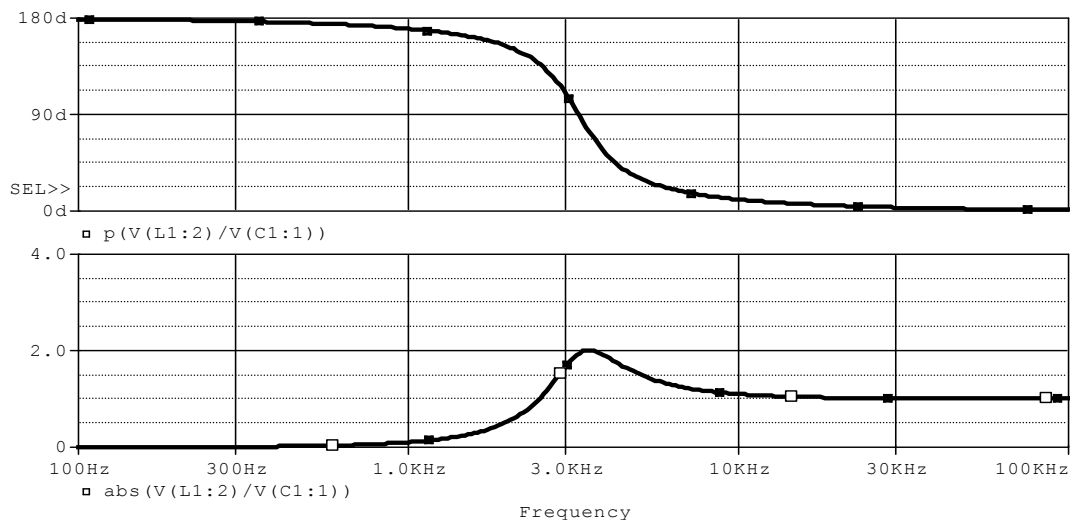Part 2: The phase and magnitude of the transfer function for this circuit are pictured below:



2a) Use the graph to determine the resonant frequency of the circuit (in Hertz). Show your work. (2 pt)

from plot: $f = 10^{3.55} = 3550\text{Hz}$

(Answers will vary. Student must use log scale to get reasonable answer for credit.)

2b) If the following input signal is applied to the circuit, what will be the amplitude and phase (in radians) of the output signal? [Please include all units.] (4 pt)

$$v_{in}(t) = A_{in} \sin(\omega t + \phi_{in}) = 500\text{mV} \sin(18850t + 2.09 \text{ rad})$$

$\omega = 18850 \text{ rad/sec } f = 3000\text{Hz}$

from plot of $|H|$: $|H|$ at 3000Hz is 1.7

$A_{out} = A_{in} \times (1.7) = (500\text{mV})(1.7) = 850\text{mV}$

from plot of $\angle H$: $\angle H$ at 3000Hz = 110 degrees = 1.92 rad


$\phi_{out} = \phi_{in} + 1.92 = 2.09 + 1.92 = 4.01 \text{ rad or } -2.27 \text{ rad (both ok)}$

(Answers will vary depending upon value read from plot.)


$A_{out} = 850\text{mV}$

$\phi_{out} = -2.27 \text{ rad}$

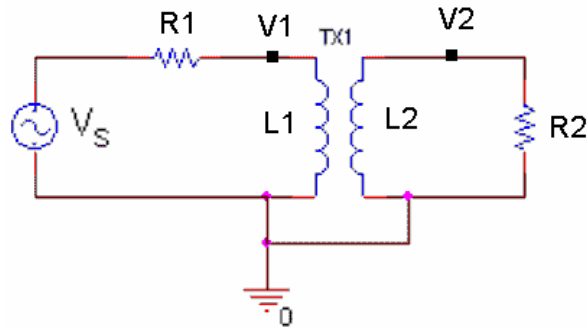Question 4 – Transformers and Inductors (20 points)



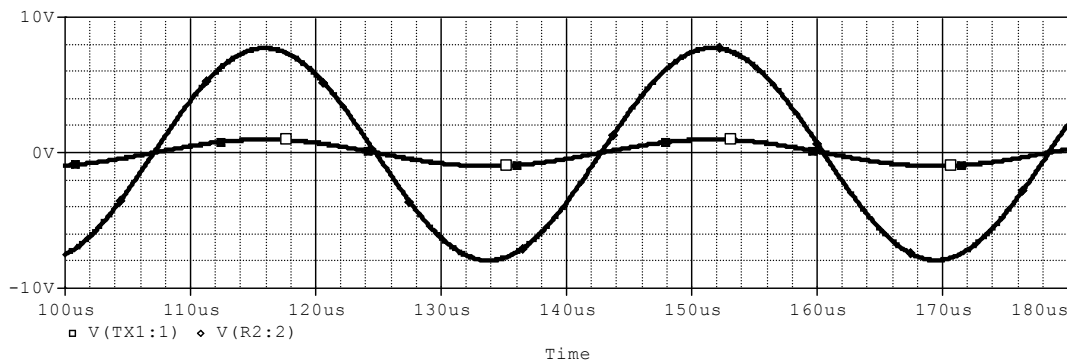You are given the above transformer. You can assume the transformer is ideal, the coupling coefficient is 1, and the resistance of R1 is negligible compared to the resistance of R2. The plot below shows the input to the transformer at V1 and the output at V2. The output is the signal with the larger amplitude.



1) Give the values of the following for the input signal (smaller amplitude) shown. Give units for each. (7 pt)

Amplitude (A): $1V$

Frequency (f): $f=1/(143us-107us)$
 $f=27.8K Hz$

Angular frequency (ω):
 $\omega=2\pi f=175K rad/sec$

Phase (ϕ) relative to 100us:
 $\phi=-\omega t_0 = -(175k)(7\mu) = -1.22 rad$

rms voltage (V_{rms}):
 $V_{rms} = 1/\sqrt{2} = 0.707 V$

peak to peak voltage (V_{p-p}):
 $V_{p-p} = 2V$

DC offset voltage (V_{DC}):
 $V_{DC} = 0V$

(These answers will vary depending upon the numbers they get from the plot..)

2) What is the most likely turns ratio of the transformer? (Express your answer as a whole number of turns.) (2 pt)

$Turns\ ratio = 1V:8V = 1:8 \quad (a=8)$

3) If the primary inductor, L1, has an inductance of 1mH, what must the inductance of the secondary inductor, L2, be? (2 pt)

$$a = \sqrt{\frac{L2}{L1}} \quad 8 = \sqrt{\frac{x}{1m}} \quad L2 = 64mH$$

4) If the impedance of the input inductor L1 is 250Ω, what is the value of R2? (3 pt)

$$Z_{in} = \frac{R2}{a^2} \quad 250 = \frac{R2}{8^2} \quad R2 = 16k\Omega$$

5) Write an expression in the form, $i(t) = I_{max} \sin(\omega t + \phi)$, that represents the current through the load resistor, R2, as a function of time. [Assume again that the phase is defined relative to 100us.] (3 pt)

$$i(t) = I_{max} \sin(\omega t + \phi) \quad V=IR \quad 8V = I*(16K) \quad I=0.5mA \quad \omega=175K \text{ rad/s} \quad \phi = -1.22 \text{ rad}$$

$$i(t) = 0.5mA \sin(175K t - 1.22 \text{ rad})$$

(These answers will vary. If they substitute ϕ , ω , and the amplitude of the voltage correctly from part 1), then this is correct.)

6) Assume the inductor, L1, is a long, thin coil with a length of 8.5 cm and 38 turns. If the radius of the transformer core is 0.5 cm, what material is the core most likely made of? [Assume there is no mutual inductance.] (3 pt)


Some values for μ

- Air 1.257×10^{-6} H/m
- Ferrite U M33 9.42×10^{-4} H/m
- Nickel 7.54×10^{-4} H/m
- Iron 6.28×10^{-3} H/m
- Ferrite T38 1.26×10^{-2} H/m
- Silicon GO steel 5.03×10^{-2} H/m
- Supermalloy 1.26 H/m

$$L = \frac{\mu N^2 \pi r_c^2}{d} \quad 1m = \frac{\mu(38)^2 \pi(0.005)^2}{(0.085)} \quad \mu = 7.49 \text{ EE-4 H/m} \quad \text{Material} = \text{nickel}$$

Question 5 – PSpice, Instrumentation and Components (20 points) Quiz B

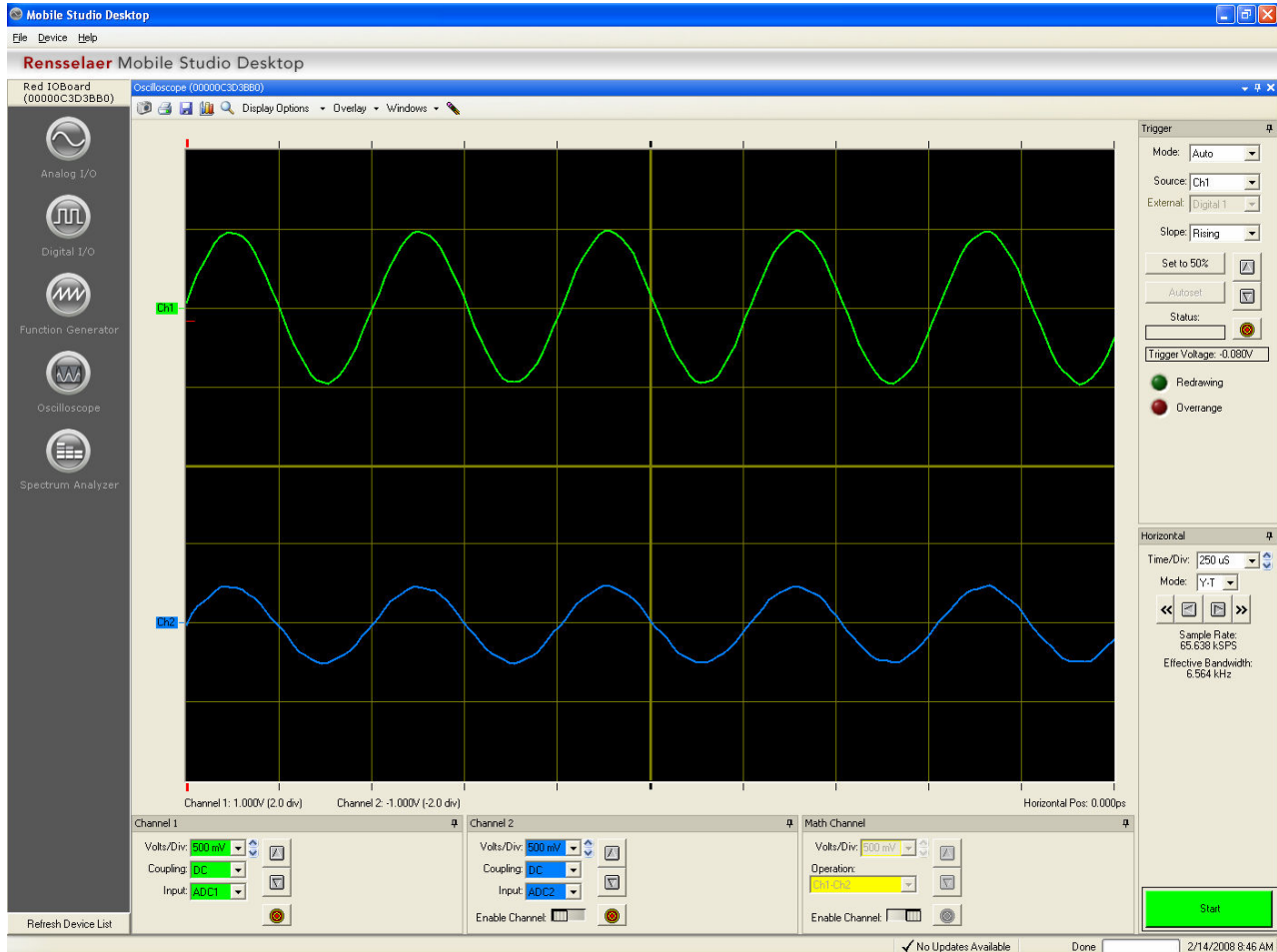Part A: Given the scope setup shown below (w/ Channel 1 at 500mV/division, Channel 2 at 500mV/division and the timebase at 250µsec/div):



a) What are the peak-peak amplitudes and the frequency of the two signals shown (5 pt)?

V_{p-p} of the top signal (channel 1): $1.0V$


V_{p-p} of the bottom signal (channel 2): $500mV$

Frequency: $Freq = 1/500\mu s = 2k Hz$


DC offset of top signal (channel 1): $0V$

DC offset of bottom signal (channel 2): $0V$

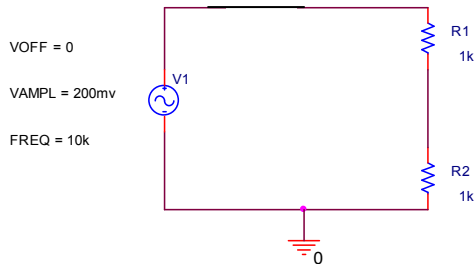b) The two scope traces were produced using a function generator and a circuit built with up to four 1K ohm resistors. Draw a schematic for a circuit that would produce the input (ch1) and output (ch2) signals shown on the previous page. You can use all or some of the resistors. The schematic does not need to show the scope connections. (3 pt)



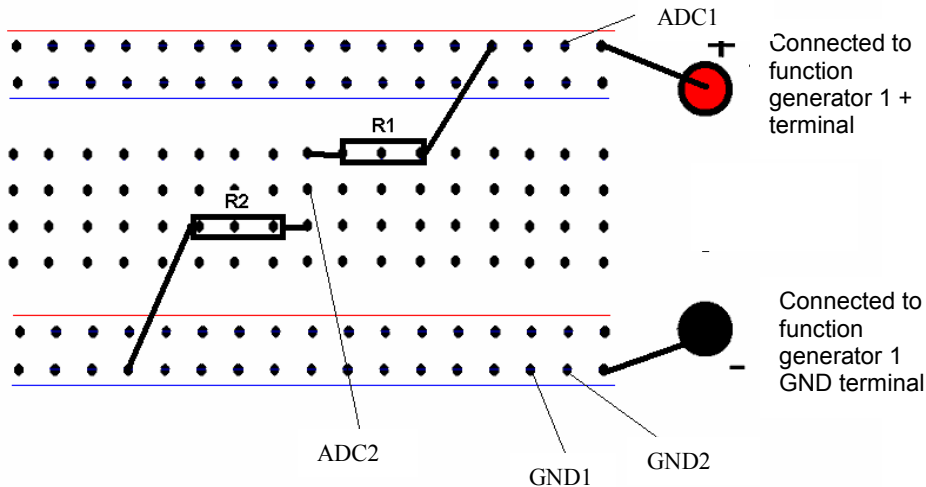c) Show how you would wire the circuit in part b on the protoboard below. Assume the function generator has already been connected to the board using banana plugs. (2 pt)



d) On the figure above, indicate the location you would place the scope probes to get the signals shown in the scope picture for part A. Name the leads as follows: ADC1 (ADC 1 +), GND1 (ADC 1 -/GND), ADC2 (ADC 2 +), and GND2 (ADC 2 -/GND). (2 pt)


e) In the circuit you created, is the input impedance of the oscilloscope (in comparison to the value of the resistors) a significant influence on the circuit? Why or why not? (2 pt)

The input impedance of the oscilloscope is of relatively little significance. It is on the order of three orders of magnitude larger than the resistors, which means that they have around 1000 times more influence on the circuit. If I make a voltage divider it becomes clearer:


With oscilloscope: $R = (1k)(1M)/(1k+1M) = 0.999k$

Without oscilloscope: $R = 1k$

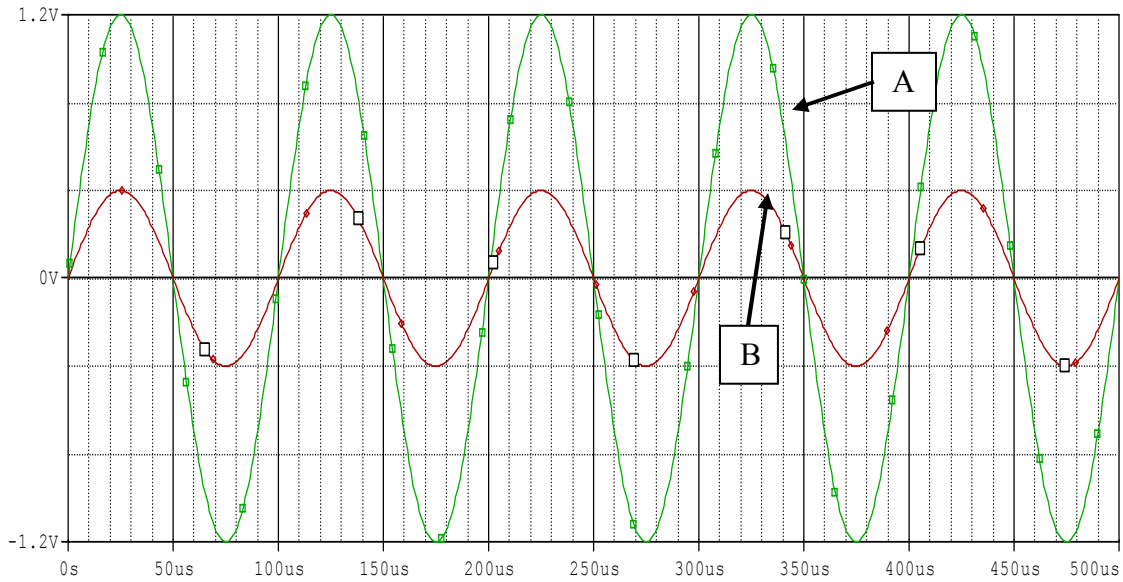Part B: You have created a circuit in PSpice to produce the following output.



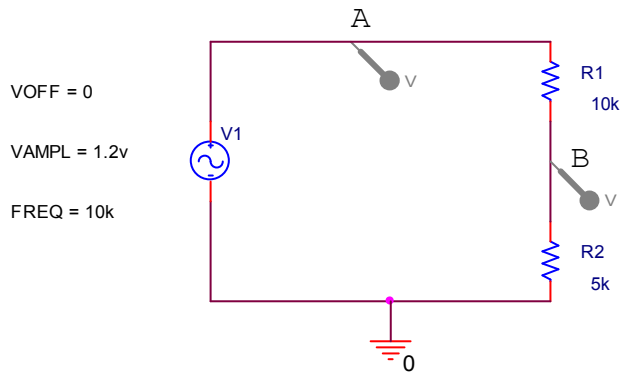a) Here is the circuit you used to create the signals. Fill in the boxes with the missing information. (4 pt)



b) Indicate on the schematic above where you would place the voltage probes to produce signal A and signal B. Indicate which is which. (Do not use differential probes.) (2 pt)