

ENGR4300
Spring 2006
Test 2 version A

Name _____

Sola

Section _____

Question 1 (25 points) _____

Question 2 (15 points) _____

Question 3 (20 points) _____

Question 4 (20 points) _____


Question 5 (20 points) _____

Total (100 points): _____

On all questions: SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS. No credit will be given for numbers that appear without justification.



50/4


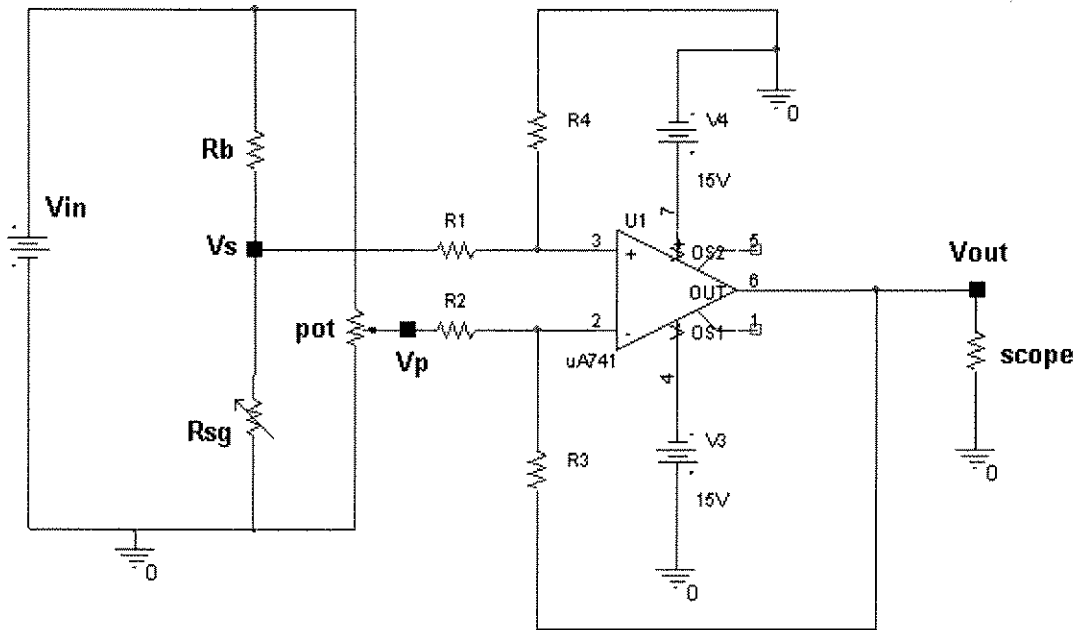
Question 1 – Bridges and Damped Sinusoids (25 points)



Above is figure of an amplified strain gauge bridge similar to the one you are using for project 2. The circuit has the following values: $V_{in} = 5V$, $R_b = 1K$ ohms, $R_1 = 2K$ ohms, $R_2 = 2K$ ohms, $R_3 = 10k$ ohms, $R_4 = 10k$ ohms, and the pot is a 2k pot.

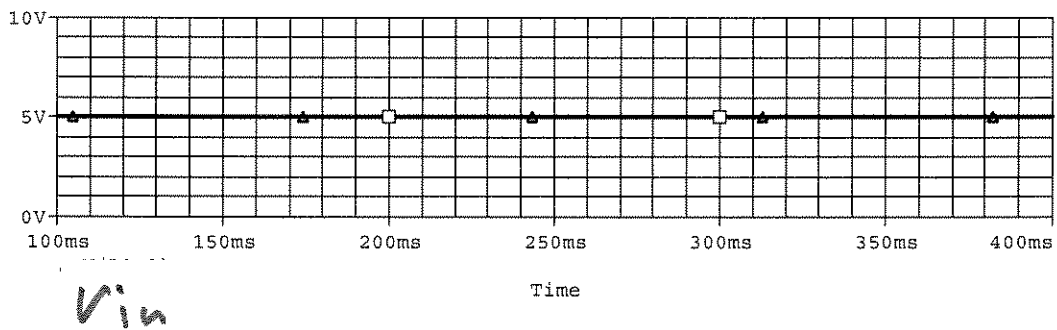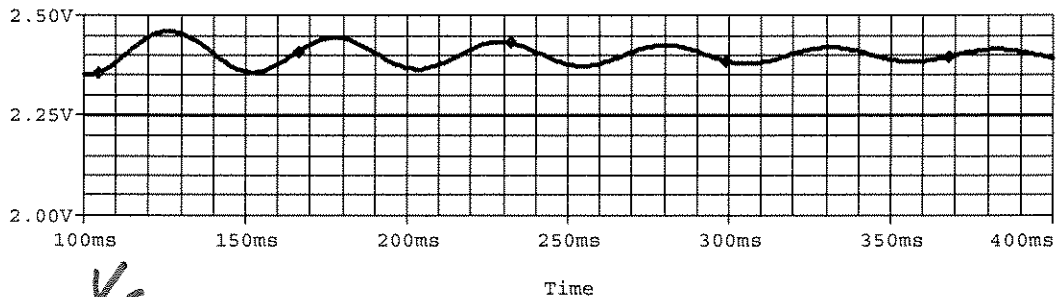a) Assuming the bridge is ideal and that it has been properly balanced, which of these four plots is correct for each of the following four voltages on the figure: V_{in} , V_s , V_p , and V_{out} . (Indicate the signal in the box below the plot). (8 points)



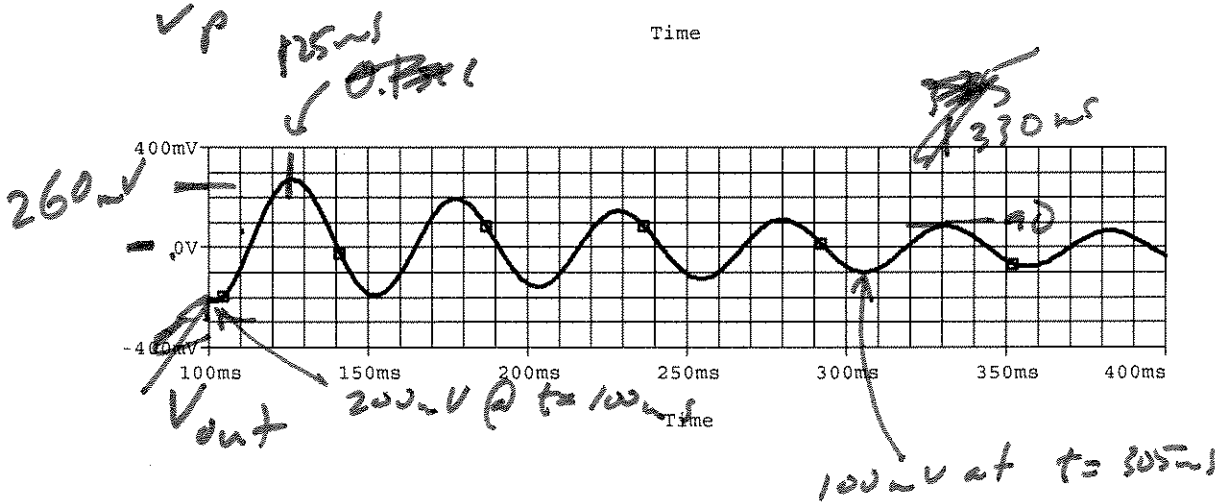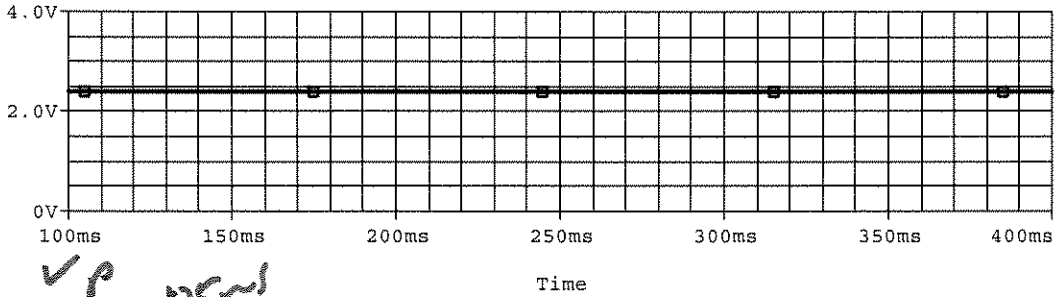

b) What is the resonant frequency of the output signal in Hertz? (3 points)

$$T = (305ms - 100ms) / 4 \Rightarrow 19.5Hz$$

~~or 22Hz~~

out c
ok at
the data
points are.

c) What is the damping constant of the output signal? (4 points)

Positive Peaks
260mV at 125ms, 90mV at 330ms

$$\alpha = \frac{\ln(V(t_1)/V(t_2))}{t_2 - t_1}$$

$$\alpha = \frac{\ln(260/90)}{330 - 125} = 5.2/sec$$

Neg. peaks 200mV at $t_1 = 100ms$, 100mV @ $t_2 = 305ms$

$$\alpha = \frac{\ln(V(t_1)/V(t_2))}{(t_2 - t_1)} = 3.4/sec$$

d) Write an equation for V_{out} in terms of V_s and V_p . Do not substitute numerical values for the resistors. (2 points)

$$V_{out} = \frac{R_4}{R_1} (V_s - V_p) \text{ or } V_{out} = \frac{R_3}{R_2} (V_s - V_p)$$

e) If R_{pot} is the total resistance of the potentiometer, R_{top} is the resistance between the center of the pot and the source voltage, R_{bottom} is the resistance between the center of the pot and ground, R_{sg} is the resistance of the strain gauge, and R_b is as shown in the figure, which of the following are true statements? Assume the bridge is balanced and in its rest position. (4 points) (Circle T or F for each statement.)

$$\frac{R_b}{R_b + R_{sg}} = \frac{R_{top}}{R_{pot}} \quad \text{T} \quad \text{F}$$

$$\frac{R_b}{R_{sg}} = \frac{R_{top}}{R_{bottom}} \quad \text{T} \quad \text{F}$$

$$R_{top} + R_{bottom} = R_{pot} \quad \text{T} \quad \text{F}$$

$$\frac{R_{top}}{R_b} = \frac{R_{pot} - R_{top}}{R_{sg}} \quad \text{T} \quad \text{F}$$

f) Starting with the equation from part d, derive an equation for V_{out} in terms of V_{in} for this circuit. Use the resistor naming conventions we used in part e (R_{pot} , R_{top} , R_{bottom} , R_{sg} , and R_b) and the other resistors in the circuit (R_1 , R_2 , R_3 , and R_4). You will not need all of these resistors in the answer. You cannot assume the bridge is balanced. You cannot substitute numerical values for the resistors. You cannot express your answer in terms of V_s and V_p . (4 points)

version A, Prob 1 soln.

Answers:

a) $V_s, V_{in}, V_p, V_{out}$

b) $T = (305m - 100m) / 4 = 51.25m \text{ s} \Rightarrow f = 1 / 51.25m \text{ s} = 19.5 \text{ Hz}$

c) $v_0, t_0 = 200mv, 0.1s \quad v_1, t_1 = 100mv, 0.305s$

$100m = 200m e^{EE(-\alpha * 0.205)} \quad \alpha = 3.4/s$

d) $V_{out} = \frac{R_4}{R_1} (V_s - V_p)$ (R_4 could also be R_3 , R_1 could also be R_2)

e) TTTT

f)

$$V_{out} = \frac{R_4}{R_1} (V_s - V_p) \quad V_s = \frac{R_{sg}}{R_{sg} + R_b} V_{in} \quad V_p = \frac{R_{bottom}}{R_{pot}} V_{in}$$

$$V_{out} = \frac{R_4}{R_1} \left(\frac{R_{sg}}{R_{sg} + R_b} V_{in} - \frac{R_{bottom}}{R_{pot}} V_{in} \right)$$

$$V_{out} = \frac{R_4}{R_1} \left(\frac{R_{sg}}{R_{sg} + R_b} - \frac{R_{bottom}}{R_{pot}} \right) V_{in}$$

(R_4 could be R_3 , R_1 could be R_4 , R_{pot} could be $R_{top} + R_{bottom}$)
 (The above amount of simplification is sufficient.)

Alternate answers:

a) ~~$V_{out}, V_s, V_{in}, V_p$~~

b) ~~$T = (510m - 100m) / 9 = 45.56m \text{ s} \Rightarrow f = 1 / 410m \text{ s} = 22.0 \text{ Hz}$~~

c) ~~$v_0, t_0 = 300mv, 0.1s \quad v_1, t_1 = 200mv, 0.305s$~~

~~$200m = 300m e^{EE(-\alpha * 0.46)} \quad \alpha = 0.9/s$~~


d) ~~of f) same~~

~~please note:~~
 I don't agree with this answer

For part a, it does matter which peaks they use.
 For positive peaks
 $260mv @ 125\mu s, 90mv @ 330\mu s$
 $\alpha = \frac{\ln [V(t_1) / V(t_2)]}{t_2 - t_1} \approx 5.2 / sec$

Answers A:

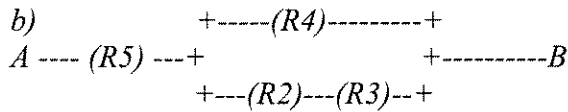
a) $V_{th} = V_{AB} = V1 * (R4) / (R2 + R4 + R3) = 6V * (2k) / (500 + 2k + 1k) = 3.43V$



$R_{23} = 500 + 1000 = 1500$ $R_{234} = (1500 * 2000) / (1500 + 2000) = 857 \text{ ohms}$

$R_{th} = 3000 + 857 = 3857 \text{ ohms}$

c)

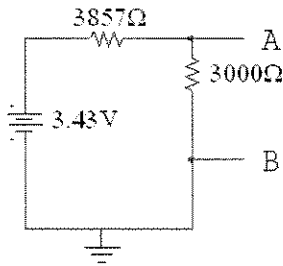


d) $3.43 = I(3857 + 3000)$ $I = 0.5mA$

*Prob 2
Soln.*

Answers B:

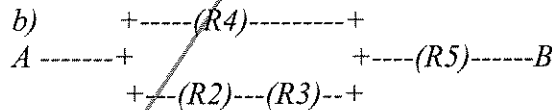
a) $V_{th} = V_{AB} = V1 * (R4) / (R2 + R4 + R3) = 8V * (1k) / (400 + 1k + 2k) = 2.35V$




$R_{23} = 400 + 2000 = 2400$ $R_{234} = (2400 * 1000) / (2400 + 1000) = 706 \text{ ohms}$

$R_{th} = 706 + 2000 = 2706 \text{ ohms}$

c)

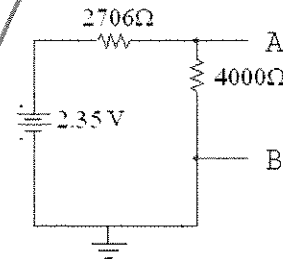

d) $2.35 = I(2706 + 4000)$ $I = 0.35mA$

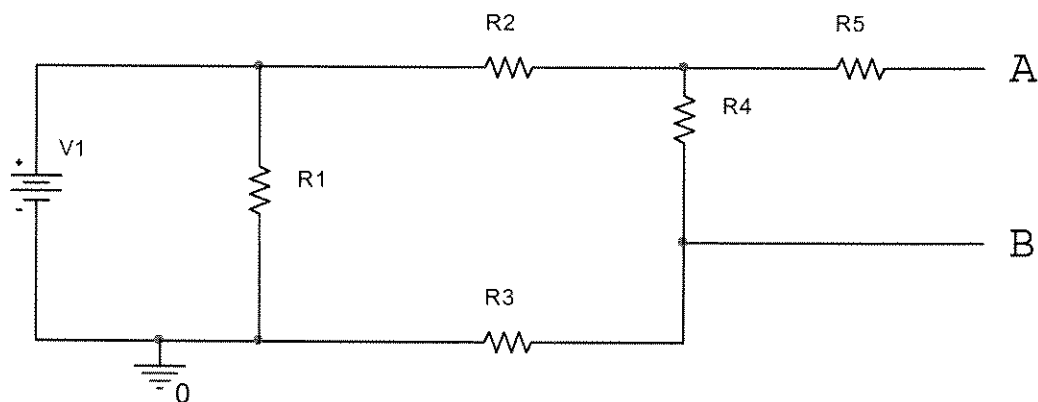Question 2 – Thevenin Equivalents (15 points)

$V1=6V$, $R1=2k$ ohms, $R2=500$ ohms, $R3=1k$ ohms, $R4=2k$ ohms, $R5=3k$ ohms

- a) Find the Thevenin equivalent voltage with respect to A and B for the circuit shown above. (5 points)


- b) Find the Thevenin equivalent resistance with respect to A and B for the circuit shown above. (5 points)

- c) Draw the Thevenin equivalent circuit with a load resistor of 3K between points A and B. (3 points)

- d) What is the current through the 3K load resistor in the circuit you drew in part c? (2 points)

Problem 3

Given the following circuit:

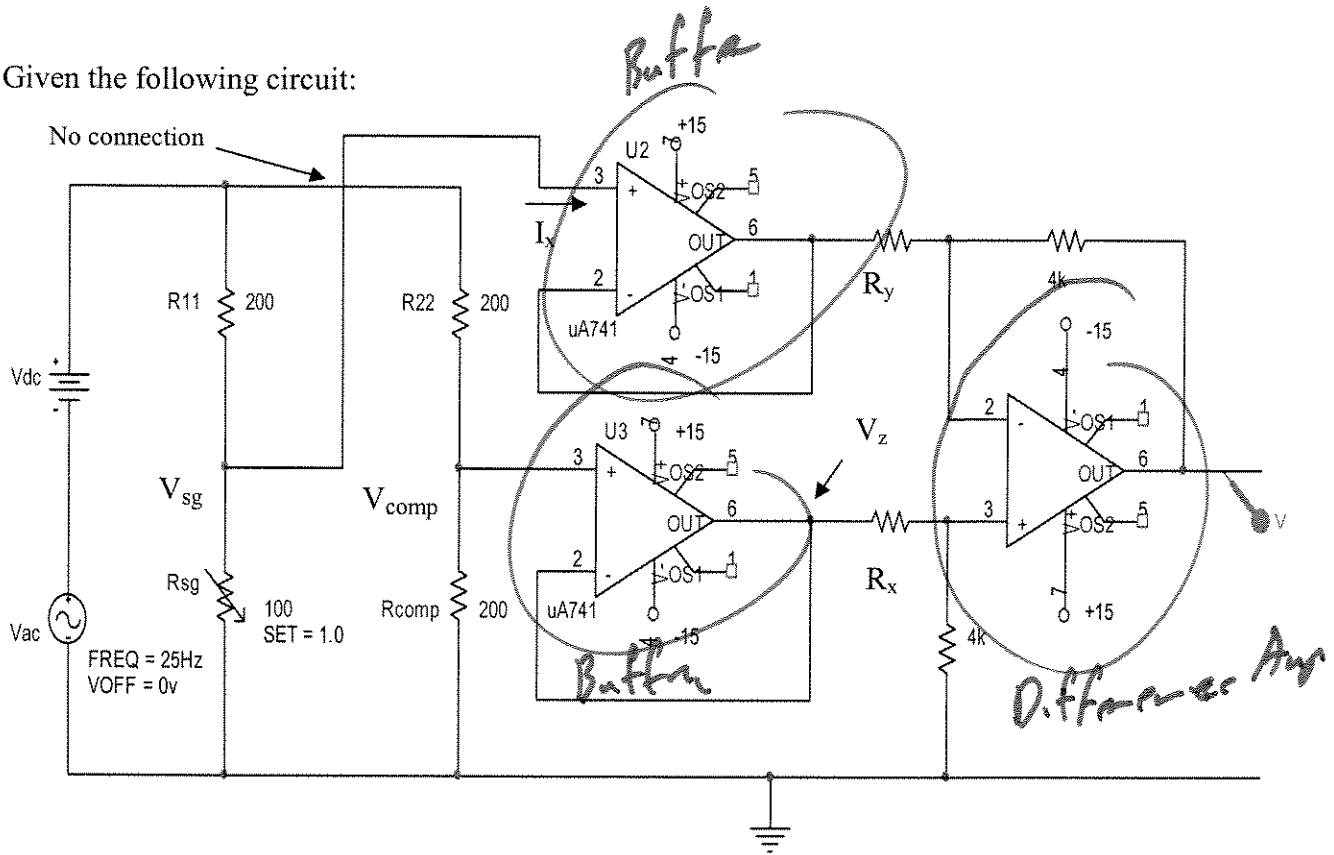

Note: Rsg is variable resistor to model a strain gauge. The SET=1.0 simple means that the nominal resistance is the full 100Ω. Use 100Ω for you analysis.

a) What is the voltage V_{sg} in the circuit above if the amplitude $V_{ac}=6$ and $V_{dc} = 0v$?

2pts V_{sg} is an AC voltage with a magnitude of 3V
 an 0 dc } allowed answers 3V, 3Vac, magnitude of 3V

b) What is the voltage V_{comp} in the circuit above if the amplitude $V_{ac}=6$ and $V_{dc} = 0v$?

2pts 3Vac

c) With $V_{dc} = 6v$ and the amplitude of $V_{ac} = 0v$, what is I_x ?

2pts 0mA

d) What is the voltage V_z if $V_{dc} = 6v$ and the amplitude of $V_{ac} = 0v$?


2pts 3Vdc

e) Circle and label the op amp configurations on the schematic above, choosing from the following types:

1. Follower/Buffer
2. Inverting Amp
3. Non-inverting Amp
4. Differentiator
5. Integrator
6. Adding (Mixing) Amp
7. Difference (Differential) Amp

6 pts
2 each

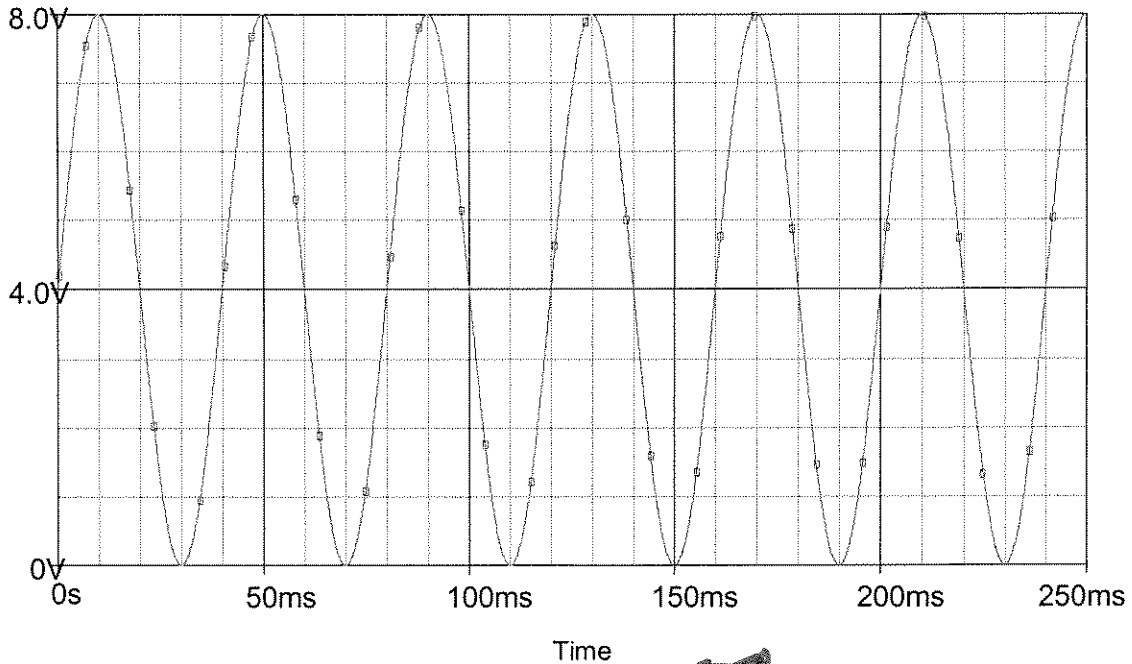
f) What values of R_x and R_y would you use to produce the following plot with $V_{dc} = 6v$ and the amplitude of $V_{ac} = 6v$, if the probe's output appeared as follows?



$R_x = R_y = 1k\Omega$
 $V_{SS} = \left(\frac{1}{3}\right)6V_{ac} + \left(\frac{1}{3}\right)6V_{DC} = 2V_{ac} + 2V_{DC}$
 $V_z = V_{comp} = \left(\frac{1}{2}\right)(6V_{ac}) + \left(\frac{1}{2}\right)(6V_{DC}) = 3V_{ac} + 3V_{DC}$
 $V = \frac{4k}{R_y} (V_z - V_{SS}) = \frac{4k}{R_y} (1V_{ac} + 1V_{DC}) = 4V_{ac} + 4V_{DC}$
 $\frac{4k}{R_y} = 4 \implies R_y = 1k$
 $R_x = R_y = 1k$

1 pt
1 pt
4 pt

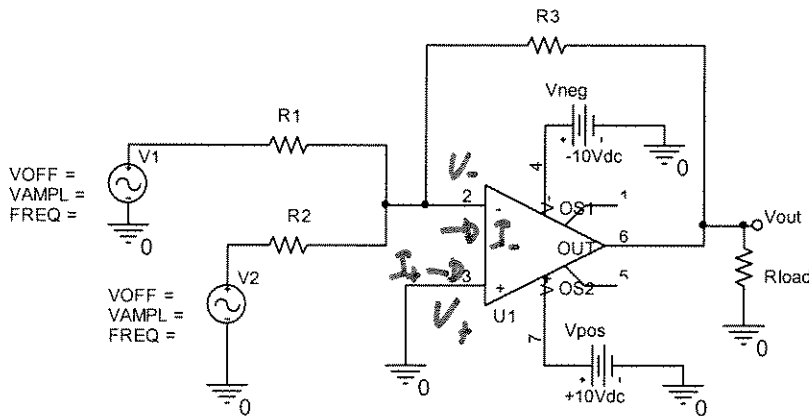Question 4 Op-Amp circuits (20 points) Assume the op-amp is ideal.



a) Above is a Capture schematic of an op-amp circuit that you should recognize. What type of circuit is it?

adder (2 pts)

b) We assume that the op-amp is ideal. What are the two “golden rules” that we then use to analyze the circuit? In some sections of the course this was referred to as the “virtual short model.” So an alternative wording of this question is: what are the characteristics of the virtual short op-amp model? (The answer is the same for either wording.)

$V_+ = V_-$, $I_- = 0$, $I_+ = 0$ (2 pts)

c) If $V1 = 0.8V$, $V2 = 0.5V$, $R1 = 5k\Omega$, $R2 = 5k\Omega$, and $R3 = 20k\Omega$, what is the value of V_{out} in Volts? Show your work.

$$V_{out} = -\frac{R_3}{R_1} V_1 - \frac{R_3}{R_2} V_2 = \left(-\frac{20}{5}\right)(0.8) + \left(-\frac{20}{5}\right)(0.5)$$

$$= -5.2 V$$

(3 pts)

d) Repeat the last question but with $R2$ replaced with a $2k\Omega$ resistor.


$$V_{out} = \left(-\frac{20}{5}\right)(0.8) - \left(\frac{20}{2}\right)(0.5)$$

$$= -3.2 - 5$$

$$= -8.2 V$$

(3 pts)

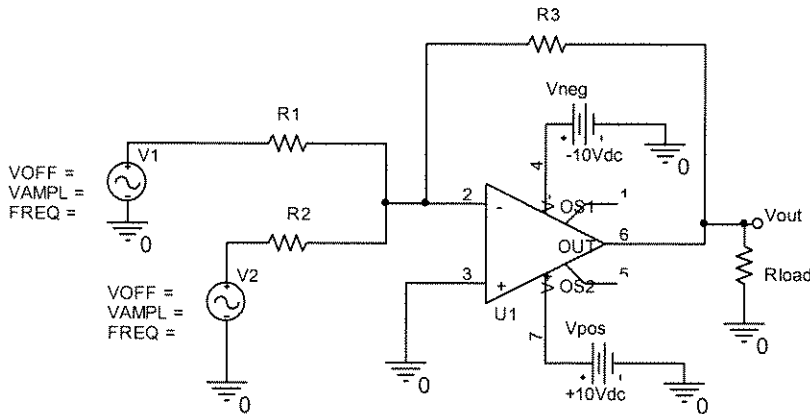This is the same circuit as on the previous page.



e) Write an expression for V_{out} in terms of V_1 , V_2 , R_1 , R_2 and R_f . 3

$$V_{out} = -\frac{R_3}{R_1} \cdot V_1 - \frac{R_3}{R_2} \cdot V_2$$

2 pt

f) Assume that V_{out} on this op-amp will saturate if it gets to within 1.5V of either power supply. If $V_1 = -1.0V$, $R_1 = 5k\Omega$, $R_2 = 2k\Omega$, and $R_3 = 20k\Omega$: what is the range of voltage for V_2 that will keep the op-amp out of saturation? Give your answer in volts with 2 significant digits. (Note that the resistors have the same values as those used in part 4 of this problem, but V_1 and V_2 may be different.) 3 pt

$$V_{out \max} = 8.5V \quad 2 \text{ pt}$$

$$\text{if } V_{out} = (-4)V_1 + (-10)(V_2)$$

$$\text{if } V_1 = -1V$$

$$V_{out} = 4 - 10 \cdot V_2$$

$$V_2(\max) = 1.25V$$

$$V_2(\min) = -0.45V$$

$$V_{out}(\max) = 8.5 = 4 - 10(V_2(\min))$$


$$V_2(\min) = \frac{4.5}{10} = 0.45V \quad 2 \text{ pt}$$

$$V_{out}(\min) = -8.5 = 4 - 10(V_2(\max))$$

$$V_2(\max) = \frac{12.5}{10} = 1.25 \quad 2 \text{ pt}$$

↓
2 pt
for correct
answer

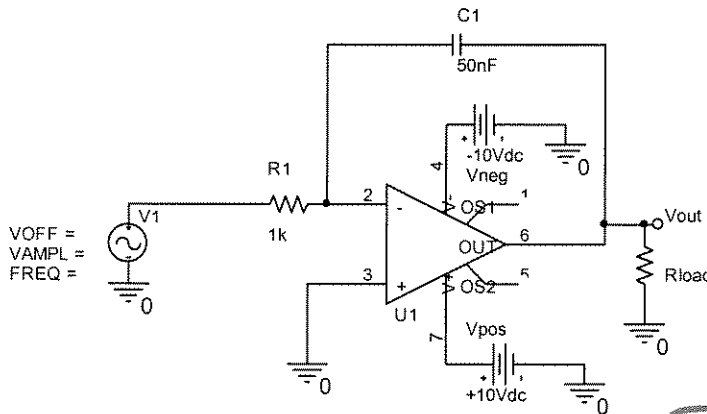Question 5 Op-Amp Integrators and Differentiators (20 points)




a) Above is a Capture schematic of an op-amp circuit that you should recognize. What type of circuit is it?

1pt
Integrator 1pt

b) For this part, plot the output signal for this circuit if the input is as shown below. Use the lower plot for your output. Assume that the output is at 0 volts at t=0.

7pt

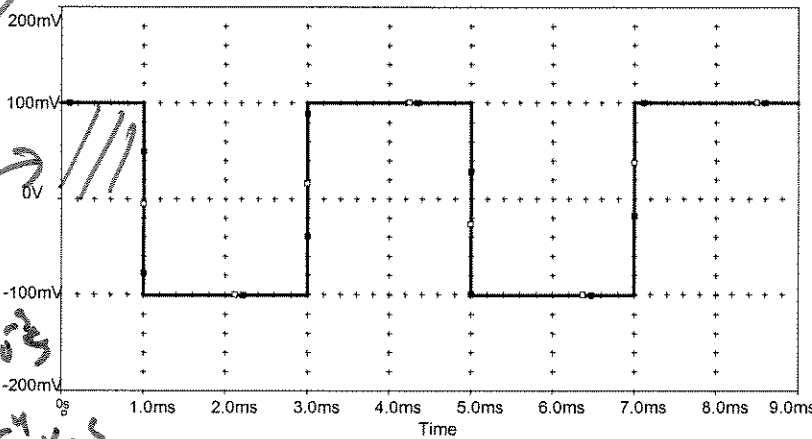


Input signal

at first 1pt
area till 1ms 3pt
area from 1-3ms 3pt

area
100mV · 10⁻³s
1ms = 10⁻³s
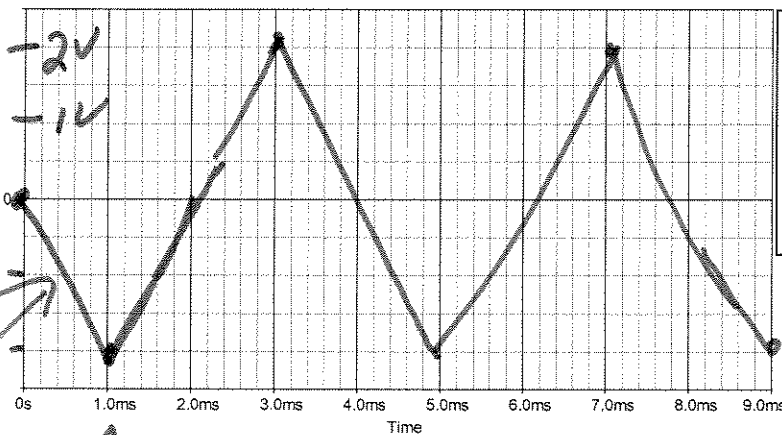
$$V_{out} = \frac{1}{RC} \int V_{in} dt$$




Draw output signal
 Label minimum and maximum voltages.
 Label the vertical axis.
 Assume $V_{out}=0$ at $t=0$.

1pt
 $\frac{1}{RC} = 2 \times 10^4$
2pt

1pt for neg
 $2 \times 10^4 \int_0^{1ms} 0.1V dt$
 $2V$

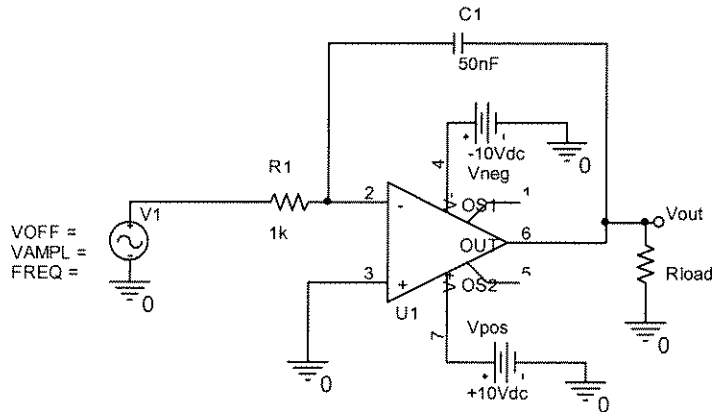10 of 12 *2pt* to get $V_{out} \min = -2$
 " " " " $V_{out} \max = +2$



(3pt) c) The circuit above is the same circuit as the one used for parts 1 and 2, but now assume that the input is sinusoidal and that we are interested in steady state response. What is $H(j\omega)$, the transfer function for this circuit? $H(j\omega) = \mathbf{Vout/V1}$. You must use the component values, don't leave the answer in terms of $R1$ or $C1$. Simplify your answer.


$$H(j\omega) = \frac{-1}{j\omega RC} = -\left(\frac{1}{j\omega}\right)(2 \times 10^4)$$

$$H(j\omega) = -\frac{2 \times 10^4}{j\omega}$$

$$\text{OR} = \frac{(j)(2 \times 10^4)}{\omega}$$

3pt

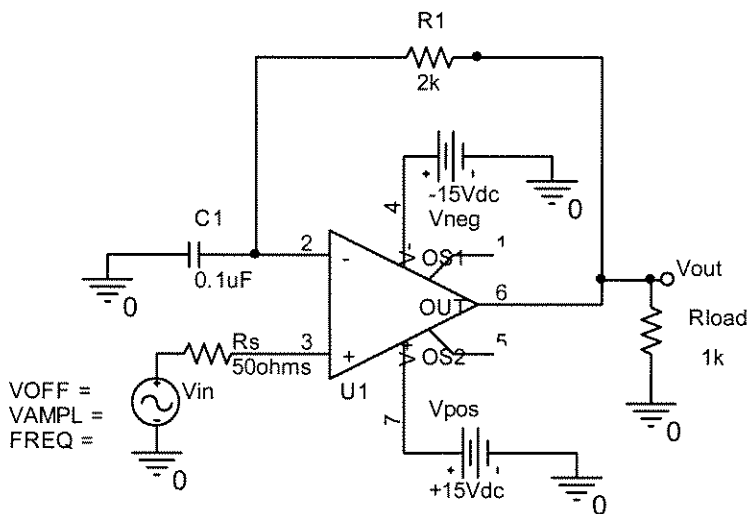The circuit below is used for the next two parts.



d) For this circuit, the input is sinusoidal. What is $H(j\omega)$, the transfer function for this circuit? $H(j\omega) = \mathbf{Vout/V1}$. You must use the component values, don't leave the answer in terms of $R1$ or $C1$. Simplify your answer. 5pts

4pt

$$H(j\omega) = \frac{Z_f}{Z_i} + 1 = \frac{R_1 + \frac{1}{j\omega C_1}}{1/j\omega C_1} = 1 + j\omega R_1 C_1$$

$R_1 = 2 \times 10^3, C_1 = 10^{-7}$ $R_1 C_1 = 2 \times 10^{-4}$

e) The circuit shown in part 4 was simulated with an AC sweep. At one frequency, the output was found to have a 45 degree phase shift relative to the input. Calculate that frequency in Hz, f_{45} . Now determine the effective gain at this frequency, $A_{45} = |Vout|/|Vin|$ at f_{45} . Show your work or method for partial credit. 5pts

$f_{45} = 796$ (Hz) or 800 Hz 3pt

$H(j\omega) = 1 + j\omega(2 \times 10^{-4})$
2pt

$A_{45} = \sqrt{2} = 1.4$
- (2pt)

OR arc tan = 45° \Rightarrow real part = imaginary part
 $\omega \cdot 2 \times 10^{-4} = 1$
 $\omega = 5000$ rad/sec
 $f = \frac{\omega}{2\pi} = 796$ Hz