

Quiz 1



**TRANSMISSION LINES**

Name \_\_\_\_\_

Section \_\_\_\_\_

**Short Answer Questions**

1. (15 Pts) \_\_\_\_\_

2. (15 Pts) \_\_\_\_\_

3. (5 Pts) \_\_\_\_\_

4. (5 Pts) \_\_\_\_\_

**Regular Questions**

5. (20 Pts) \_\_\_\_\_

6. (20 Pts) \_\_\_\_\_


7. (20 Pts) \_\_\_\_\_

**Total**

\_\_\_\_\_

**Notes:**

- 1. Please read over all questions before you begin your work. There may be some information in a later question that helps you with an earlier question.
- 2. For short answer questions, you may add some comments to justify your answer.
- 3. Make sure your calculator is set to perform trigonometric functions in radians & not degrees & use 4 significant digits.

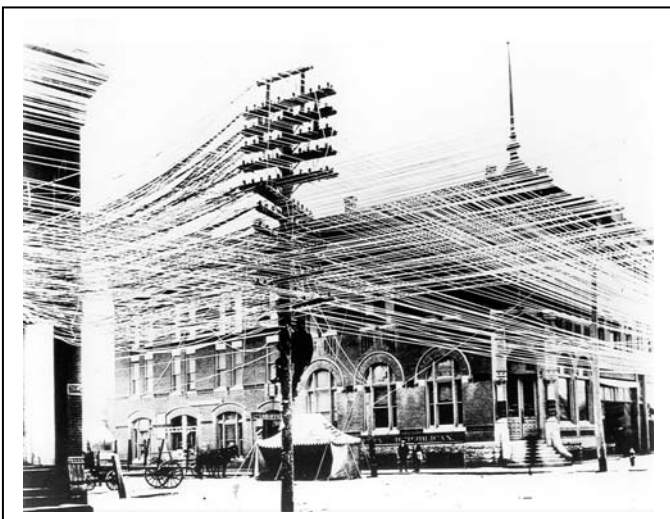

Quiz 1

**MULTIPLE CHOICE AND SHORT ANSWER QUESTIONS**


**1. Input Impedance of Transmission Lines (15 points)**



Assume a sinusoidal source is connected to a transmission line, as shown.

- a. (3 pts) The transmission line is of infinite length and it has characteristic impedance  $Z_o$ . What is the input impedance of the transmission line?  $Z_{IN} =$
  
- b. (3 pts) What is the input impedance of a transmission line of length  $\lambda/4$ , terminated by an open circuit?  $Z_{IN} =$
  
- c. (3 pts) A transmission line has length  $\lambda/2$ , characteristic impedance  $Z_o = 50\Omega$  and load  $Z_L = 75\Omega + j50\Omega$ . What is the input impedance?  $Z_{IN} =$
  
- d. (3 pts) A transmission line has characteristic impedance  $Z_o = 50\Omega$  and the load is short-circuited. What is the minimum length the line should have (in terms of wavelength) so that the input impedance is  $Z_{IN} = j50\Omega$ ? What minimum line length for  $Z_{IN} = -j50\Omega$ ?

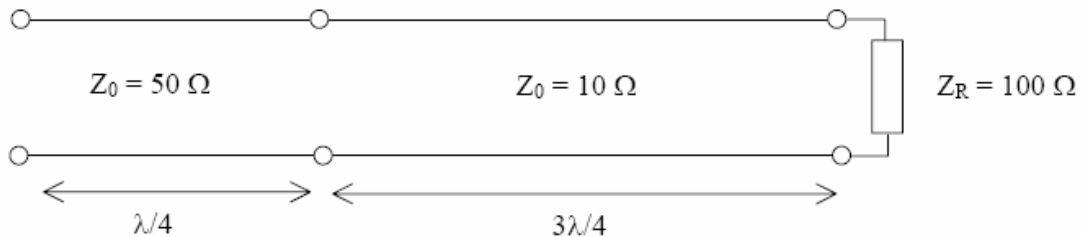e. (3 pts) What is the input impedance of the network below?



$Z_{IN} =$

Quiz 1


**2. Waves on Transmission Lines (15 points)** *(Includes an extra credit question.)*

For all of the following questions, assume that a lossless transmission line has a characteristic impedance of  $Z_o = 50\Omega$ .

a. (3 pts) The load reflection coefficient for a given transmission line is  $\Gamma_L = 0.5$ . What is the load impedance?  $Z_L =$

b. (3 pts Extra Credit) Same question as a, but for  $\Gamma_L = j0.5$ .  $Z_L =$

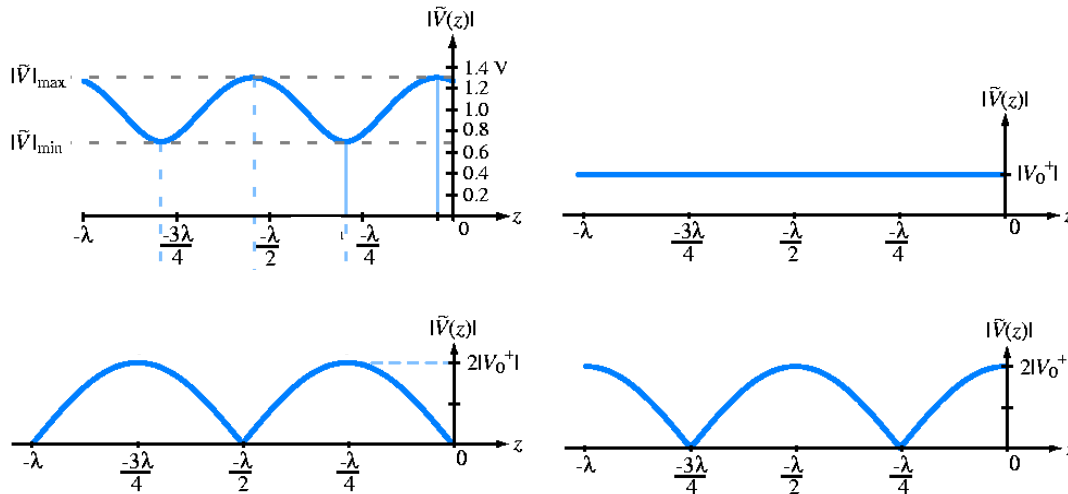c. (3 pts) A transmission line has a matched load ( $Z_L = Z_o$ ). What does the Standing Wave Pattern look like? Circle the correct diagram below.




d. (4 pts) The voltage wave propagating on a transmission line is given in real space-time form as  $v(z,t) = 10\cos(8\pi 10^7 t - 0.4\pi z) - 6\cos(8\pi 10^7 t + 0.4\pi z)$ . Write this voltage expression in phasor form.

e. (2 pts) Is the wave of part d a traveling wave or a standing wave?

## Quiz 1

**3 Lossy Transmission Line (5 points)**


A sinusoidal voltage wave is propagating on a low loss transmission line. The voltage as a function of position appears as shown below. From this plot, determine the damping coefficient.  $\alpha =$

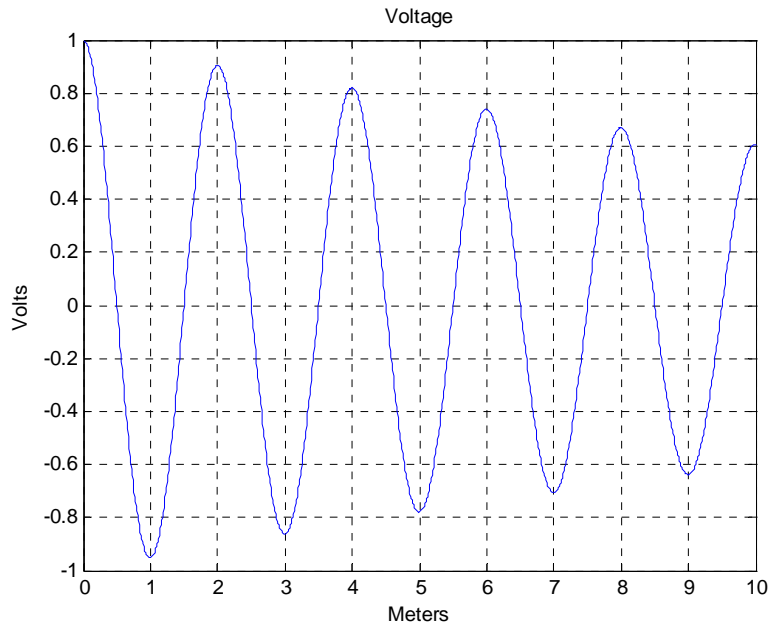**4. Freebies (5 points)**


Circle the photos of all who were educated as electrical engineers (all are engineers).



Rowan Atkinson

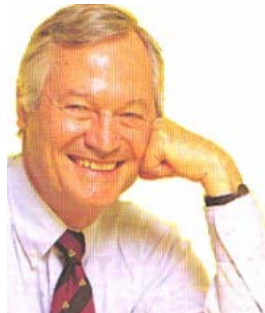

Roger Corman

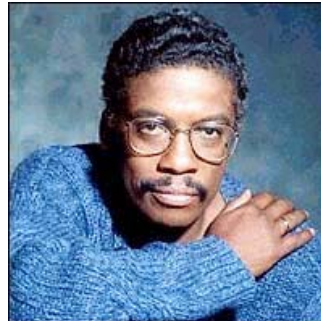

Herbie Hancock



Allen Dumont

What is each known for?

## Quiz 1

**REGULAR QUESTIONS****5. Sinusoidal Voltages on a Lossless Transmission Line (20 points)**

A lossless transmission line has a characteristic impedance of  $Z_o = 50$  Ohms. The propagation velocity on the line is  $u = 1.5 \times 10^8$  m/s. The load impedance  $Z_L$  is purely resistive.



a. (3 pts) Consider the voltage Standing Wave Pattern shown on the following page. What is the Voltage Standing Wave Ratio?  $VSWR =$

b. (2 pts) Is the load impedance larger or smaller than the characteristic impedance  $Z_o$ ?


c. (3 pts) What is the load reflection coefficient?  $\Gamma_L =$

d. (3 pts) What is the value of the load impedance?  $Z_L =$

e. (3 pts) What is the amplitude of the injected voltage wave?  $V^+ =$

f. (2 pts) What percentage of power is reflected by the load?

## Quiz 1

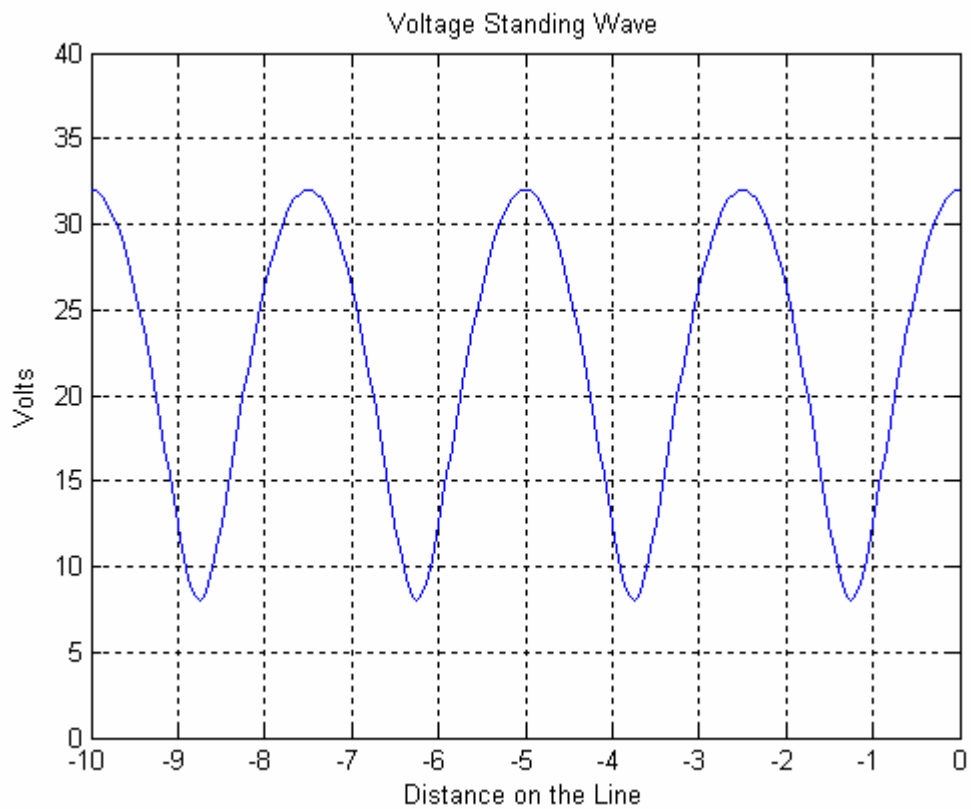


g. (2 pts) What is the wavelength?  $\lambda =$

h. (2 pts) What is the frequency of the source?  $f =$

## Quiz 1

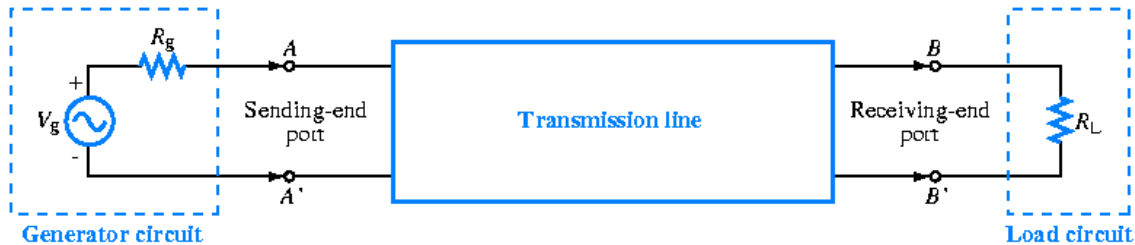
**6. Sinusoidal Transmission Line (20 pts)**

A long lossless transmission line is driven by a standard source with  $R_g = 50 \text{ Ohms}$ , but has no load (open circuit). The propagation velocity on the line is  $u = 1.6 \times 10^8 \text{ m/s}$  and the characteristic impedance of the line is  $Z_o = 100 \text{ Ohms}$ .



- What is the reflection coefficient  $\Gamma_L$  at the load? (2 pts)
- What is the standing wave ratio  $SWR$ ? (2 pts)
- For a frequency  $f = 100 \times 10^3 \text{ Hz}$ , what is the propagation constant  $\beta$ ? (2 pts)
- What is the wavelength  $\lambda$ ? (2 pts)
- Will the voltage be a maximum or a minimum at the load? (2 pts)
- If the voltage at the load is a maximum, what is the distance from the load to the first minimum? If the voltage at the load is a minimum, what is the distance from the load to the first maximum? (Answer only one of these questions.) Express this length both in meters and in wavelengths. *Distance =*
- As luck would have it, this transmission line is made up of 10 lines connected in series. Thus, it is possible to monitor the voltage at the input and output and 9 evenly spaced internal locations. A PSpice simulation of the line and the voltages observed are shown on the following page. From the information given, determine the length of the entire line. Express this length both in meters and in wavelengths. *Length =*

Quiz 1

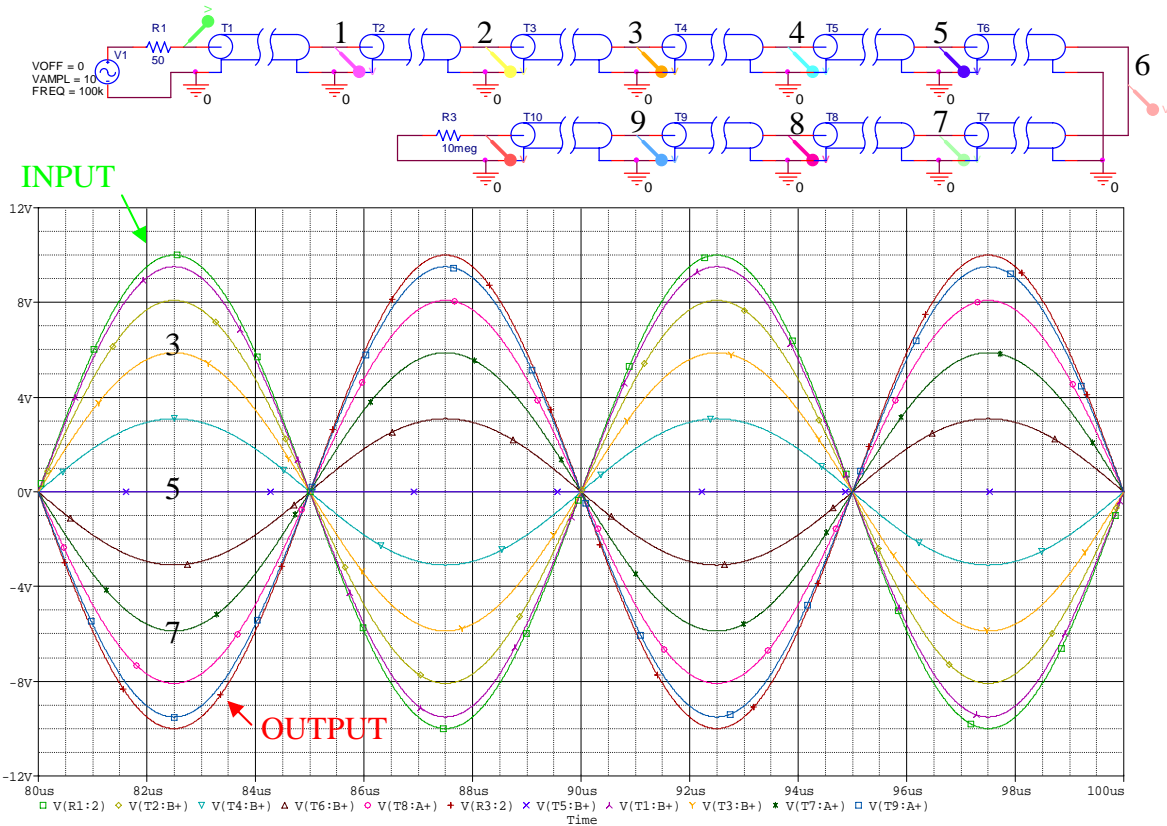


Note: In the first half cycle, the top sinusoid is the input and the bottom is the output. The nine internal points sequence from the top to the bottom. Only 3, 5, and 7 are shown to avoid clutter in the diagram.

- h. What voltages will be observed at each location if a matched load is connected to the line?




Quiz 1

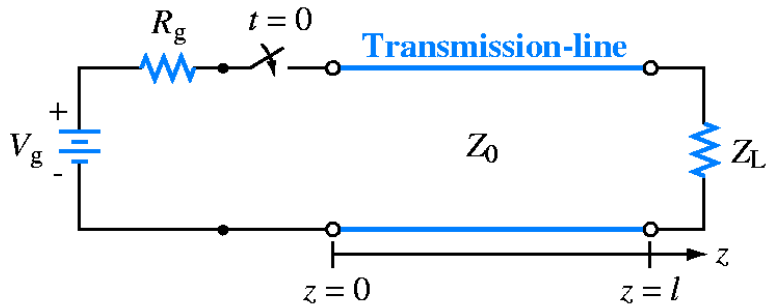7. Transients on Transmission Lines (20 points)



A 9V battery with a 10 Ohm internal impedance is connected to a 50 Ohm transmission line with a 10 Ohm load. The length of the line is 10 meters and the propagation speed is  $2.5 \times 10^8$  m/s.

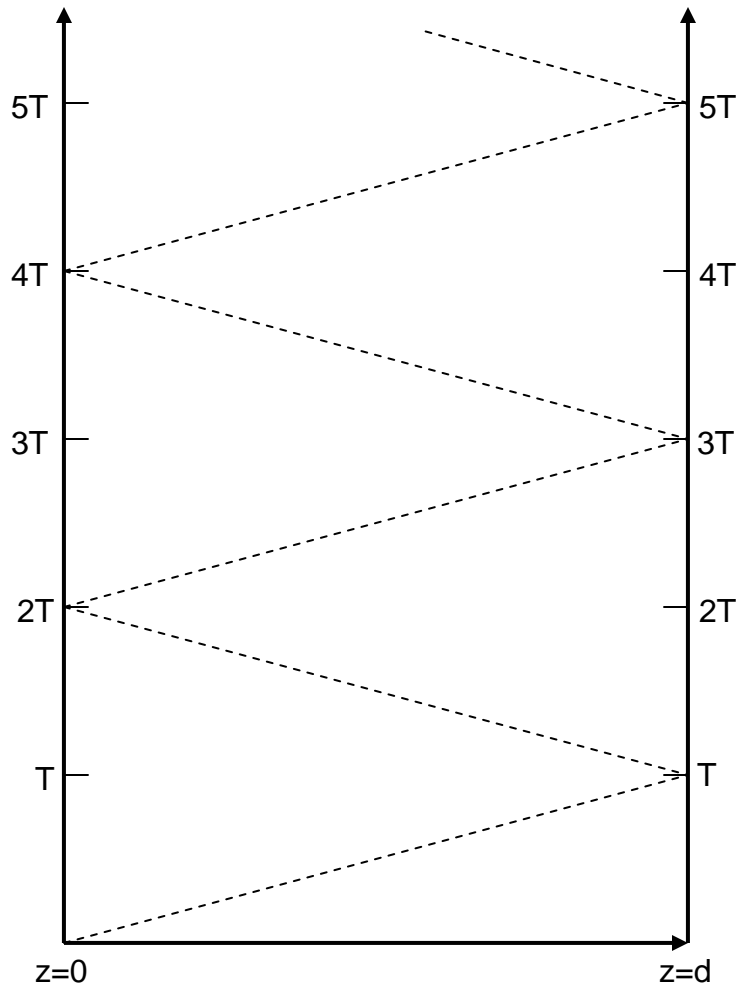- a. Generate the bounce diagram for this configuration. (6 pts)



- b. Determine and plot the voltage observed at the load as a function of time. Indicate the value the voltage will eventually reach if we wait long enough (time goes to infinity). (6 pts)

