

Transmission Lines Steady State

Phasor Notation

$$V(z, t) = \text{Re}(\hat{V}(z)e^{j\omega t})$$

$$I(z, t) = \text{Re}(\hat{I}(z)e^{j\omega t})$$

Voltage Wave

$$\hat{V}(z) = \hat{V}_m^+ e^{-\hat{g}z} + \hat{V}_m^- e^{+\hat{g}z} = \hat{V}_m^+ e^{-\hat{g}z} (1 + \hat{\Gamma}(z)) \text{ for lossy lines}$$

$$\hat{V}(z) = \hat{V}_m^+ e^{-jbz} + \hat{V}_m^- e^{+jbz} = \hat{V}_m^+ e^{-jbz} (1 + \hat{\Gamma}(z)) \text{ for lossless lines}$$

Current Wave

$$\hat{I}(z) = \frac{\hat{V}_m^+}{Z_o} e^{-\hat{g}z} - \frac{\hat{V}_m^-}{Z_o} \hat{V}_m^- e^{+\hat{g}z} = \frac{\hat{V}_m^+}{Z_o} e^{-\hat{g}z} (1 - \hat{\Gamma}(z)) \text{ for lossy lines}$$

$$\hat{I}(z) = \frac{\hat{V}_m^+}{Z_o} e^{-jbz} - \frac{\hat{V}_m^-}{Z_o} \hat{V}_m^- e^{+jbz} = \frac{\hat{V}_m^+}{Z_o} e^{-jbz} (1 - \hat{\Gamma}(z)) \text{ for lossless lines}$$

Propagation Constant

$$\hat{g} = \mathbf{a} + j\mathbf{b} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

Characteristic Impedance

$$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Phase Velocity

$$v_{ph} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{me}} \text{ for lossless or low loss lines}$$

Total Wave Impedance

$$\hat{Z}(z) = \frac{\hat{V}(z)}{\hat{I}(z)} = Z_o \frac{1 + \hat{\Gamma}(z)}{1 - \hat{\Gamma}(z)}$$

Reflection Coefficient

$$\hat{\Gamma}(z) = \frac{\hat{V}_m^-}{\hat{V}_m^+} e^{2\hat{g}z} = \hat{\Gamma}(z') e^{2\hat{g}(z-z')} \text{ for lossy lines}$$

$$\hat{\Gamma}(z) = \frac{\hat{V}_m^-}{\hat{V}_m^+} e^{j2bz} = \hat{\Gamma}(z') e^{j2b(z-z')} \text{ for lossless lines}$$

$$\text{Reflection from load } \Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

$$\text{Reflection from generator } \Gamma_g = \frac{Z_g - Z_o}{Z_g + Z_o}$$

Input Impedance of a Transmission Line of Length d with load Z_L

$$Z_{in}(z=0) = Z_o \frac{Z_L + Z_o \tanh gd}{Z_o + Z_L \tanh gd} \text{ for a lossy line}$$

$$Z_{in}(z=0) = Z_o \frac{Z_L + jZ_o \tan bd}{Z_o + jZ_L \tan bd} \text{ for a lossless line}$$

Z_o is real when the line is lossless

Average Power

$$P_{ave}(z) = \frac{1}{2} \text{Re}(\hat{V}(z)\hat{I}^*(z))$$

Standing Wave Ratio

$$SWR = \frac{|V_{\max}|}{|V_{\min}|} = \frac{|I_{\max}|}{|I_{\min}|} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

Transients

Lossless Wave Equation

$$\frac{\partial^2 V}{\partial z^2} = LC \frac{\partial^2 V}{\partial t^2}$$

$$\frac{\partial^2 I}{\partial z^2} = LC \frac{\partial^2 I}{\partial t^2}$$

Voltage and Current Waves

$$V(z,t) = V^+ \left(t - \frac{z}{v_{ph}} \right) + V^- \left(t + \frac{z}{v_{ph}} \right) \equiv V^+ + V^-$$

$$I(z,t) = \frac{V^+}{Z_o} - \frac{V^-}{Z_o}$$

Z_o is also called the surge impedance