

## Preparation Assignments

### Due Monday, September 9

Is it possible for the input impedance of a lossless transmission line with a resistive (real) load to look like a short circuit ( $Z_{in} = 0$ )?

Is it possible for the input impedance of a lossless transmission line with an open circuit load to look like a short circuit ( $Z_{in} = 0$ )?


What condition is necessary for the input impedance of a transmission line to be identical to the load impedance ( $Z_{in} = Z_l$ )? (Zero length transmission lines are not possible.)

### Due Wednesday, September 11

Using formulas 2.25 and 2.29, determine the attenuation constant ( $\alpha$ ), phase constant ( $\beta$ ) and line impedance ( $Z_0$ ) for the lossy lumped parameter model with  $l = 1\text{E-}6$  [H/m],  $c = 1.11\text{E-}11$  [pF/m],  $r = 2.3$  [ $\Omega$ /m],  $g = 0$ .

Does the line impedance differ significantly from our lossless model?

### Due Monday, September 16

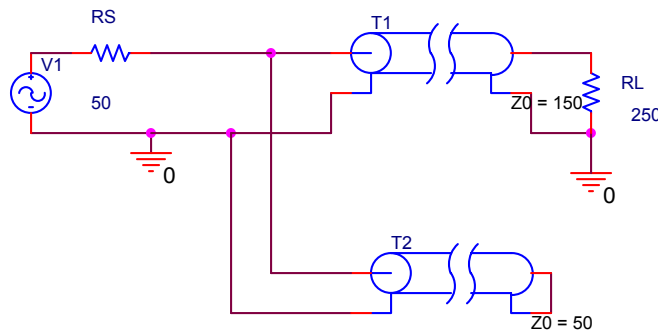

For the above circuit, both transmission lines are 200 [m] in length and have a propagation velocity of  $2.5\text{E}8$  [m/s]. Determine the reflection coefficient looking from T1 to the load (RL), looking from T1 to the source (RS), and the propagation delay of T1.

### Due Monday, September 18

Do well on Quiz 1.