

QUIZ 3

- 1. **555-Timer (25 points)** _____
 - 2. **NAND Gate Circuit (20 points)** _____
 - 3. **Op-Amp (20 points)** _____
 - 4. **Circuit Functionality (26 points)** _____
 - 5. **Short Questions (25 points)** _____
 - 6. **Diodes and Rectifiers (15 points)** _____
 - 7. **Labs, Projects, Demos (19)** _____
- Total** _____