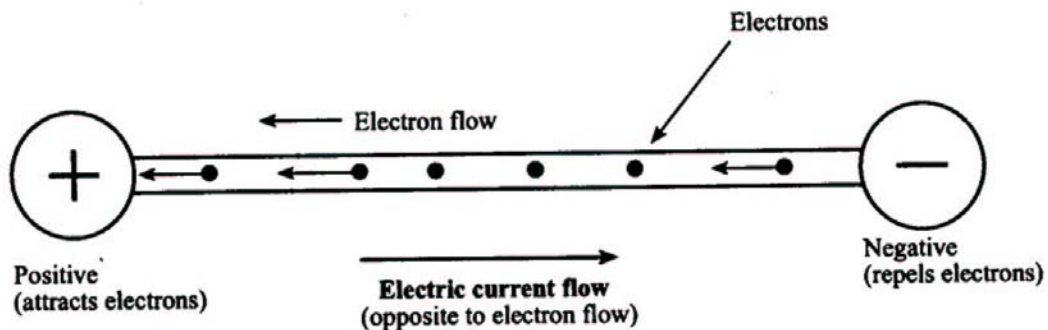


Lecture 2. Transistors

ELECTRON AND CURRENT FLOW

When electrons were discovered and were found to flow through a wire, early investigators believed they flowed from a higher potential to a lower one, similar to water flowing down hill. Further investigation showed that electrons flow from a negative charge to a positive charge. The concept of current flow was developed to explain charged particles moving in semiconductor devices.


When an atom loses an electron a hole is left in the covalent bands. This hole may be considered to have a positive charge, since it lacks a negative one, the charge on the electron. If electron flow is the movement of electrons from a lower potential to a higher one, current flow is the movement of holes from a higher potential to a lower one.




ELECTRON AND CURRENT FLOW DIAGRAM

DIODE

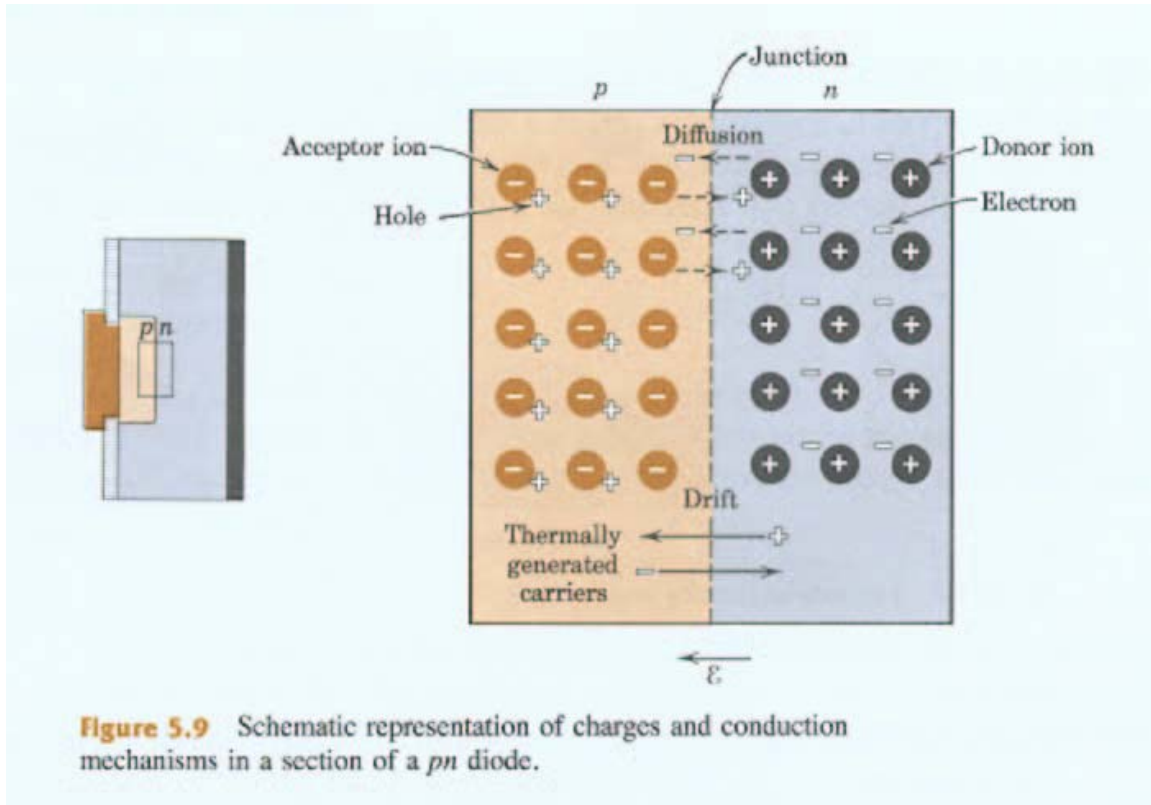A diode is a two terminal electrical device created by joining two materials together, one having an excess of positive charge carriers, P material, and the other having an excess of negative charge carriers, N material. When the two materials are joined there is a migration of carriers across the junction bond creating a depletion region whereby no charged particles reside.



DIFFUSION AT THE PN JUNCTION

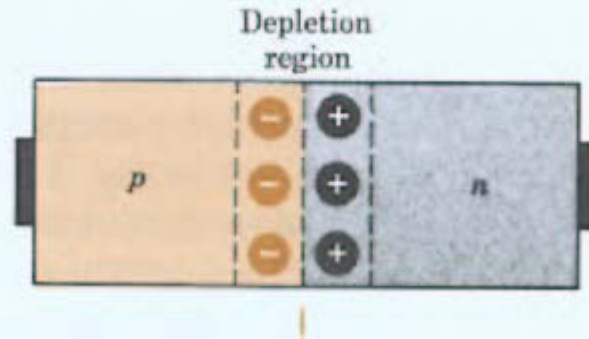

DEPLETION REGION AFTER DIFFUSION

An electric field is created in the depletion region and it has a potential in this area. In order to have current flow through the diode it must be forward biased. Forward biasing makes the depletion region smaller so that it is easier for the current to flow through the device.


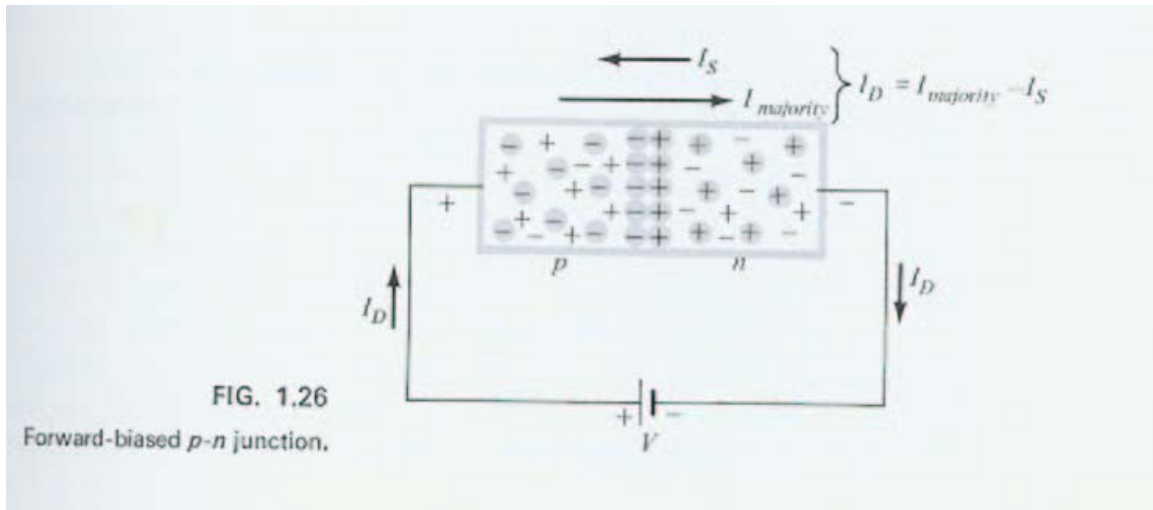


FIG. 1.26

Forward-biased *p-n* junction.

FORWARD BIAS CIRCUIT

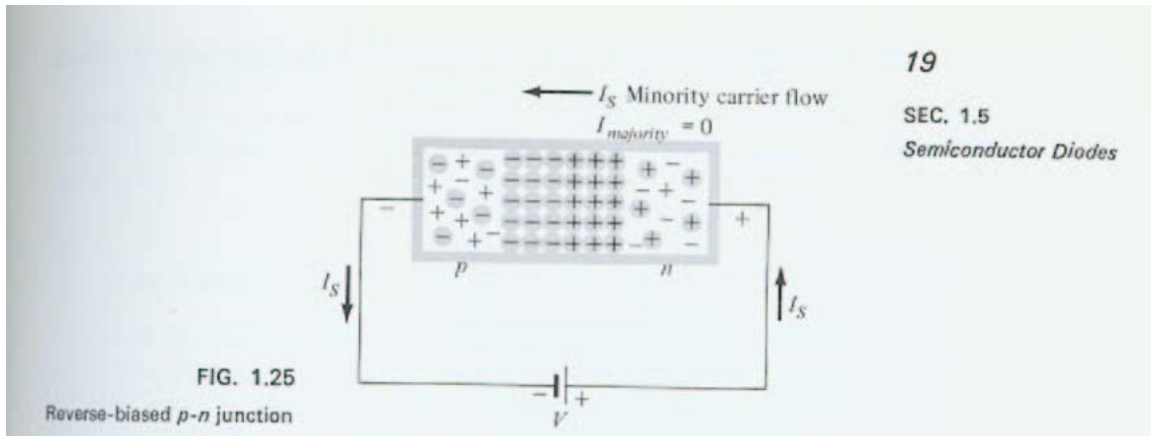
Reversing the bias voltage increases the depletion region.



REVERSE BIAS CIRCUIT

Bipolar Junction Transistor – BJT

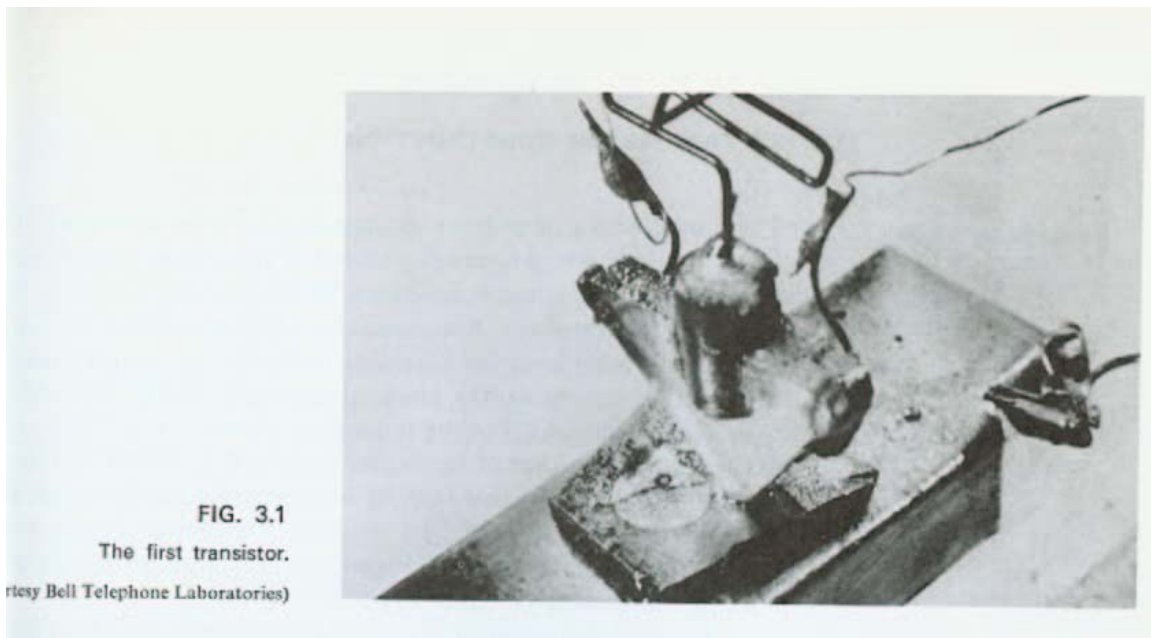Here is a picture of the first bipolar junction transistor invented by Bell Laboratories in New Jersey.



THE FIRST TRANSISTOR

The bipolar junction transistor is basically two diodes connected back to back. The transistors can be made in two different configurations, NPN or PNP. For

our study we will use the NPN since it is more common. There are three terminals which need to be connected for the transistor, base, collector, and emitter. The connection between the emitter and base is forward biased and the connection between the collector and base is reverse biased.

Pictured below is the biasing for an NPN transistor.

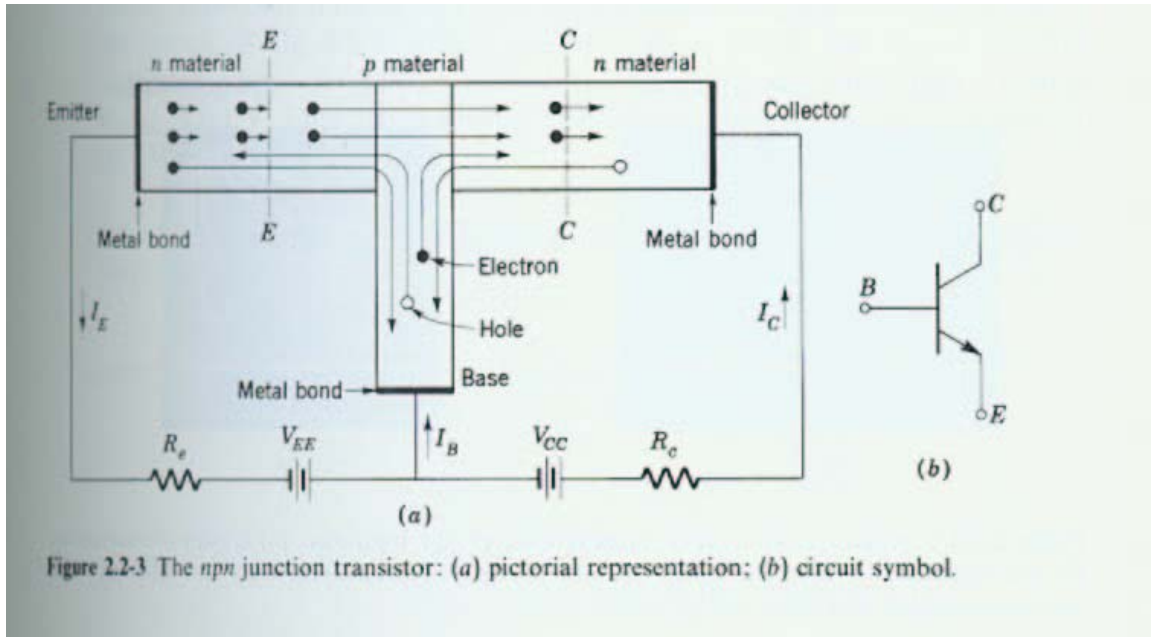


Figure 2.2-3 The npn junction transistor: (a) pictorial representation; (b) circuit symbol.


NPN TRANSISTOR

V_{EE} is connected to the base and emitter terminals so that their junction is forward biased. V_{CC} is connected to the collector and base terminals so that their junction is reverse biased.

A transistor is a current amplifier and usually the collector current is much larger than the base current, $I_C \gg I_B$.

By controlling the base current, I_B , you control the size of the depletion region from the base to the emitter. The narrower the depletion region more electrons flow into the collector.

SCHEMATIC SYMBOLS

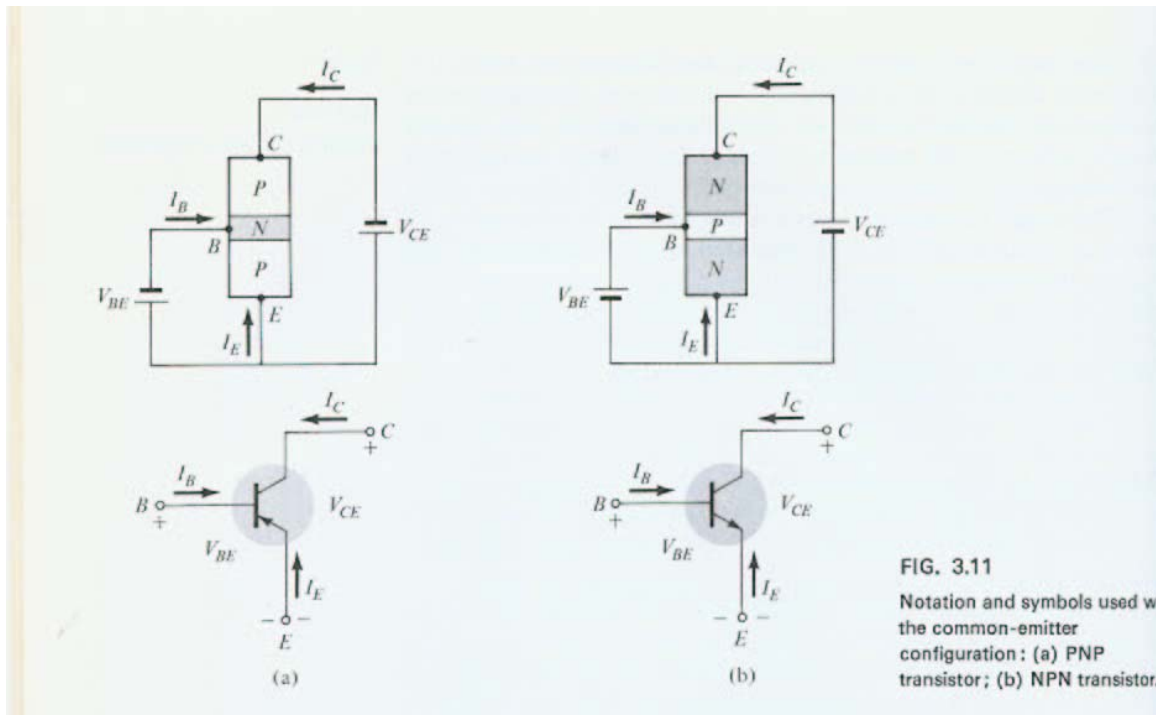

BASIC EQUATIONS

$$I_C = \beta I_B, \quad \beta = \frac{\alpha}{1 - \alpha}, \alpha \text{ is usually given in the spec sheet}$$

$$\beta = \frac{I_C}{I_B}$$

$$\text{Gain} = \frac{\text{output of something}}{\text{input of something}}$$

There are three different ways to connect a transistor in a circuit:

- common base
- common collector
- common emitter

The most widely used configuration is common emitter due to the fact it has power, voltage, and current gain.

COMMON EMITTER CHARACTERISTICS

The characteristic curves of the common emitter configuration are shown below. The input characteristic curve shows that the base-emitter junction must be biased at least by 500 mV before current will flow.

Sec. 3-6

BIPOLAR TRANSISTOR CHARACTERISTICS 71

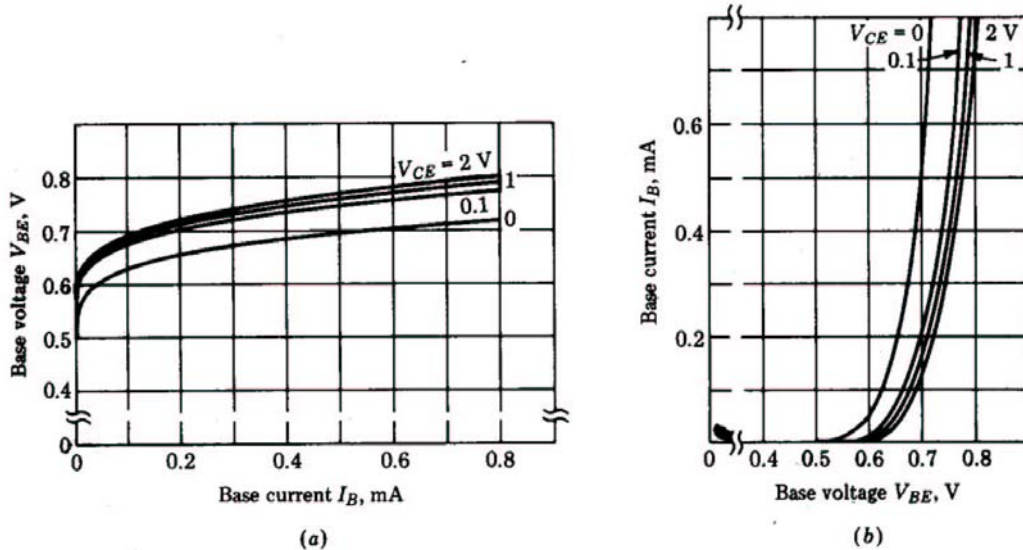


Figure 3-10 (a) Common-emitter input characteristics (V_{BE} versus I_B) for the 2N2222A *n-p-n* transistor. (b) The same characteristics plotted with V_{BE} horizontal and I_B vertical. Note the similarity to a diode curve.

COMMON-EMITTER INPUT CHARACTERISTICS

The output curves show typical collector currents dependent upon the base current supplied by the input circuitry and the voltage drop measured across the collector and emitter terminals.

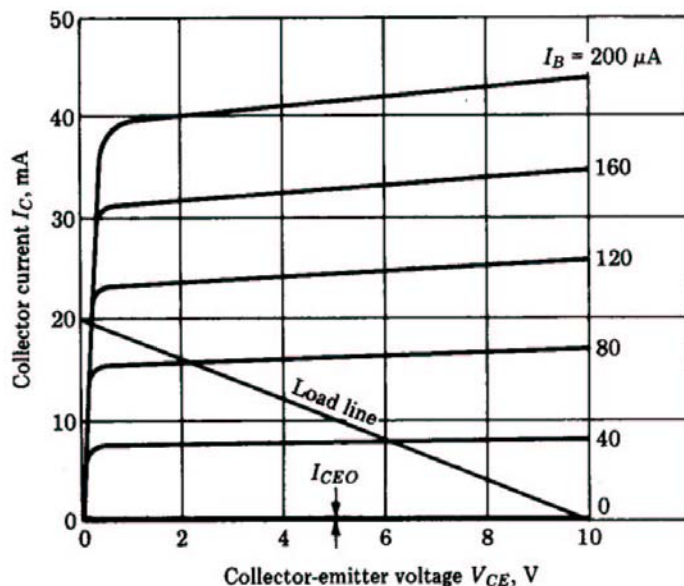



Figure 3-9 Common-emitter output characteristics of a 2N2222A *n-p-n* silicon transistor. A load line corresponding to $V_{CC} = 10$ V and $R_L = 500$ is superimposed.

COMMON-EMITTER OUTPUT CHARACTERISTICS

To make the transistor functional you select resistors that create the base and collector currents, and V_{CE} voltage drop to make it perform to your specifications. If you measure the voltage across the collector and emitter terminals (V_{CE}) and you measure the power supply value (V_{CC}), the collector current (I_C) is zero and the transistor is said to be in the cutoff mode. If V_{CE} is zero volts then I_C is at the load line maximum and is said to be in saturation mode.

TRANSISTOR SWITCH

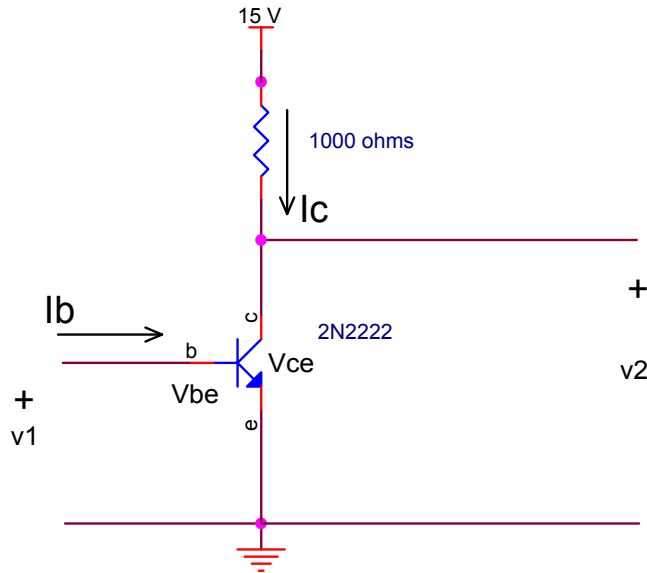Transistors were first used in telephone circuitry to act as a switch. Control signals were applied to the base of the common-emitter input to either have the transistor in the off condition (the transistor in cutoff mode) or on (the transistor in saturation mode). The first step is to create a load line. For this example $V_{CC} = 15$ V and $R_L = 1,000$ Ohms.



2N222 TRANSISTOR IN COMMON-EMITTER CONFIGURATION


Since $V_{cc} = 15V$ the maximum V_{ce} can be is 15V. Therefore the maximum collector current is

$$I_{C \max} = \frac{V_{cc}}{R_L} = \frac{15V}{1K\Omega} = 15mA$$


For this example assume $\beta=50$.

FIND THE CONDITIONS WHERE THE TRANSISTOR ACTS AS A SWITCH

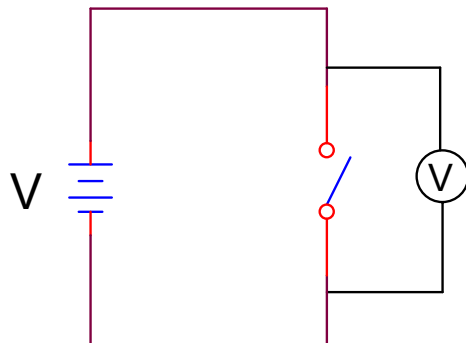The voltage across the switch when it is open is V



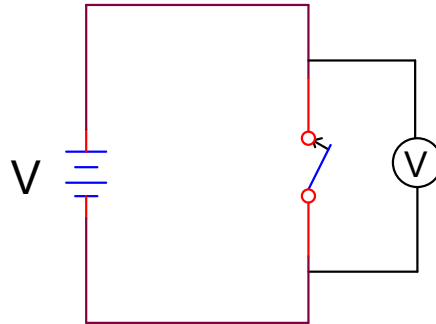The voltage across the switch when it is closed is zero



So, when the voltage across the collector-emitter terminals equals 15V (V_{CC}) the transistor is acting like an open switch and no current is flowing.

When $V_{CE} \approx$ zero volts then the transistor acts like a closed switch.

From the input curve, V_{BE} from 0V to $\approx 0.5V$, $I_B \approx 0$ mA. If $I_B \approx 0$ mA, $I_C = 0$ mA. As seen from above if no current is flowing you have an open circuit. This condition is called cutoff.

Next, select $V_{BE} = 0.7$ V since this is a typical diode conduction voltage. Again, from the input curve, for $V_{CE} = 1.0$ V, $I_B = 0.19$ mA.

$$I_C = \beta I_B = 50(0.17mA) = 8.5mA$$

$$V_{CE} = V_{CC} - 1,000\text{ohms}(8.5mA) = 15V - 8.5V = 6.5V$$

When $V_{BE} = 0.7$ V the transistor is operating in the normal operating range. This is also called the linear range of operation.

Let $V_{BE} = 0.8$ V. From the input curve $I_B > 0.7$ mA. For the analysis select 0.7 mA.

$$I_B = 0.7mA, I_C = 50(0.7mA) = 35mA$$

The power supply is not able to drive this much current through the 1,000 ohm resistor, therefore, with $V_{BE} = 0.8$ V the transistor is supplying all the current it can. This condition is called saturation.

In practical terms, V_{CE} never fully reaches 0V. When a transistor is in cutoff, V_{CE} typically is ≤ 1 V. Since 1 V is much smaller than 15 V, when $V_{CE} \leq 1$ V we can say the switch is closed.

For $V_{BE} \leq 0.5 \text{ V}$, the transistor switch is open.

For $V_{BE} \geq 0.8 \text{ V}$, the transistor switch is closed.

TYPICAL COMMON-EMITTER CIRCUIT WITH LOAD LINE.

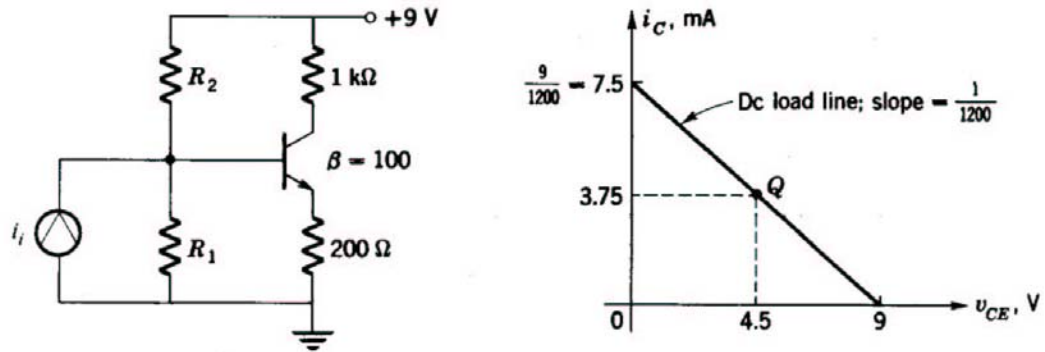


Figure 2.3-6 Circuit and load line for Example 2.3-2.