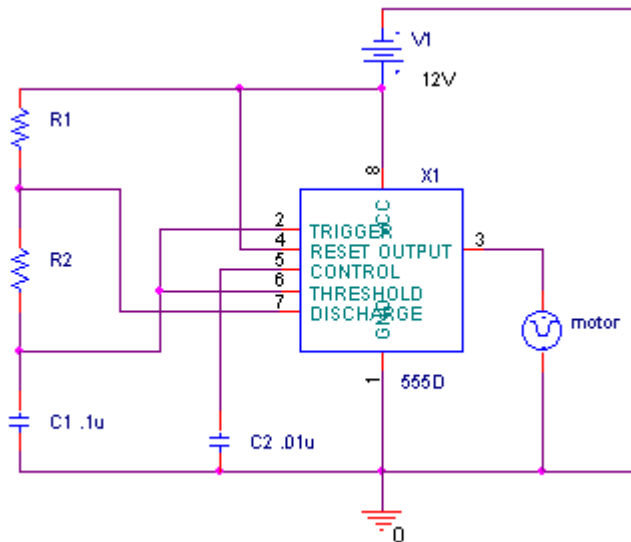


1) 555-Timer (20 pts)

You create the following circuit to control a motor with pulse width modulation:



a) If $R1=1K$ ohms and $R2=3K$ ohms, what will be the duty cycle of the output at pin 3 (8 pts)?

$$\begin{aligned} DC &= T1/(T1+T2) = 0.693(R1+R2)(C1)/0.693(R1+2R2)(C1) \\ &= (R1+R2)/(R1+2R2) \\ &= [(R1/R2)+1] / [(R1/R2)+2] \end{aligned}$$

$$(R1/R2) = 1K/3K = 1/3 \quad DC = 1.333/2.333 = .57 \quad \text{Duty Cycle} = 57\%$$

b) If $R1=3K$ ohms and $R2=1K$ ohms, what will be the duty cycle of the output at pin 3 (8 pts)?

$$(R1/R2) = 3K/1K = 3 \quad DC = 4/5 = .8 \quad \text{Duty Cycle} = 80\%$$

c) Which of the scenarios above (a or b) will cause the motor to spin faster? Why? (4 pts)

b will spin faster because the time it is on relative to the time it is off is greater.

2) Inductance Calculation and Measurement (30 points)

You have found an inductor and wish to determine its inductance. Here is a picture:



You find that it has a wire gauge diameter of 0.51 mm (24 gauge), a length of 14.5 mm, a core diameter of 5.0 mm and 27 turns. You assume that it has an air core ($\mu = 1.257 \times 10^{-6}$ Henries/meter).

a) Calculate the theoretical inductance of the inductor. (5 pts)


$$L = [\mu N^2 \pi r^2 / d] \quad d = 14.5 \times 10^{-3} \text{ m} \quad r = 2.5 \times 10^{-3} \text{ m}$$

$$L = [1.257 \times 10^{-6} \times 729 \times \pi \times 6.25 \times 10^{-6}] / (14.5 \times 10^{-3}) = 1.24 \times 10^{-6} \text{ H}$$

$$L = 1.24 \text{ mH}$$

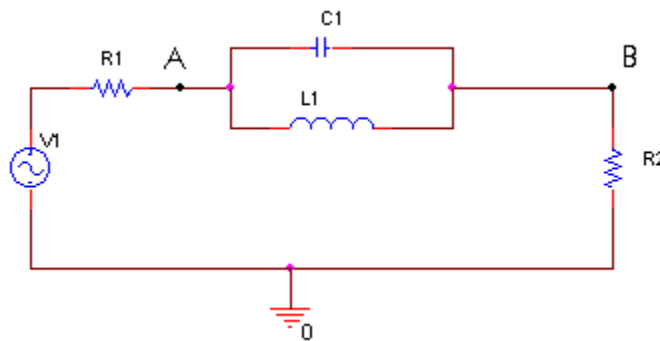b) You wish to verify that the core is indeed air, so you place the inductor into the circuit you used in experiment 9.

[Note: $R_1 = 50$ ohms, $R_2 = 50$ ohms, $C_1 = 0.68 \mu\text{F}$, and L_1 is your inductor.]




You generate the three plots on the following page.


i) Label the three circuits. Which one is at the resonance frequency? below the resonance frequency? above the resonance frequency? (6 pts)

ii) Label the input (point A) and the output (point B) on the plot at resonance on the following page. (4 pts)


Show work here:

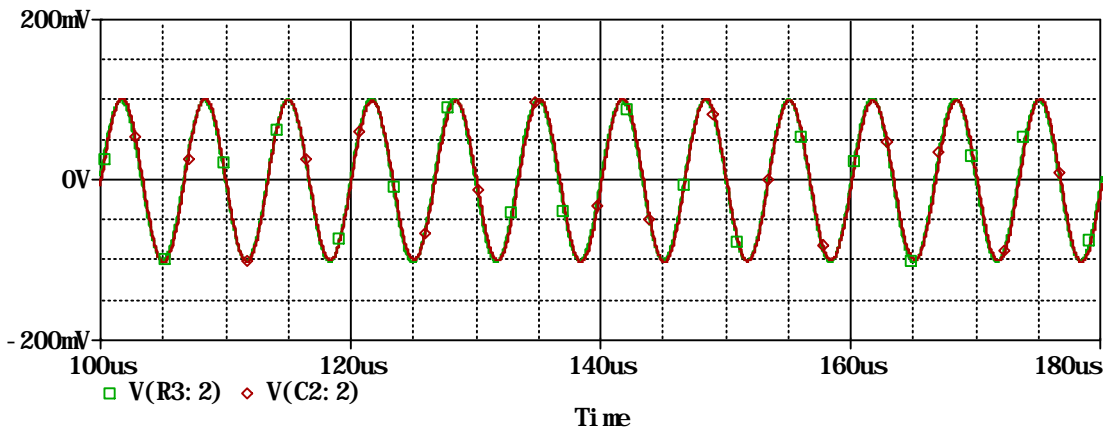
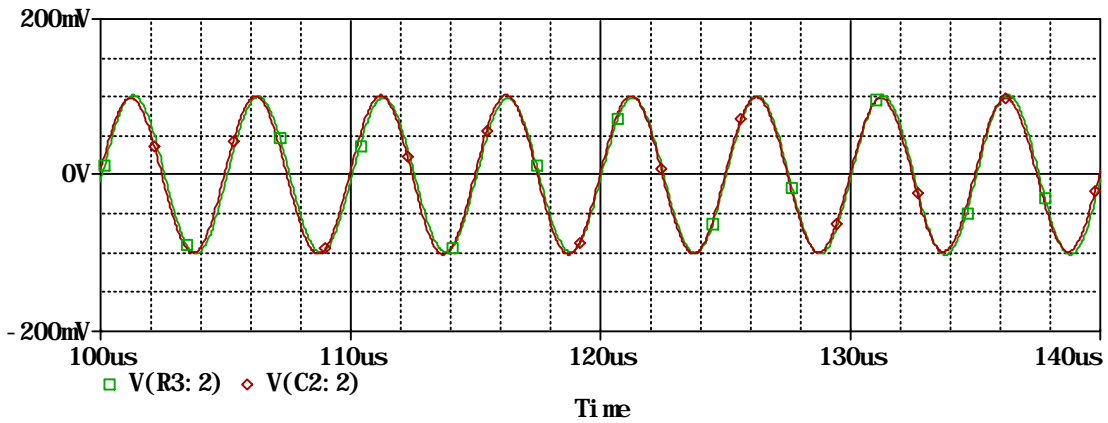
$$f = 12 \text{ cycles} / 80 \text{ms} = 0.15 \text{ Meg Hz} = 1500 \text{K Hz} \quad \text{BELOW RESONANCE}$$


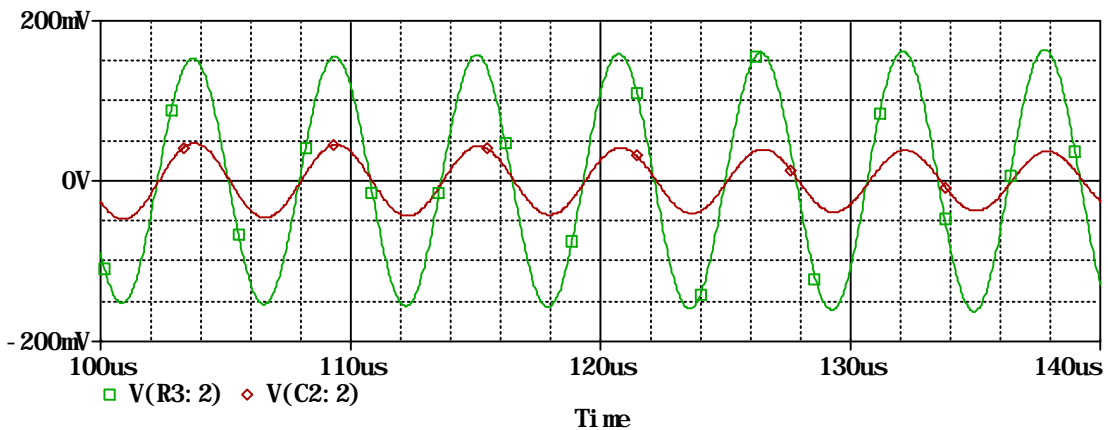
$$f = 8 \text{ cycles} / 40 \text{ms} = 0.2 \text{ Meg Hz} = 2000 \text{K Hz} \quad \text{ABOVE RESONANCE}$$



$$f = 5 \text{ cycles} / (136.3 - 108) \text{ms} = .1767 \text{ Meg Hz} = 1767 \text{K Hz} \quad \text{AT RESONANCE}$$

iii) Given the above plots, calculate the resonance frequency, ω_0 , of your circuit. (3 pts)

$$\omega_0 = 2\pi f_0 = 2 \times \pi \times 1767 \text{K} = 1110.1 \text{K rad/sec} \quad \omega_0 = 1.11 \text{ Meg rad/sec}$$

iv) According to the frequency in iii), what is your inductance? (3 pts)

$$\omega = 1/\sqrt{LC} \quad L = 1/C(\omega)^2 = 1/(1110K)^2(0.68 \times 10^{-6}) = 1.193 \times 10^{-6} H$$

$$L = 1.193 \text{ mH}$$

iv) Given your calculations in part a), calculate the theoretical resonance frequency, ω_0 , of your circuit. (3 pts)


$$\omega_0 = 1/\sqrt{LC} \quad \omega_0 = 1/\sqrt{1.24 \times 10^{-6} \times 0.68 \times 10^{-6}} \quad \omega_0 = 1.089 \text{ Meg rad/sec}$$

c) Does the inductance equation overestimate or underestimate inductance? Is your guess that the core is probably made of air correct? Why or why not? (6 pts)

The equation should overestimate the inductance, as stated in experiment 9. From the two inductances we found here, we have verified that this is true. $1.24 \text{ mH} > 1.19 \text{ mH}$

The values 1.24 mH and 1.19 mH are not exactly alike, but they are very close. The core must be air. If we had used something besides air (like iron, for example) they would be different by several orders of magnitude.

3. Integrator/Differentiator (30 pts)

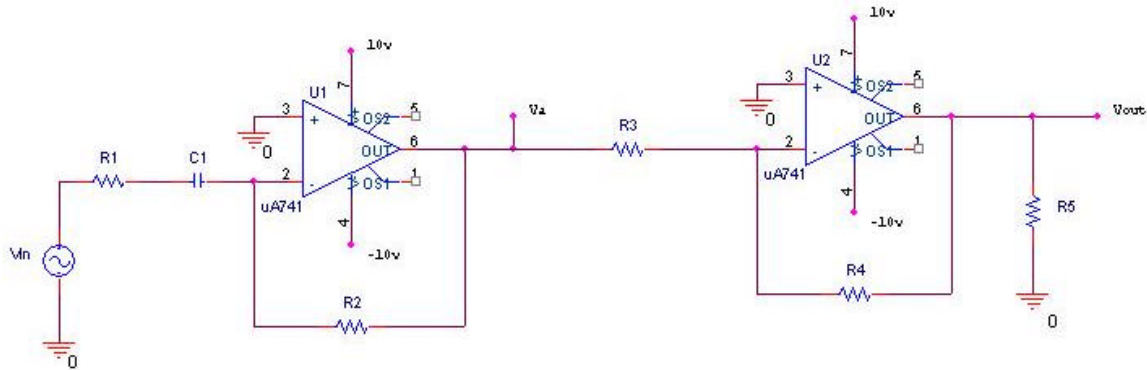

- a) Write down the transfer function for the first circuit $H_1(j\omega) = V_a/V_{in}$? (4 pts)

$$H_1(j\omega) = -(j\omega R_2 C_1) / (1 + j\omega R_1 C_1)$$

- b) Write down the transfer function for the second circuit $H_2(j\omega) = V_{out}/V_a$? (4 pts)

$$H_2(j\omega) = -R_4/R_3$$

- c) Find the total transfer function $H(j\omega) = V_{out}/V_{in}$. (4 pts)

$$H(j\omega) = H_1(j\omega) \times H_2(j\omega) = j\omega R_2 R_4 C_1 / (R_3 + j\omega R_1 R_3 C_1)$$

- d) By calculating the approximate transfer function, show that at frequencies much lower than $\omega_c = 1/(R_1 C_1)$, the circuit acts as a differentiator and at frequencies much higher than ω_c , it acts as an amplifier. (6 pts)

$$H_{Lo}(j\omega) = j\omega R_2 R_4 C_1 / R_3 \quad \text{This is a differentiator.}$$

$$H_{Hi}(j\omega) = j\omega R_2 R_4 C_1 / j\omega R_1 R_3 C_1 = R_2 R_4 / R_1 R_3 \quad \text{This is an amplifier.}$$

- e) In the range where the circuit works as a differentiator, what is the time domain equation for the whole circuit? i.e. write an expression for $V_{out}(t)$ as a function of $V_{in}(t)$ (and the necessary component values). (5 pts)

The time domain equation for a differentiator is $V_{out}(t) = -RC(dV_{in}(t)/dt)$ and $H(j\omega) = -j\omega RC$.

Our integrator has a transfer function of $H(j\omega) = +j\omega R_2 R_4 C_1 / R_3$, therefore the time domain equation must be

$$V_{out}(t) = (R_2 R_4 C_1 / R_3)(dV_{in}(t)/dt) = 0.01(dV_{in}(t)/dt)$$


(If we substitute the values, we get $(R_2 R_4 C_1 / R_3) = 1K \times 10K \times 1m / 1K = .01$)

Name _____

Section _____

Assume $R1 = 100\Omega$, $R2 = 1K\Omega$, $R3 = 1K\Omega$, $R4 = 10K\Omega$, $R5 = 1M\Omega$ and $C1 = 1\mu F$.

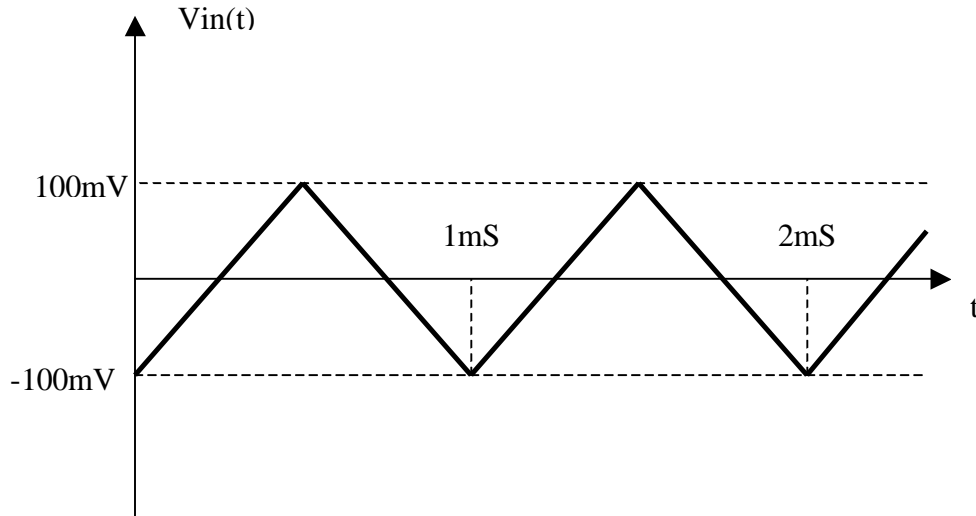f) Assume that the input voltage is the triangular wave shown below, draw the waveform of the output signal $V_{out}(t)$. Make sure that you clearly label all important times and voltages on the plot. (7 pts) (Hint: Compare the frequency of the signal with ω_c and decide how does the circuit act at this frequency.)




$$\omega_c = 1/R1C1 = 1/(100 \times 1\mu) = 0.01 \times 10^6 = 10,000 \text{ rad/sec}$$

$$f_c = \omega_c / (2\pi) = 10000 / (2\pi) = 1600 \text{ Hz}$$


$T = 1\text{ms}$ $f = 1000\text{Hz}$ $1000 \ll 1600$ Therefore, we have a differentiator.

$$\text{slope} = \Delta y / \Delta x = 200\text{mV} / 0.5\text{ms} = 400\text{mV/ms} = 400 \text{ V/s}$$
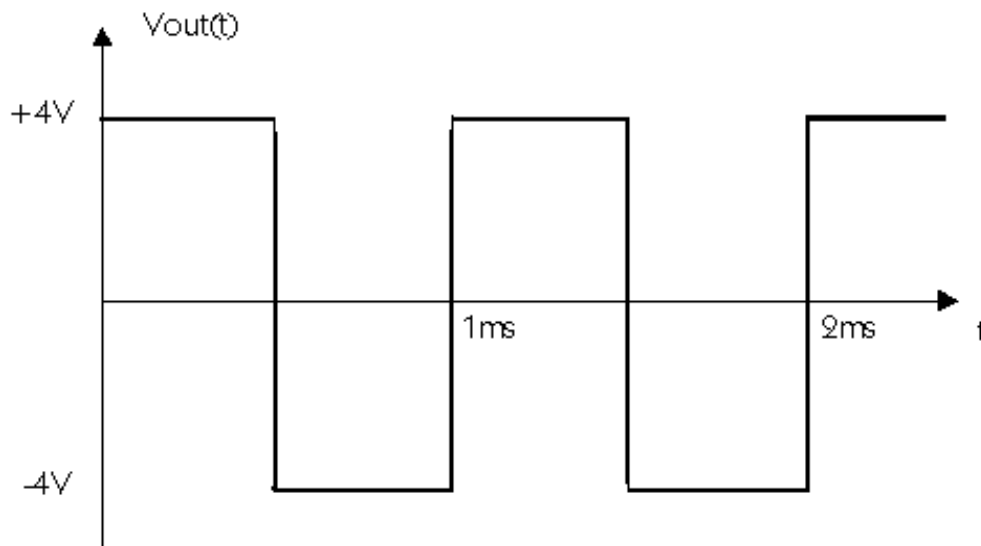
$$V_{out}(t) = 0.01 (dV_{in}(t)/dt) = 0.01 \times 400 = 4\text{V}$$




4. Transformer (20 pts)

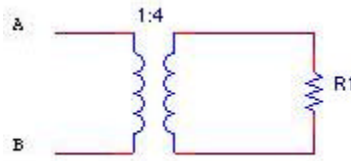

- a) In the circuit above, the transformer is ideal. If $R1=1K\Omega$, find the equivalent impedance, Z_{AB} , seen from points A and B. (6 pts)

$$Z_{AB} = R1/a^2 \quad a=N2/N1=4 \quad Z_{AB} = 1K/16 \quad Z_{AB}=62.5ohms$$

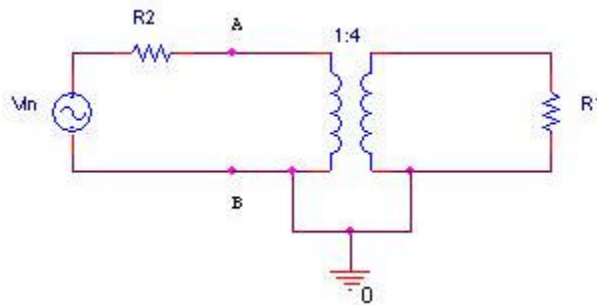- b) We have connected the above circuit to an AC source with a resistor of $R2 = 1K\Omega$.



- If the input voltage has an amplitude of 10V, find the voltage at point A. (8 pts)

$$V_A = [(62.5)/(1062.5)]10V = .588V \quad V_A = 588mV$$

- c) What is the value of the voltage across $R1$? (6 pts)

$$V2/V1 = a \quad V_A = V1 \quad V2 = .588(4) = 2.35V \quad V_{R1}=2.35V$$