

Homework #2

Circuit Transfer Functions

*Due: Tuesday, 23 February (Can be turned in the studio
during open shop times or at Prof. Connor's Office, JEC 6002)*

There is an example in Gingrich that begins on p. 56 where he determines the transfer function of an RLC circuit. Repeat this analysis for the circuit of problem 1 on page 61. That is, do just the analysis of the example, not all that is asked for in the problem statement.