

**Homework 9**  
**Circuit Components and Magnetic Fields – Inductors, Transformers, and ...**

**1. Inductance of a coil**


Remembering from your experiment. The equation for an inductor is given by  $L = (\mu N^2 \pi R^2)/d$  Henries, where the core cylinder has a radius equal to  $R$  and we wind a coil  $N$  times around the cylinder to cover a length  $d$ . If the coil is wound like a coin, and not along the length of the core, then the equation is given by  $L \cong \mu N^2 R \{ \ln(8R/r) - 2 \}$ , where  $R$  is the major radius of the coil and  $r$  is the radius of the wire.

Also recall that  $\mu_0$  has a different constant value depending upon the ferromagnetic properties of the material the inductor is wound around. Here are some typical values for  $\mu$ .

MATERIAL	$\mu$ in Henries/meter
air	$4\pi \times 10^{-7}$
iron	$1200 (4\pi \times 10^{-7})$


Find the inductance for the following three coils based on the appropriate equation given for  $L$ .

a. Coil 1

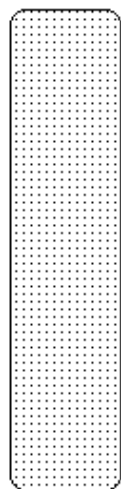


turns = 60  
 $R = .01$  m  
 gauge = 18  
 core = air  
 $d = .1$  m

b. Coil 2

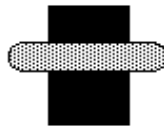

turns = 30  
 $R = .01$  m  
 gauge = 22  
 core = iron  
 $d = .001$  m

c. Coil 3

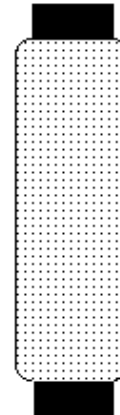

turns = 40  
 $R = .01$   
 gauge = 18  
 core = iron  
 $d = .08$  m

**2. Resistance of a Coil**


The resistance of a coil is given by  $R = l/(\mathcal{S}A)$  where  $l$  is the length of the wire,  $A$  is the cross sectional area of the wire (thickness), and  $\mathcal{S}$  is the conductivity of the wire material. For copper, the conductivity is about  $6 \times 10^7$  Siemens/meter. Assuming all coils above are made of copper. Find the resistance of each coil.

a. Coil 1

b. Coil 2

c. Coil 3

**3. Transformers**

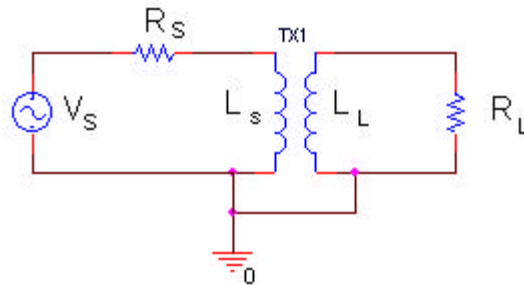

Assume coils 1 and 3 are connected together with an iron core and used as a transformer. Use coil 3 for the source inductance and coil 1 for the load inductance. The equation for the impedance of the transformer is given by  $Z_{in} = R_L/a^2$  where  $R_L$  is the resistance of the load circuit and  $a^2 = L_L/L_S$ . You can find the current through the loops by applying the following equations:  $I_L/I_S = 1/a$  or  $N_S I_S = N_L I_L$ . Additionally, the induced output voltage can be found using  $V_L/V_S = N_L/N_S$ . (Assume  $R_S = R_L = 50$  ohms and  $V_S = 20$  Volts). Find...

- a. the inductance of coil 1 when it is wound around the iron core.
  
  
  
  
  
  
  
  
  
  
- b. the input impedance,  $Z_{in}$ , of the transformer
  
  
  
  
  
  
  
  
  
  
- c. the output voltage of the secondary coil,  $V_L$
  
  
  
  
  
  
  
  
  
  
- d. the current through the primary coil
  
  
  
  
  
  
  
  
  
  
- e. the current through the secondary coil
  
  
  
  
  
  
  
  
  
  
- e. recalling the equation for power  $P = I^2 R$ , explain how the voltage induced in the second coil could possibly be bigger than the input voltage.

**Electronic Instrumentation**  
**ENGR-4300 Spring 2002 Section \_\_\_\_**

**4. Digital Electronics**

Read through sections 7.1-7.3 at the following website:  
<http://www.phys.ualberta.ca/~gingrich/phys395/notes/node117.html>

Here is a proof of De Morgan's first law.

$$\overline{A \bullet B} = \bar{A} + \bar{B} \quad \text{This can also be written } \sim(A \bullet B) = (\sim A) + (\sim B)$$

A	B	$\sim A$	$\sim B$	$A \bullet B$	$\sim (A \bullet B)$	$(\sim A) + (\sim B)$
0	0	1	1	0	1	1
1	0	0	1	0	1	1
0	1	1	0	0	1	1
1	1	0	0	1	0	0

Can you prove De Morgan's second law?

$$\overline{A + B} = \bar{A} \bullet \bar{B} \quad \text{This can also be written } \sim(A + B) = (\sim A) \bullet (\sim B)$$

A	B	$\sim A$	$\sim B$	$A + B$	$\sim (A + B)$	$(\sim A) \bullet (\sim B)$
0	0					
1	0					
0	1					
1	1					