
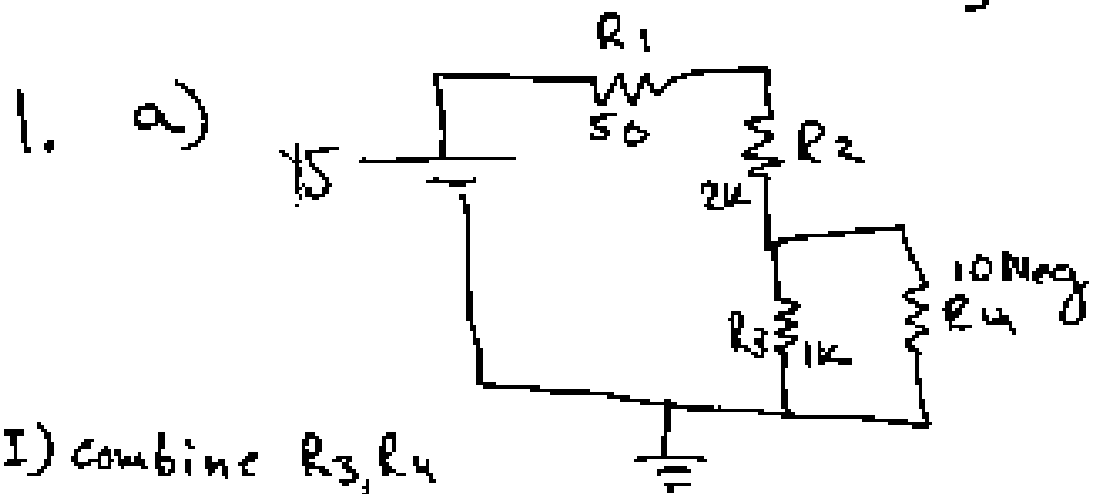


# HW #1 Solutions

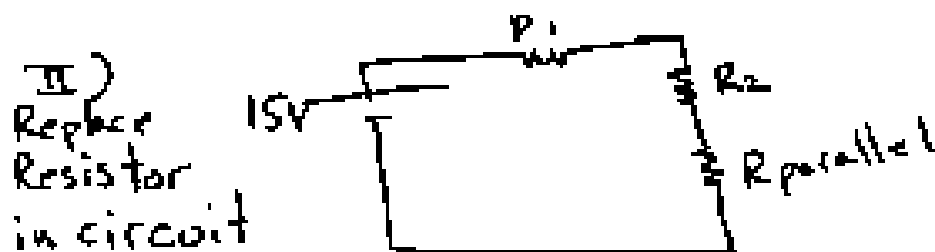

I) combine  $R_3, R_4$   
in parallel

$$\frac{R_3 \cdot R_4}{R_3 + R_4} = \frac{1k \cdot 10Meg}{1k + 10Meg} = 999.9 = R_{parallel}$$



III) All resistors now in series  
Add them

$$R_{eq} = R_1 + R_2 + R_{parallel}$$

$$R_{eq} = 50 + 2000 + 999.9$$

$$R_{eq} = 3049.9 \approx 3050$$

B)

HW #1 solutions

I) Do parts C, and D first

II)  $V = I_1 R_1$  ohm's law

for  $R_1$   $V = .25$   $R = 50$

$$I_1 = \frac{.25 \text{ V}}{50}$$

$$I_1 = 5 \mu\text{A}$$

$R_2$  has the same current because it is in series. THE CURRENT ONLY HAS ONE PATH.

check.  $V = I_2 R_2$   $V_2 = 9.84 \text{ V}$   $R_2 = 2000$

$$I_2 = \frac{9.84 \text{ V}}{2000} = 4.92 \mu\text{A} \approx 5 \mu\text{A}$$

$$V_3 = I_3 R_3$$

$$V_3 = 4.91 \text{ V} \quad R_3 = 1000$$


$$I_3 = \frac{4.91}{1000} = 4.91 \mu\text{A}$$

$$V_4 = I_4 R_4 \quad V_4 = 4.91 \text{ V} \quad R_4 = 10 \text{ M}\Omega$$

$$I_4 = \frac{4.91 \text{ V}}{10 \text{ M}\Omega} = 491 \text{ nA}$$

\* Most current goes through  $R_3$  because  $R_4 = 10 \text{ M}\Omega$  is so big. Current takes path of least resistance.

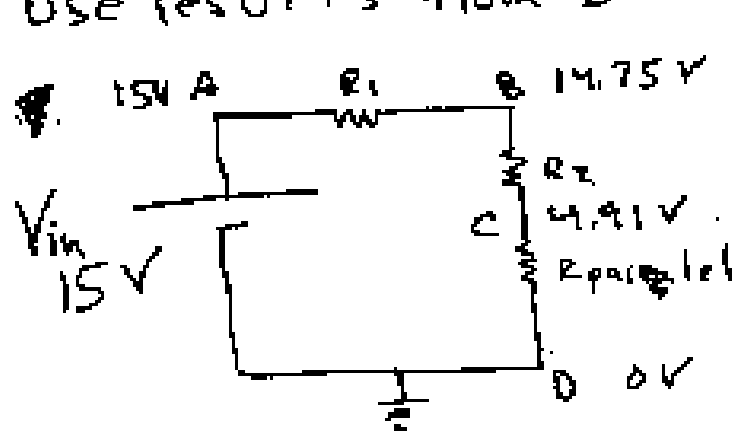c) Find Voltage across  $R_1, R_2, R_3, R_4$   
 use results from D



Check ✓  
 use KVL  
 + contribution of voltage + to equal the total V drop across all resistors  
 $V_{in} = V_{R1} + V_{R2} + V_{R3,4}$   
 $V_{in} = 0.25 + 9.84 + 4.91$   
 $V_{in} = 15 \text{ should be } 15$


$R_1$  Voltage across  $R_1 = A - B$   
 $15 - 14.75$   
 $V_{R1} = 0.25 \text{ V}$

$R_2$  Voltage across  $R_2$   
 $B - C = 14.75 - 4.91 = V_{R2} = 9.84 \text{ V}$


$R_3, R_4$  Voltage across  $R_3, R_4$   
 is the same  $V_{R3, R4}$   
 $V_{R3, R4} = C - D = 4.91 - 0 = 4.91$

Why?

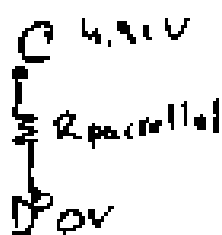Voltage is the same across resistors in parallel  
 \* Current will be different.




Expand back to original

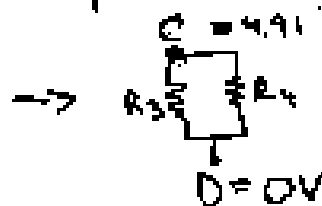

D Find voltage at points A, B, C, D

II) use results of part I) a) II)

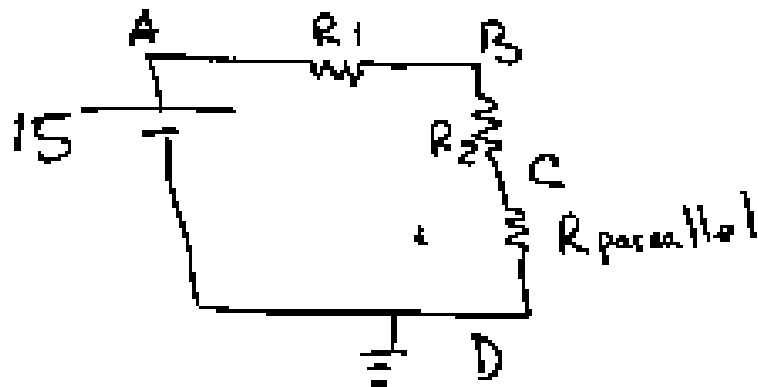

Do voltage divider and observation

A is across voltage supply

$$A = 15 \text{ V}$$

D is at ground

$$D = 0 \text{ V}$$

C use voltage divider

$$V_{out} = \frac{R_x}{R_x + R_y} V_{in}$$



$$V_{at C} = \frac{R_{parallel}}{R_{parallel} + R_1 + R_2} (15 \text{ V}) = \frac{1000(15)}{1000 + 50 + 200}$$

$$C = 4.91 \text{ V}$$

cont. on next  
- 100 +

D) Find Voltage at A, B, C, D cont.

B use voltage divider

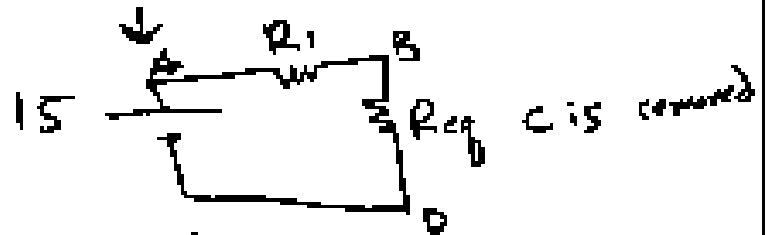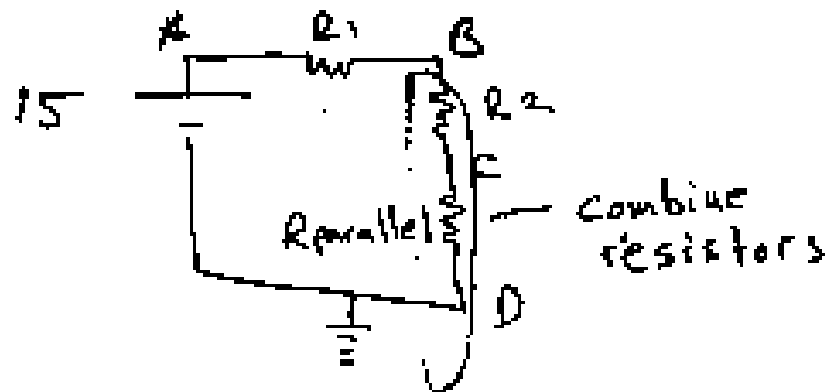


$$R_{eq} = R_2 + R_{parallel}$$


$$V_{at B} = \frac{R_{eq} (15)}{R_{eq} + R_1} = \frac{3000 (15)}{3000 + 50} = 14.75$$

$$B = 14.75 V$$

# Wheat Stone Bridge

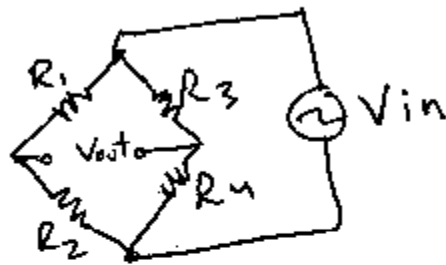

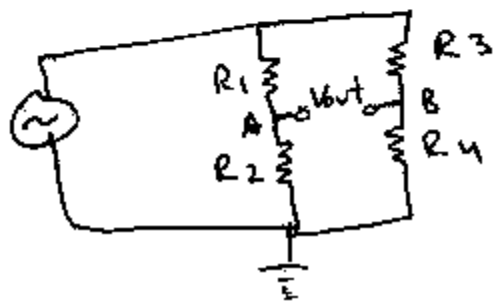Follow circuit paths to determine  
PSPICE Equivalent.



$$V_{out} = V_A - V_B$$