

Homework #4 Solution

The feedback impedance = $R = Z_{\text{feedback}}$

The input impedance = $R_S + 1/(j\omega C) = Z_{\text{in}}$

Then, $V_{\text{out}} = -(Z_{\text{feedback}}/Z_{\text{in}}) V_{\text{in}}$

From page 111, to act like an ideal differentiator, $V_{\text{out}} = -j\omega RC V_{\text{in}}$

This is only true when $R_S \ll (1/\omega C)$ or when $\omega \ll 1/(R_S C)$

Remember that $\omega = 2\pi f$

To select some component values and a frequency, we can use the values from problem 4 on last semester's Quiz 3.


$C = 0.2\mu\text{F}$, $R = 10\text{k}\Omega$, $R_S = 50\Omega$

Then, $R_S C = 10 \times 10^{-6} = 10^{-5}$


$f \ll 1/(2\pi \times 10^{-5}) = 1.6 \times 10^4$

$f = 1\text{kHz}$ should easily satisfy this inequality.

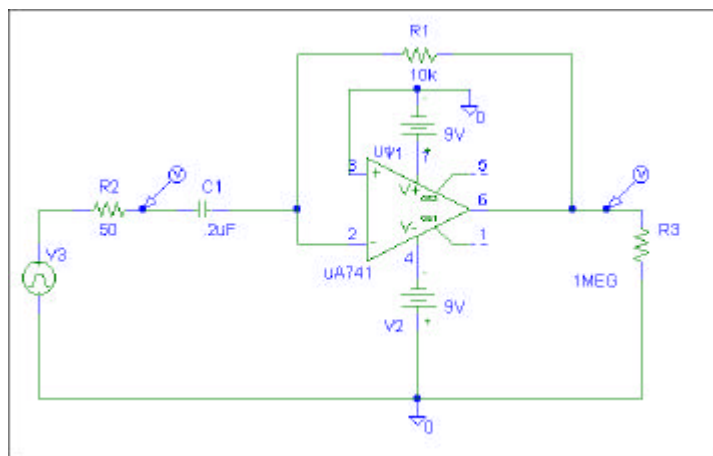
The circuit from Quiz 3 is shown below. We need to change to a sinusoidal source.



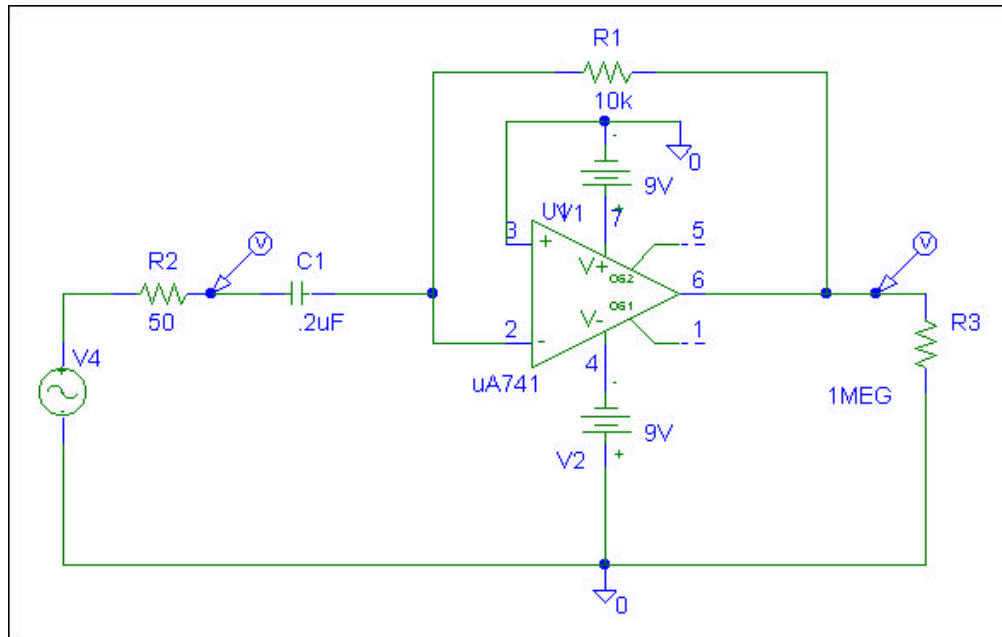The new circuit and its probe outputs follow:



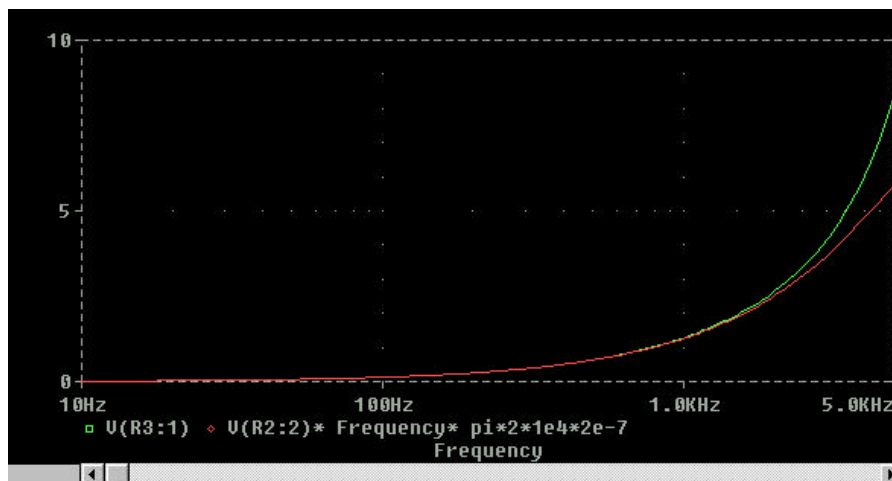The only change to the circuit is the sinusoidal source rather than the pulse



source. The AC sweep shown demonstrates that the circuit works like a differentiator for frequencies above 1kHz, since essentially both sides of equation 6-20 are plotted. The transient analysis again shows the differentiator is working at 1kHz, since the output voltage is 90° out of phase with the input.

