

1) Read the pages in Essence of Analog Electronics indicated in Experiment 8 (76-79, 88-99, 127,128)

2) Write the equation that goes with each op amp, Voltage Summer, Integrator, Differentiator, Follower. Draw the schematic next to the equation. Make sure you understand how these op amps behave. They WILL be on your next test.