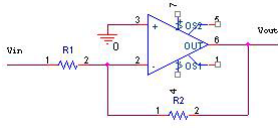
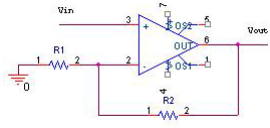
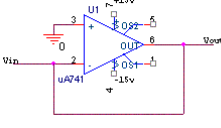
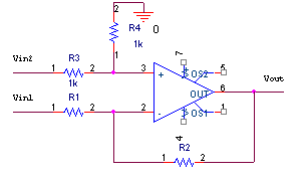
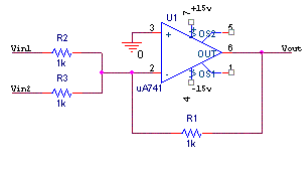


## Op-Amps:

- Op-Amp Rules (when negative feedback exists): 1.  $V_+ = V_- = 0$  2.  $I_+ = I_- = 0$
- Op-Amp Circuits:

<p><b>Inverting Amplifier</b></p>  $A_V = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$	<p><b>Non-Inverting Amp.</b></p>  $A_V = \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$	<p><b>Buffer</b></p>  $A_V = \frac{V_{out}}{V_{in}} = 1$
<p><b>Differential Amplifier</b></p>  <p>If <math>R_1 = R_3</math> and <math>R_2 = R_4 \Rightarrow V_{out} = \frac{R_2}{R_1}(V_{in2} - V_{in1})</math></p>	<p><b>Adder</b></p>  $V_{out} = -\frac{R_1}{R_2}V_{in1} - \frac{R_1}{R_3}V_{in2}$	

### Some useful identities on complex numbers:

- Complex number representations:  $z = x + jy = re^{j\theta}$ ,  
 $j = \sqrt{-1}$
- Euler's identity:  $e^{j\theta} = \cos\theta + j\sin\theta$
- Polar to Cartesian transform:  $x = r\cos\theta$ ,  $y = r\sin\theta$
- Cartesian to Polar transform:  $r = \sqrt{x^2 + y^2}$ ,  $\theta = \tan^{-1}\frac{y}{x}$
- $z_3 = z_2 z_1 \Rightarrow |z_3| = r_3 = r_2 r_1, \angle z_3 = \theta_3 = \theta_2 + \theta_1$
- $z_3 = z_2 / z_1 \Rightarrow |z_3| = r_3 = r_2 / r_1, \angle z_3 = \theta_3 = \theta_2 - \theta_1$

Table of $\tan^{-1}$	
$A$	$\tan^{-1} A$
0	0, $\pi$
$\infty$	$\pi/2$
$-\infty$	$-\pi/2$
1	$\pi/4, 3\pi/4$
-1	$-\pi/4, -3\pi/4$

### Phasors:

- Definition of phasor:  $v(t) = A\cos(\omega t + \phi) \Rightarrow \vec{V} = Ae^{j\phi}$
- Time signal given phasor  $v(t) = \text{Re}\{\vec{V}e^{j\omega t}\} = \text{Re}\{Ae^{j(\omega t + \phi)}\} = A\cos(\omega t + \phi)$


### Impedances:

Resistor	Capacitor	Inductor
$\vec{V}_R = Z_R \vec{I}_R$	$\vec{V}_C = Z_C \vec{I}_C$	$\vec{V}_L = Z_L \vec{I}_L$
$Z_R = R$	$Z_C = \frac{1}{j\omega C}$	$Z_L = j\omega L$

- Impedances in series:  $Z_{eq} = Z_1 + Z_2 + \dots + Z_N$
- Impedances in parallel:  $\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$
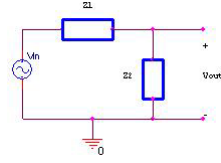
## Transfer Functions

- Definition:  $H(j\omega) = \frac{\vec{V}_{out}}{\vec{V}_{in}}$



- For a voltage divider (see figure):  $H(j\omega) = \frac{Z_2}{Z_1 + Z_2}$

- Corner Frequencies RC circuit:  $\omega_c = 1/RC$  RL circuit:  $\omega_c = R/L$
- Resonance Frequency RLC circuit:  $\omega_0 = 1/\sqrt{LC}$

## Approximations of transfer functions:

- Low Frequencies:  $\frac{A_n \omega^n + A_{n-1} \omega^{n-1} + \dots + A_k \omega^k}{A_m \omega^m + A_{m-1} \omega^{m-1} + \dots + A_r \omega^r} \approx \frac{A_k \omega^k}{A_r \omega^r} = \frac{A_k}{A_r} \omega^{k-r}$
- High Frequencies:  $\frac{A_n \omega^n + A_{n-1} \omega^{n-1} + \dots + A_k \omega^k}{A_m \omega^m + A_{m-1} \omega^{m-1} + \dots + A_r \omega^r} \approx \frac{A_n \omega^n}{A_m \omega^m} = \frac{A_n}{A_m} \omega^{n-m}$



## Diodes models:

- Exact formula:  $I_D = I_S (e^{\frac{V_D}{V_T}} - 1)$ ,  $I_S$ : Saturation current,  $V_T = 25.9mV$ ,  $n \approx 1-2$



<p style="text-align: center;"><b>Ideal Diode</b></p> $\begin{cases} \text{On: } V_D = 0 & I_D > 0 \\ \text{Off: } I_D = 0 & V_D < 0 \end{cases}$	<p style="text-align: center;"><b>Von Model</b></p> $\begin{cases} \text{On: } V_D = V_{on} & I_D > 0 \\ \text{Off: } I_D = 0 & V_D < V_{on} \end{cases}$
<p style="text-align: center;"><b>Zener Diode</b></p> $\begin{cases} \text{On: } V_D = V_{on} & I_D > 0 \\ \text{Off: } I_D = 0 & V_z < V_D < V_{on} \\ \text{Zener: } V_D = -V_z & I_D < 0 \end{cases}$	<p style="text-align: center;"><b>Zener Diode, with knee current</b></p> $\begin{cases} \text{On: } V_D = V_{on} & I_D > 0 \\ \text{Off: } I_D = 0 & V_z < V_D < V_{on} \\ \text{Zener: } V_D = -V_z & I_D < -I_{knee} \end{cases}$

## Diode Circuits:



### Half-Wave Rectifier

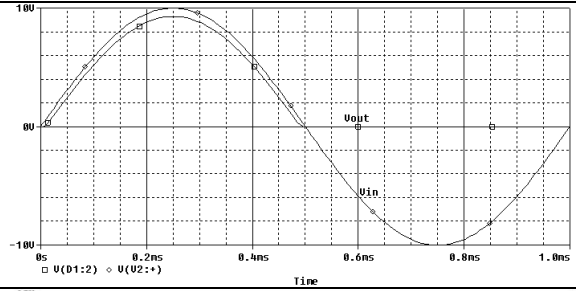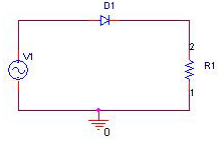



### Half-Wave Rectifier with Smoothing

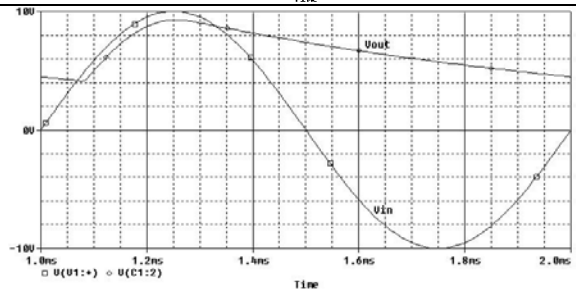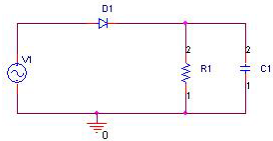

### Full-Wave Rectifier

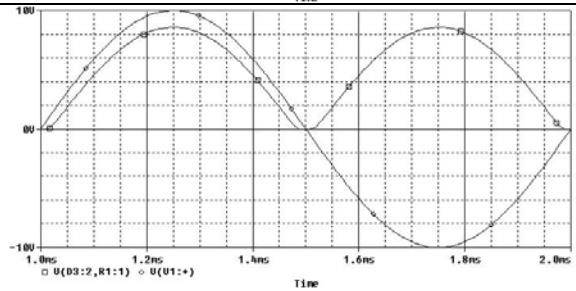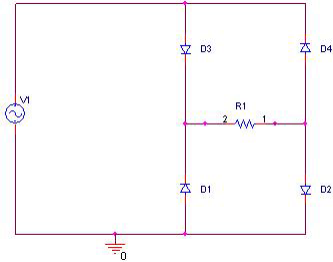

### Full-Wave Rectifier with Smoothing

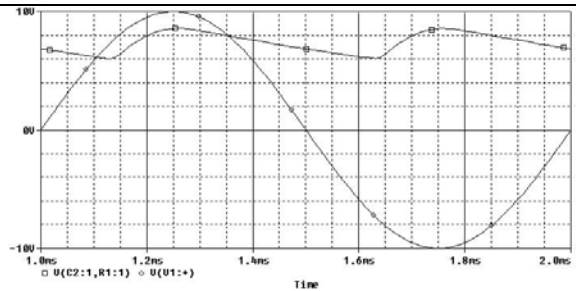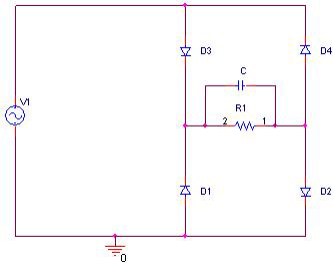

### Limiter

