


Standing Wave Patterns

Reading assignment

Ulaby, 2-5.1, 2-5.2

Experiment 1 - Standing wave pattern - lumped line

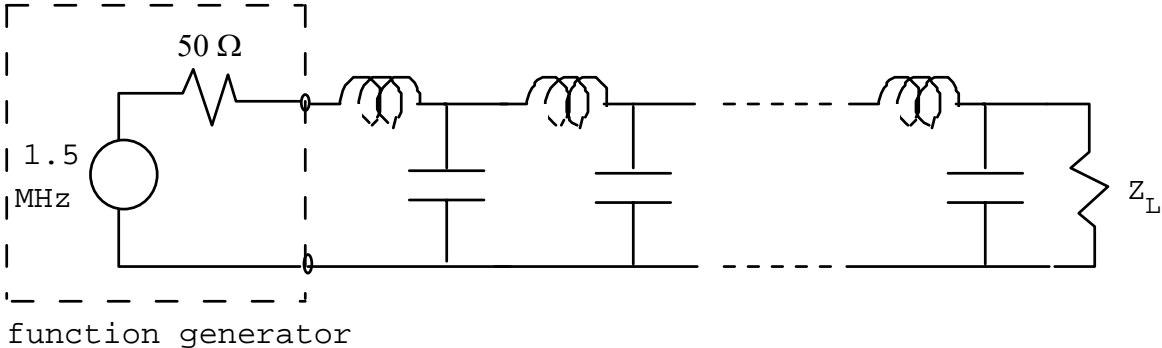Obtain a lumped model of a transmission line and connect it as shown. This lumped line models an 80 meter length of RG-58 A/U coaxial cable and each L-C section has an equivalent length of 4 meters. Set the function generator amplitude to 1 V P-P.




- a. Set $Z_L = 93 \Omega$.
 - 1) Measure the voltage magnitude as a function of node number and sketch the result. (Suggestion: first measure the even nodes, then the odd nodes).
 - 2) How many nodes separate V_{\max} and V_{\min} locations? Convert your answer to an equivalent length in the coaxial line.
 - 3) What is V_{\max}/V_{\min} ?
- b. Repeat part a. for $Z_L = \infty$, $Z_L = 50$, and $Z_L = 0$. To save time, you don't need to record all values. Concentrate on finding V_{\max} , V_{\min} , and their locations.
- c. Repeat part b. with a capacitor of 3.3 nF. What happens to the V_{\max} and V_{\min} locations?
- d. Run the `sing_bnd.m` code (Matlab file in the waves folder) which illustrates standing wave patterns.

Standing Wave Patterns

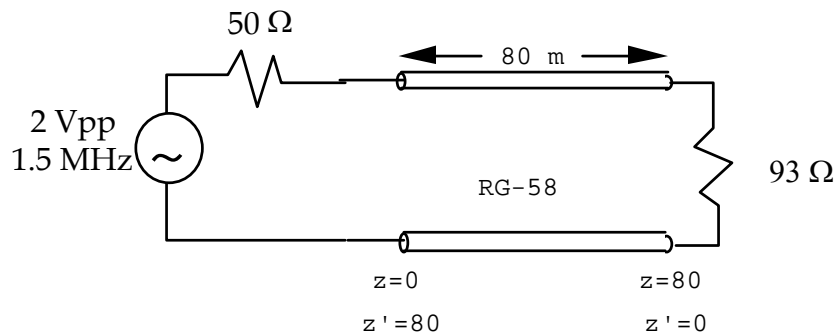Problem 1 - Standing wave pattern - coaxial cable

The equivalent coaxial cable circuit for Experiment 1 is shown below. You should compare answers with the experiment wherever you can.



RG 58 coaxial cables have the following parameters: $a = 0.4 \text{ mm}$, $b = 1.4 \text{ mm}$, R_C or $Z_0 = 50 \Omega$, $l = 2.5 \times 10^{-7} \text{ H/m}$, $c = 1 \times 10^{-10} \text{ F/m}$, and $\epsilon_r = 2.3$.

- Determine β and the wavelength λ at 1.5 MHz. Take your measurement of the distance between V_{\max} and V_{\min} from the experiment and express in terms of λ . What is the distance between two maxima?
- Determine the reflection coefficient at the load, Γ_L and the standing wave ratio, VSWR.
- Assume that the forward traveling wave has an amplitude of 1 Volt. Sketch the standing wave pattern for voltage and current. Include numbers for amplitudes and distances.
- Under what conditions do you get a voltage maximum at the load? a minimum?
- If the load is a 3.3 nF capacitor, what is the reflection coefficient at the load? Where is the location of the first minimum?

Experiment 2 - Input impedance, lumped line

Set $Z_L = 0$ on the lumped line. Examine the signal at both the input and output of the lumped line.

- Set the frequency to 1 kHz. Does the input look like it is shorted?
- Increase the frequency to 400 kHz. Does the input look like it is shorted?