


## Transmission line matching &amp; Smith charts

**Reading assignment**


Popović and Popović, Chapter 18.6

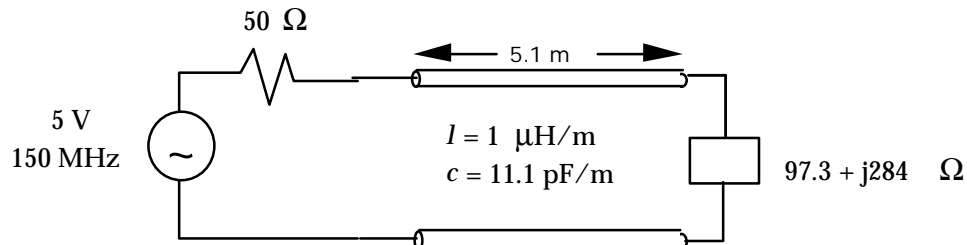**Problem 1 - Matching a complex load**

The following transmission line problem has a complex load as is often encountered in antenna applications. Assume the transmission line is lossless.



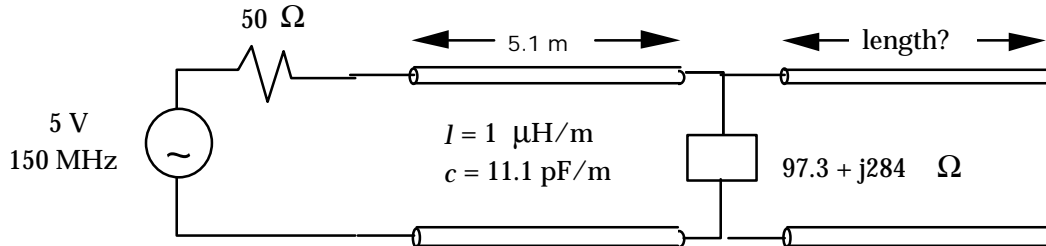- Find the reflection coefficient.
- Determine the standing wave ratio on the transmission line.



- A second transmission line can be added in parallel to the load to give a total impedance that is real. What  $Z_{\text{line}}$  in parallel with the load gives a total impedance that is real? (Hint: Use admittances  $Y = 1/Z$ ).
- Determine the length of open-circuited transmission line that gives the desired  $Z_{\text{line}}$ .
- Calculate the new reflection coefficient and standing wave ratio for the modified load. Compare with the answers to part a. and b.

**Problem 2 - Smith chart***Unmodified load*

- Find the normalized impedance of the unmodified load of Problem 1a and locate it on the Smith chart.
- Determine the reflection coefficient of the unmodified load.

*Modified load*

- In Problem 1c and 1d, you determined that an open circuited transmission line with  $Z_{\text{line}} = -317.3j$  could be used to reduce reflections. Locate the position on the Smith chart of the open circuit load and  $Z_{\text{line}}$ . Use the Smith chart to find the length of transmission line needed to create  $Z_{\text{line}}$ .
- Locate the modified load on the Smith chart. Then use the Smith chart to determine  $Z_{\text{in}}(z=0)$ .